



Answer the following questions:

Q1: Complete the following sentences:

- i. The two basic types of full wave rectifier areand
- ii. The output frequency of half wave rectifier isthe input frequency.
- iii. Diode..... add a DC level to an AC voltage.
- iv. The..... operates in reverse breakdown.
- v. The DC value of a full wave rectifier voltage with a peak value of 50 is.....
- vi. Diode cut-off voltage above or below specified levels.
- vii. is the common base current gain of the transistors.
- viii. The bias methods for discrete BJT circuit are using,, and
- ix. In common emitter amplifier, the input and output voltages are..... phase.
- x. In common emitter amplifier the gainwith the emitter resistance.
- xi. In common collector amplifier, the input resistance is....., and the output resistance is

Q2: (a) Find the values of I and V in the circuits shown in Fig. (1).

(b) In fig.(2), the first transistor Q1 has a current gain of 100 and the second transistor Q2 has a current gain of 50, what is the base current in the first transistor?

Q3: A 6.8V Zener diode specified at 5mA to have $V_z = 6.8V$ and $r_z = 20\Omega$ with $I_{zk} = 0.2$ mA, is operated in a regulator circuit shown in fig. (3). Using $R_s = 200 \Omega$ resistor and a 9 V supply. Estimate the knee voltage of the Zener. For no load, what is the lowest supply voltage for which the Zener remains in breakdown operation? For the nominal supply voltage, what is the maximum load current for which the Zener remains in breakdown operation? For half this load current, what is the lowest supply voltage for breakdown operation?

Q4: For the amplifier shown in Fig.(4) $R_1=10k\Omega$; $R_2=10k\Omega$; $R_C=4.3k\Omega$; $R_E=6.8k\Omega$; $R_L=1k\Omega$; $R_{sig}=500\Omega$; $V_{cc}=15V$; $\beta=100$; and $V_A= 100$. Calculate the dc bias current I_E . Replace the transistor with its hybrid- π model, and find the values of R_{in} , R_o , the voltage gain (v_o/v_{sig}) and the current gain (i_o/i_i).

Q5: For the circuit shown in Fig. (5), draw a complete small-signal equivalent circuit utilizing an appropriate T- model for the BJT (use $\alpha = 0.99$). Your circuit should show the values of all components, including the model parameters. Find R_{in} , R_o , the voltage gain (v_o/v_{sig}) and the current gain (i_o/i_i).

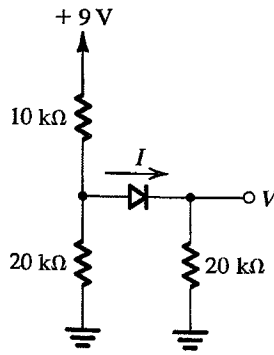
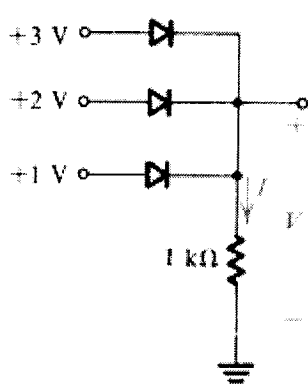


Fig.(1)

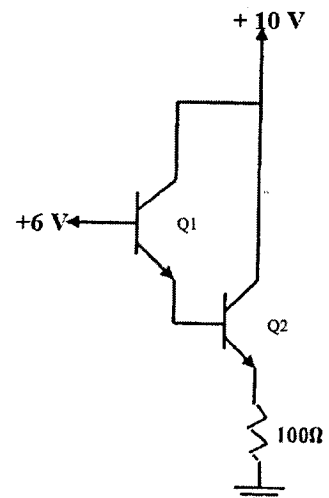


Fig.(2)

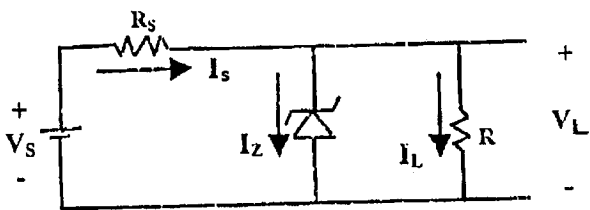


Fig.(3)

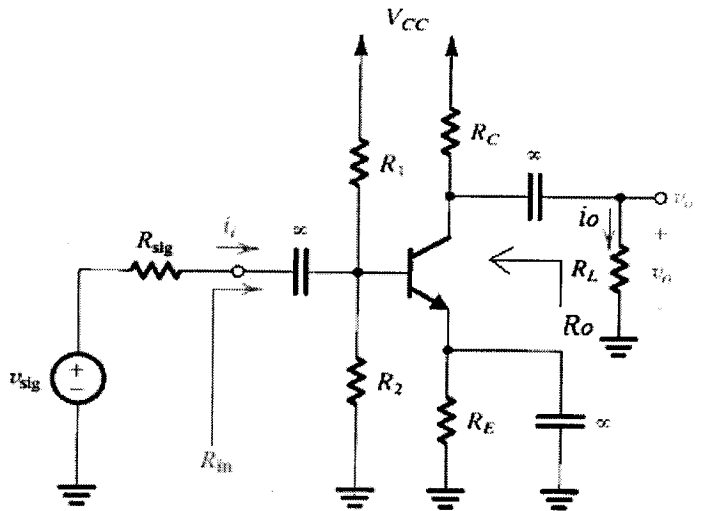


Fig.(4)

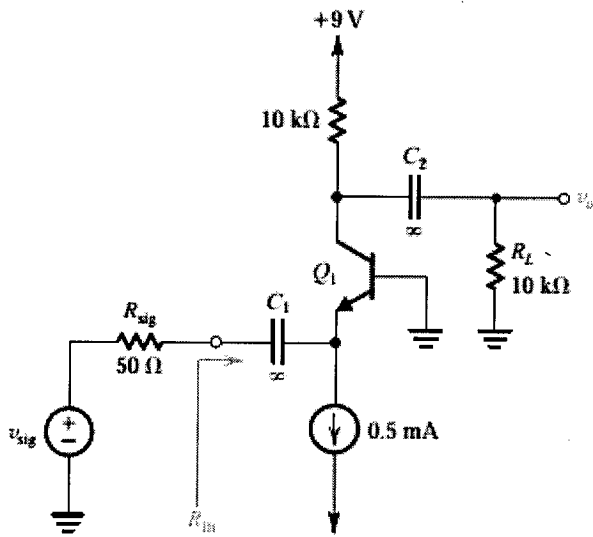


Fig.(5)

BEST WISHES

Hossam Labib



Answer the following questions:

Q1: Complete the following sentences:

- i. The two basic types of full wave rectifier are center tapped and bridge.
- ii. The output frequency of half wave rectifier is the same the input frequency.
- iii. Diode clampers add a DC level to an AC voltage.
- iv. The zener diode operates in reverse breakdown.
- v. The DC value of a full wave rectifier voltage with a peak value of 50 is
$$(V_{dc} = 2 * V_m / \pi = 100 / \pi = 31.831V).$$
- vi. Diode limiter cut-off voltage above or below specified levels.
- vii. α is the common base current gain of the transistors.
- viii. The bias methods for discrete BJT circuit are using single power supply (voltage divider bias), using two power supplies, and using a collector-to- base feedback resistor, OR using constant current source.
- ix. In common emitter amplifier, the input and output voltages are 180° out of phase.
- x. In common emitter amplifier the gain decreases with the emitter resistance.
- xi. In common collector amplifier, the input resistance is high, and the output resistance is low.


Q2 (a) Find the values of I and V in the circuits shown in Fig. (1).

For Fig. (a)

for D_1 on $V=3V$ D_2 and D_3 are off

$$\therefore V = 3V$$
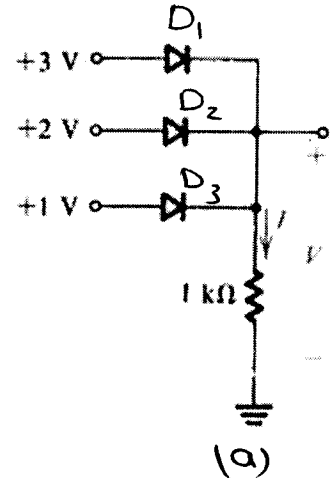
$$I = \frac{V}{R} = \frac{3}{1k\Omega} = 3mA$$





For Fig. (b)

$$V_p = \frac{9 \times 20k}{10k + 20k} = 6V$$

Then diode is on and replaced by s.c

$$V = \frac{9 \times (20k \parallel 20k)}{10 + (20k \parallel 20k)}$$

$$= \frac{9 \times 10k}{20k} = 4.5V$$

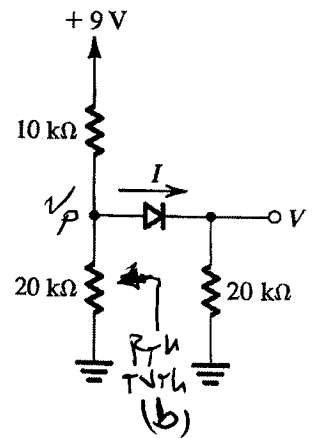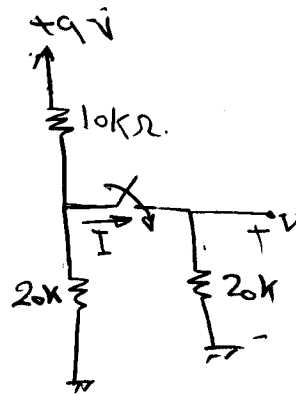

$$I = \frac{V}{20k} = \frac{4.5}{20k} = 0.225mA$$

Another solution


Using Thevenin the circuit becomes

$$V_{Th} = \frac{9 \times 20k}{10k + 20k} = 6V ; R_{Th} = 10k \parallel 20k = 6.67k$$

$\therefore V_p > V_n \Rightarrow$ diode on

$$\therefore V = \frac{6 \times 20k}{6.67k + 20k} = 4.5V$$

$$I = \frac{6}{6.67k + 20k} = 0.225mA$$

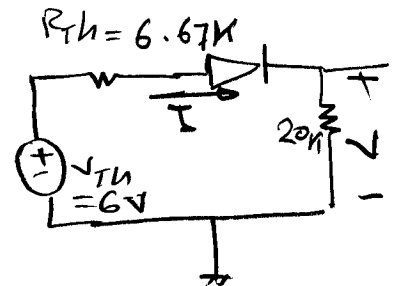

Q2(b) In Fig.(2), the first transistor Q1 has a current gain of 100 and the second transistor Q2 has a current gain of 50, what is the base current in the first transistor?

Solution

Let Q1 and Q2 in ACTIVE region

Loop (I) $\beta_1 = 100$ & $\beta_2 = 50$

$$-6 + V_{BE1} + V_{BE2} + I_{E2} * 100 = 0$$

$$I_{E2} = \frac{6 - 0.7 - 0.7}{100} = \frac{6 - 1.4}{100}$$

$$I_{E2} = 46 \text{ mA}$$

$$I_{B2} = \frac{I_{E2}}{1 + \beta_2} = \frac{46 \text{ mA}}{51} = 902 \text{ } \mu\text{A} = 0.902 \text{ mA}$$

$$\therefore I_{E1} = I_{B2} = 0.902 \text{ mA}$$

$$\therefore I_{B1} = \frac{I_{E1}}{1 + \beta_1} = \frac{0.902 \text{ mA}}{101} = 8.93 \text{ } \mu\text{A}$$

$$V_{B1} = 6 \text{ V}$$

$$V_{E1} = V_{B2} = 6 - V_{BE1} = 6 - 0.7 = 5.3 \text{ V}$$

$$V_{C1} = V_{C2} = 10 \text{ V}$$

$$V_{E2} = I_{E2} R_{E2} = 46 \text{ mA} * 100 = 4.6 \text{ V}$$

for Q1

$$V_{B1} > V_{E1} \Rightarrow \text{BE } \downarrow \text{ is Forward}$$

$$V_{C1} > V_{B1} \Rightarrow \text{BC } \downarrow \text{ is Reverse}$$


\therefore Q1 in ACTIVE Region

for Q2


$$V_{B2} > V_{E2} \Rightarrow \text{BE } \downarrow \text{ is Forward}$$

$$V_{C2} > V_{B2} \Rightarrow \text{BC } \downarrow \text{ is Reverse}$$

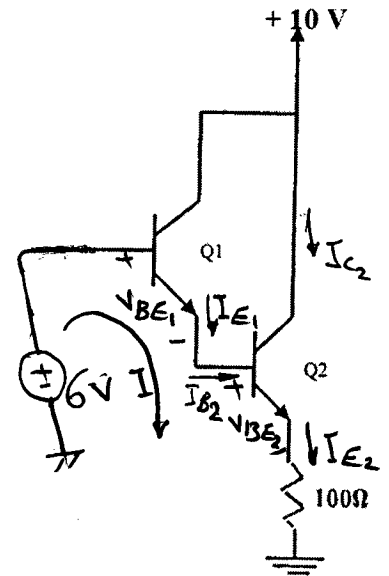\therefore Q2 in ACTIVE Region \Rightarrow \therefore Assumption is True
 $\therefore I_{B1} = 8.93 \text{ } \mu\text{A}$




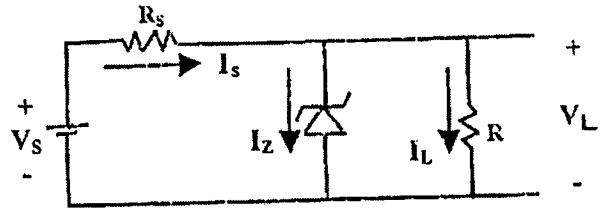Q3: A 6.8V Zener diode specified at 5mA to have $V_Z = 6.8V$ and $r_Z = 20\Omega$ with $I_{ZK} = 0.2mA$, is operated in a regulator circuit shown in Fig. (3). Using $R_s = 200\Omega$ resistor and a 9V supply. Estimate the knee voltage of the Zener. For no load, what is the lowest supply voltage for which the Zener remains in breakdown operation? For the nominal supply voltage, what is the maximum load current for which the Zener remains in breakdown operation? For half this load current, what is the lowest supply voltage for breakdown operation?



Solution

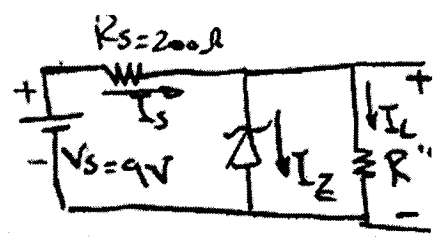$V_Z = 6.8V$; $I_Z = 5mA$; $I_{ZK} = 0.2mA$
 $r_Z = 20\Omega$



$\therefore V_Z = V_{Z0} + I_Z r_Z$; $V_{Z0} = V_{ZK}$

$\therefore V_{Z0} = V_Z - I_Z r_Z = 6.8 - 5m \times 20 = 6.7V$

\therefore Knee Voltage = $6.7V$ $\longrightarrow 2$

- For no Load find lowest V_s to operate in breakdown.

For edge of breakdown $\Rightarrow I_Z = I_{ZK} = 0.2mA$; $V_Z = V_{ZK} =$

$V_{Z0} = 6.7V$ $\longrightarrow 1$

For $R = \infty \Rightarrow I_s = I_Z \Rightarrow I_s = I_{ZK}$

$\therefore \frac{V_s - V_{Z0}}{R_s} = I_{ZK} \Rightarrow V_s = V_{Z0} + I_{ZK} R_s \longrightarrow 1$

$V_s = 6.7 + 0.2 \times 10^{-3} \times 200 = 6.74V \approx 6.7V \longrightarrow 1$

Then for no Load, breakdown is sustained to about supply

Vol Tags = $6.7V$

Q3: (Cont.)

- For nominal supply voltage i.e. $V_s = 9V$ find $I_L|_{\max}$ in which Zener remain in breakdown

$$\therefore I_s = I_Z + I_L \Rightarrow I_L|_{\max} = I_s \uparrow - I_Z \downarrow = I_{ZK} \quad ; \quad V_Z = V_{Z0}, I_Z = I_{ZK}$$

$$\therefore I_L|_{\max} = \frac{V_s - V_{Z0}}{R_s} - I_{ZK} \longrightarrow 1$$

$$= \frac{9 - 6.7}{200} - 0.2 \text{ m} = 11.5 \text{ m} - 0.2 \text{ m} = 11.3 \text{ mA} \longrightarrow 2$$

- For $\frac{I_L|_{\max}}{2} = \frac{11.3 \text{ m}}{2} = 5.65 \text{ mA}$ find lowest V_s for breakdown

$$I_L = 5.65 \quad ; \quad I_Z = I_{ZK} = 0.2 \text{ mA} \quad ; \quad V_Z = V_{Z0} = 6.7 \text{ V}$$

$$\therefore I_s = I_{ZK} + I_L = 0.2 \text{ m} + 5.65 \text{ m} = 5.85 \text{ mA} \longrightarrow 1$$

$$\therefore I_s = \frac{V_s - V_{Z0}}{R_s} \Rightarrow V_s = V_{Z0} + I_s R_s \longrightarrow 1$$


$$\therefore V_s|_{\min} = V_{Z0} + I_s R_s$$

$$= 6.7 + 5.85 \times 10^{-3} \times 200$$

$$= 7.87 \text{ V} \longrightarrow 2$$

Thus the lowest supply for regulation with half-max. Load current = 7.87 V

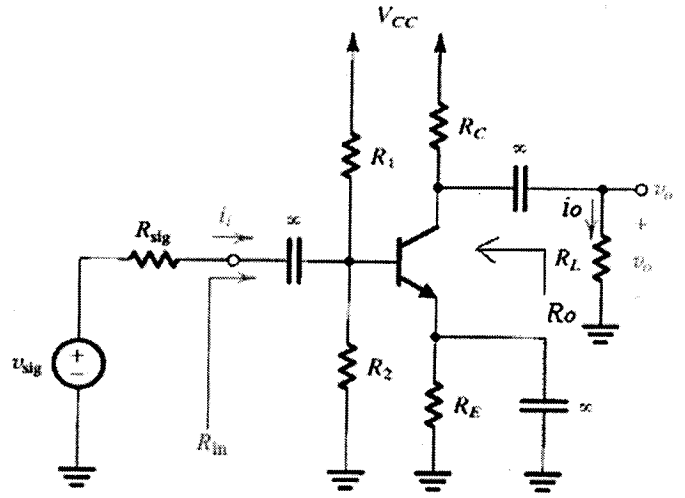Q4: For the amplifier shown in Fig.(4)
 $R_1=10k\Omega$; $R_2=10k\Omega$; $R_C=4.3k\Omega$; $R_E=6.8k\Omega$;
 $R_L=1k\Omega$; $R_{sig}=500\Omega$; $V_{cc}=15V$; $\beta=100$; and
 $V_A=100$. Calculate the dc bias current I_E .
 Replace the transistor with its hybrid- π model,
 and find the values of R_{in} , R_o , the voltage gain
 (v_o/v_{sig}) and the current gain (i_o/i_i).



Solution

DC Analysis

- ALL capacitors are o.c
- reduce AC sources

$$R_{TH} = R_1 \parallel R_2 = 10k \parallel 10k = 5k\Omega$$

$$V_{TH} = \frac{V_{cc} R_2}{R_1 + R_2} = \frac{15 \times 10k}{20k} = 7.5V$$

Loop (KVL)

$$-V_{TH} + I_B R_{TH} + V_{BE} + I_E R_E = 0$$

$$\therefore I_E = (1 + \beta) I_B$$

$$\therefore -V_{TH} + \frac{I_E}{1 + \beta} R_{TH} + V_{BE} + I_E R_E = 0$$

$$I_E \left(\frac{R_{TH}}{1 + \beta} + R_E \right) = V_{TH} - V_{BE}$$

$$I_E = \frac{V_{TH} - V_{BE}}{\frac{R_{TH}}{1 + \beta} + R_E} = \frac{7.5 - 0.7}{\frac{5k}{101} + 6.8k} = 0.993 \text{ mA}$$

$$I_C = \alpha I_E = \frac{\beta}{1 + \beta} I_E = \frac{100}{101} \times 0.993 \text{ mA} = 0.983 \text{ mA}$$



AC Analysis

- ALL capacitors are s.c
- reduce DC sources i.e v.s = s.c

$$g_m = \frac{I_C}{V_T} = \frac{0.983 \text{ mA}}{25 \text{ mV}} = 39.32 \text{ mA/V}$$


$$r_{\pi} = \frac{\beta}{g_m} = \frac{100}{39.32 \text{ mA/V}} = 2.54 \text{ k}\Omega$$
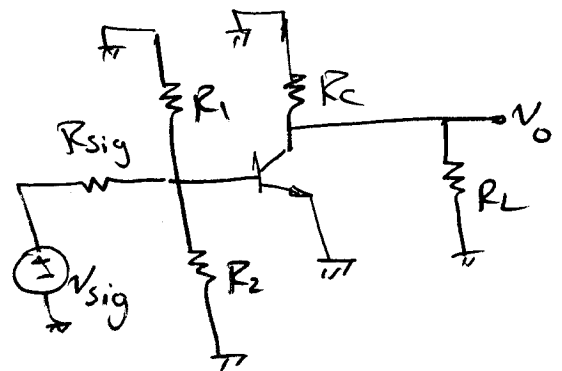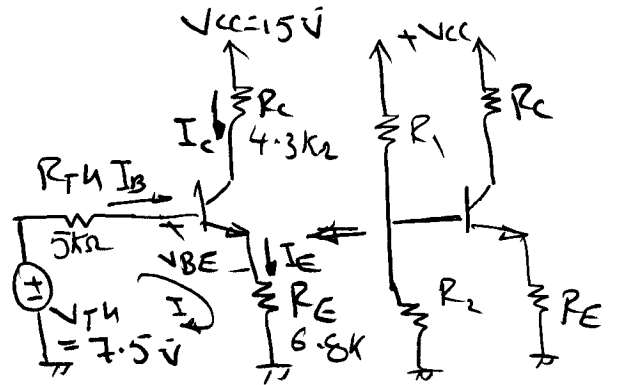
$$r_o = \frac{V_A}{I_C} = \frac{100}{0.983 \text{ mA}} = 101.73 \text{ k}\Omega$$



Q4: (Cont.)

Using π -model

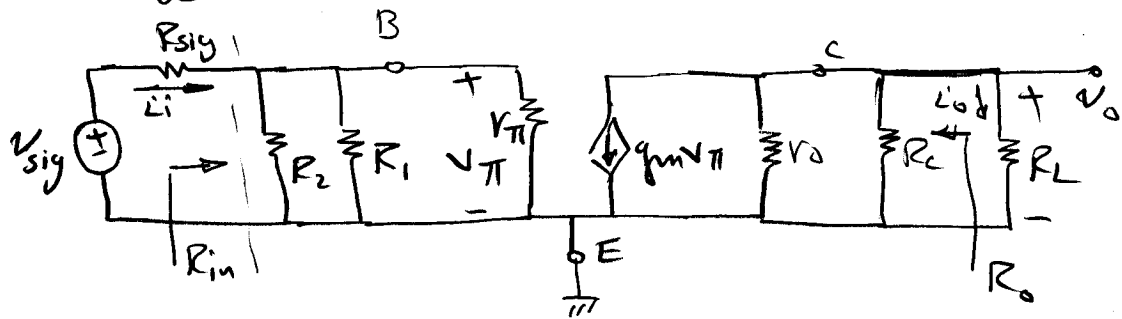

$$R_{in} = R_1 \parallel R_2 \parallel V_{\pi} = 10k \parallel 10k \parallel 2.54k\Omega$$

$$= 5k \parallel 2.54k\Omega = 1.684k\Omega$$

$$R_o |_{V_{sig}=0} = R_c \parallel r_o$$

$$= 6.8k \parallel 101.73k = 6.374k\Omega$$

To find $A_v = \frac{V_o}{V_{sig}}$

$$V_o = -g_m V_{\pi} (r_o \parallel R_c \parallel R_L)$$

$$V_{\pi} = V_{sig} \frac{R_{in}}{R_{sig} + R_{in}}$$

$$V_o = -g_m V_{sig} \frac{R_{in}}{R_{sig} + R_{in}} (r_o \parallel R_c \parallel R_L)$$

$$A_v = \frac{V_o}{V_{sig}} = -g_m \frac{R_{in}}{R_{sig} + R_{in}} (r_o \parallel R_c \parallel R_L)$$

$$= -39.32 \times 10^{-3} \frac{1.684k}{0.5k + 1.684k} (101.73k \parallel 6.8k \parallel 1k)$$

$$= -39.32 \times 10^{-3} * 771.06 * 10^3 * 864.39 = -26.21 \text{ V/V}$$

To find $A_i = \frac{I_o}{I_i}$

$$I_o = -g_m V_{\pi} \frac{R_o}{R_o + R_L}$$

$$V_{\pi} = I_i R_{in}$$

$$I_o = -g_m I_i R_{in} \frac{R_o}{R_o + R_L}$$

$$A_i = \frac{I_o}{I_i} = -g_m \frac{R_{in} R_o}{R_o + R_L}$$


$$= -39.32 \times 10^{-3} \frac{1.684k * 6.374k}{6.374k + 1k}$$

$$= -39.32 \times 10^{-3} * 1455.63 =$$

$$A_i = -57.24 \text{ A/A}$$

(7)

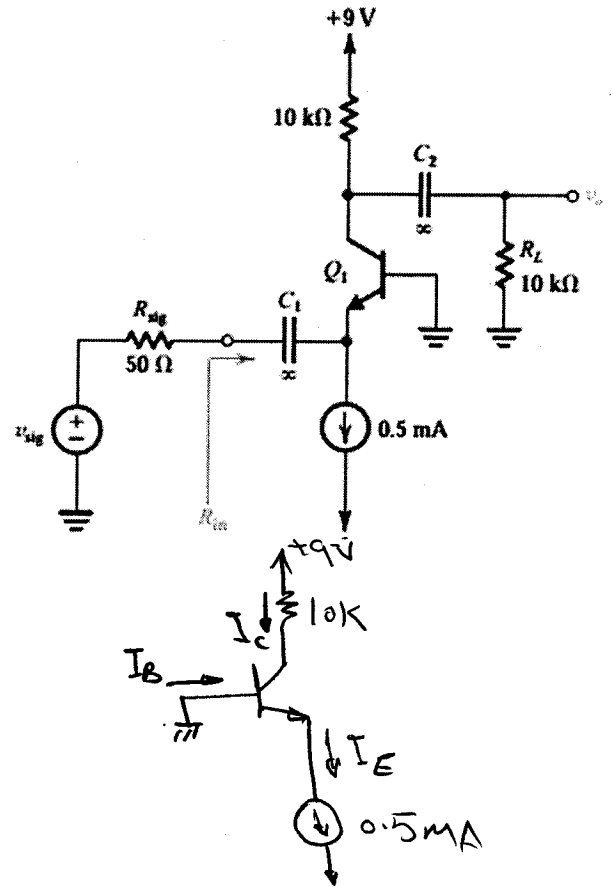Q5: For the circuit shown in Fig. (5), draw a complete small-signal equivalent circuit utilizing an appropriate T-model for the BJT (use $\alpha = 0.99$). Your circuit should show the values of all components, including the model parameters. Find R_{in} , R_o , the voltage gain (v_o/v_{sig}) and the current gain (i_o/i_i).



Solution

DC Analysis

- All capacitors are o.c
- reduce AC sources


$$I_E = 0.5 \text{ mA}$$

$$r_e = \frac{V_T}{I_E} = \frac{25 \text{ mV}}{0.5 \text{ mA}} = 50 \Omega$$

AC Analysis

- All capacitors are s.c ; reduce DC sources i.e. V.S = s.c & C.S = o.c

Using T-model

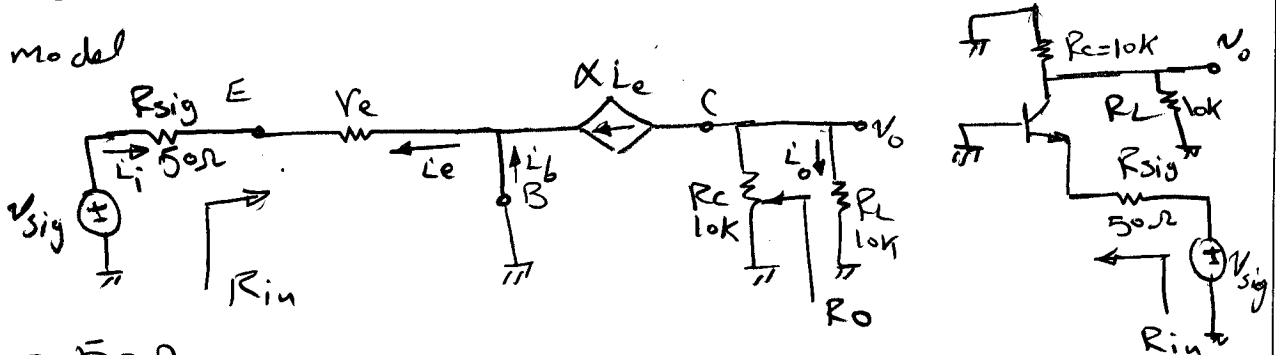

$$R_{in} = r_e = 50 \Omega$$

$$R_o = R_c = 10 \text{ k}\Omega$$

$$v_{sig} = 0$$

$$v_o = -\alpha i_e (R_c \parallel R_L)$$

$$i_e = -i_i = \frac{-v_{sig}}{R_{sig} + r_e}$$

$$\therefore v_o = \frac{+\alpha v_{sig} (R_c \parallel R_L)}{R_{sig} + r_e}$$

$$\therefore A_v = \frac{v_o}{v_{sig}} = \frac{\alpha (R_c \parallel R_L)}{R_{sig} + r_e}$$

$$A_v = \frac{0.99 (10 \text{ k}\Omega \parallel 10 \text{ k}\Omega)}{50 + 50} = \frac{0.99 * 5 \text{ k}}{100} = 49.5 \text{ V/V}$$

Q5: (Cont.)

To find $A_i = \frac{I_o}{I_i}$

$$I_o = -\alpha I_e \frac{R_c}{R_c + R_L}$$

$$I_i = -I_e$$

$$\therefore A_i = \frac{I_o}{I_i} = \frac{\alpha R_c}{R_c + R_L}$$

$$= \frac{0.99 * 10k}{10k + 10k} = \frac{0.99}{2} = 0.495 \text{ A/A}$$
