



Answer the following questions:

Q1: (a) Assuming that the diodes in the circuits of Fig.(1) are ideal, find the values of the labeled voltage, V , and current, I .

(b) For the circuit shown in Fig.(2) in which $|V_{BE}| = 0.7V$, find the voltages at nodes A, B, and C for $\beta = \infty$.

Q2: (a) Describe the output voltage of the circuit shown in Fig.(3). Assuming the diodes to be actual and $V_1 = 10 \sin \omega t$. Sketch one cycle of the output voltage.


(b) Fig.(4) shows a simpler way to draw a transistor circuit. What are collector-emitter voltage and the transistor power dissipation?

Q3: The zener diode of Fig.(5) has a breakdown voltage of 12V. Determine:

- If the zener diode is disconnected, what is the load voltage?
- Assume the supply voltage decreases from 20 to 0 V. At some point along the way, the zener diode will stop regulating. Find the supply voltage where regulation is lost.
- Assuming a tolerance of ± 10 percent in both resistors, what is zener current?

Q4: For the amplifier shown in Fig. (6), the signal source is directly coupled to the transistor base. If the dc component of v_{sig} is zero, and $R_{sig}=2.5 \text{ k}\Omega$. For $R_E=14.1 \text{ k}\Omega$, $R_C=10 \text{ k}\Omega$, $R_L=5\text{k}\Omega$ find the dc emitter current. Assume $\beta= 100$, and $V_A=100\text{V}$. Find R_{in} , the voltage gain v_o/v_{sig} , the current gain i_o/i_i , and the output resistance R_{out} .

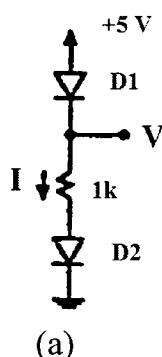Q5: For the universal BJT amplifier configuration as shown in fig. (7), let $R_B = 100 \text{ K}\Omega$, $R_C = R_E = 10 \text{ K}\Omega$, $V_{CC} = V_{EE} = 10\text{V}$, $\beta = 100$, and $I_C = 0.838 \text{ mA}$. If the amplifier is connected in the common base configuration draw the complete circuit of the amplifier and then find using T-model the values of R_i , R_o , A_v , and A_i for $R_S = R_L = 10 \text{ K}\Omega$.



(a)

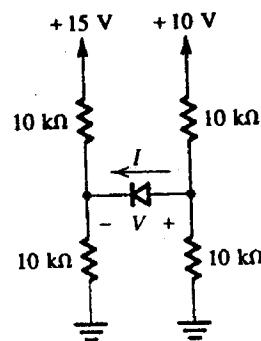


Fig.(1)

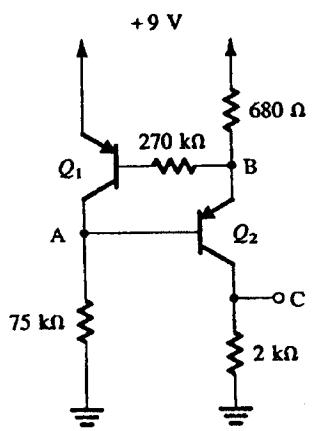


Fig.(2)

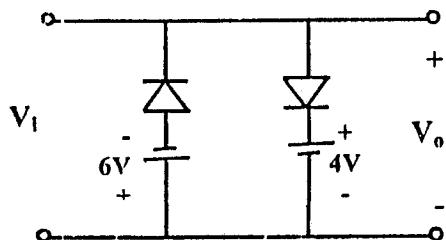


Fig.(3)

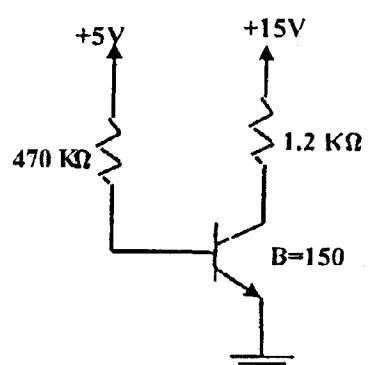


Fig.(4)

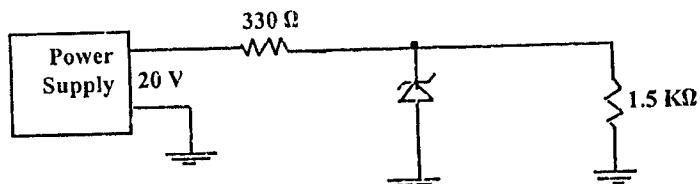


Fig.(5)

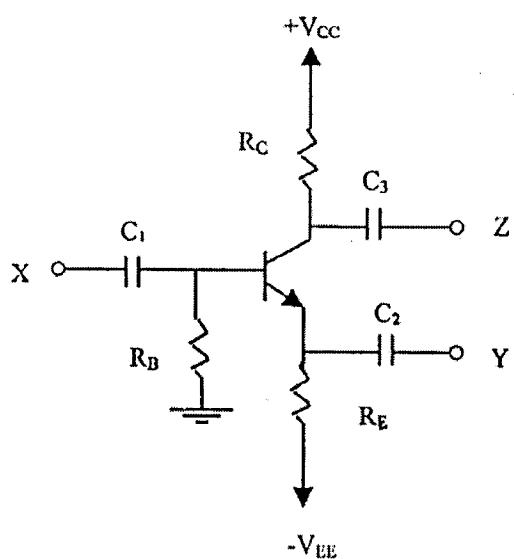


Fig.(7)

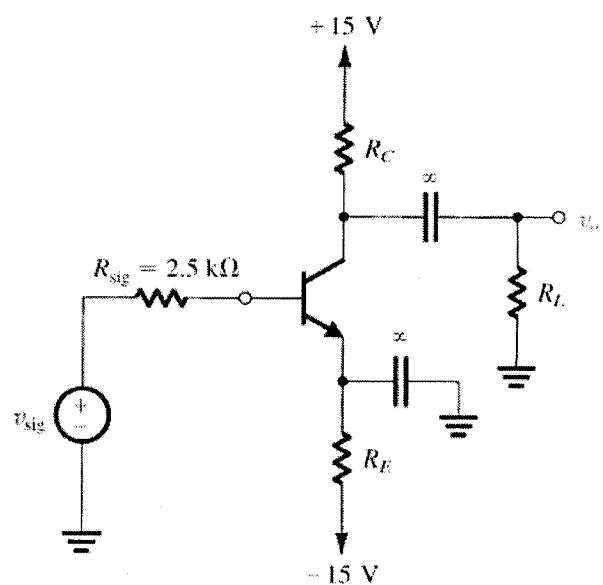


Fig.(6)

BEST WISHES
Hossam Labib

Model Answer

Q1: (15 points)

(a)

Assuming that the diode in the circuits shown are ideal find the values of labeled voltage, V , and current, I .

Solution

$$(a) \text{ For } D_1 \quad ; V_{P_1} = 5V$$


$$\because V_{P_1} > V_{N_1} \Rightarrow D_1 \text{ on} \rightarrow 1$$

$$\therefore V = 5V \rightarrow 2$$

$$\because V_{N_2} = 0V \Rightarrow V_{P_2} > V_{N_2}$$

$$\therefore D_2 \text{ on} \rightarrow 1$$
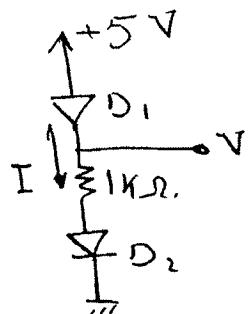
$$I = \frac{5V}{1k\Omega} = 5mA \rightarrow 1$$



$$(b) \quad V_1 = \frac{10 * 10k}{(10+10)k} = 5V \rightarrow 1$$

$$V_2 = \frac{15 * 10k}{(10+10)k} = 7.5V \rightarrow 1$$


$$V_P = V_1 = 5V$$

$$V_N = V_2 = 7.5V$$

$$\because V_P < V_N \Rightarrow \text{Diode off} \rightarrow 1$$

$$V = V_1 - V_2 = 5 - 7.5 = -2.5V \rightarrow 1$$
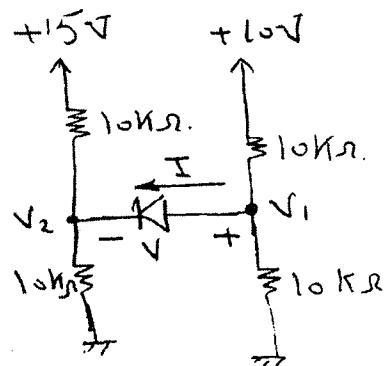
$$\therefore \text{Diode off} \Rightarrow I = 0 \rightarrow 1$$



Q1: (b)

For the circuit shown $|V_{BE}| = 0.7V$
 find the voltage at nodes A, B and C
 for $\beta = \infty$.

Solution

Let Q_1 and Q_2 in Active Region

for $\beta = \infty \Rightarrow$ Base currents ≈ 0

$$\text{i.e. } I_{B1} = I_{B2} = 0 \rightarrow \textcircled{1}$$

AT Node A

$$I_{C1} = I_1 ; I_{E1} = I_{C1} = I_1$$

at node B

$$I_{E2} = I_2 ; I_{E2} = I_{C2} = I_2$$

Loop ①

$$V_{EB1} + 270K I_{B1} - 680 I_2 = 0$$

$$I_2 = \frac{V_{EB1}}{680} = \frac{0.7}{680} = 1.029 \text{ mA} = I_{E2} = I_{C2} \rightarrow \textcircled{1}$$

$$\therefore V_B = 9 - I_2 * 680 = 9 - 0.7 = 8.3V \rightarrow \textcircled{2}$$

$$\underline{\text{OR}} (V_B = 9 - V_{EB1} = 8.3V)$$

$$V_C = I_{C2} * 2K = 1.029 * 2 = 2.058V \rightarrow \textcircled{2}$$

$$\therefore V_B = V_{EB2} + V_A \Rightarrow V_A = V_B - V_{EB2}$$

$$V_A = 8.3 - 0.7 = 7.6V \rightarrow \textcircled{2}$$


$$I_1 = \frac{V_A}{75\text{N}} = \frac{7.6}{75\text{N}} = 101.33 \text{ mA} = I_{C1} = I_{E1}$$

for Q_1

$$V_{E1} = 9V \quad \& \quad V_{B1} = V_B = 8.3V \quad \& \quad V_{C1} = V_A = 7.6V$$

$$V_{B1} < V_{E1} \Rightarrow EBJ \text{ Forward}$$
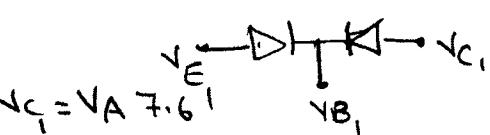
$$V_{B1} > V_{C1} \Rightarrow CBJ \text{ Reverse}$$



Then Q_1 in Active Region

for Q_2

$$V_{E2} = V_B = 8.3V \quad \& \quad V_{B2} = V_A = 7.6V \quad \& \quad V_{C2} = V_C = 2.058V$$

$$V_{B2} < V_{E2} \Rightarrow EBJ \text{ Forward} \quad \& \quad \text{Then } Q_2 \text{ in Active Region}$$

$$V_{B2} > V_{C2} \Rightarrow CBJ \text{ Reverse}$$

\therefore The assumption is TRUE

(2)

Q2: (15 Points)



Q2 (a)

Describe the o/p voltage of the circuit shown.

Assuming the diode to be actual and $V_I = 10 \sin \omega t$.

Sketch one cycle of the o/p.

Solution

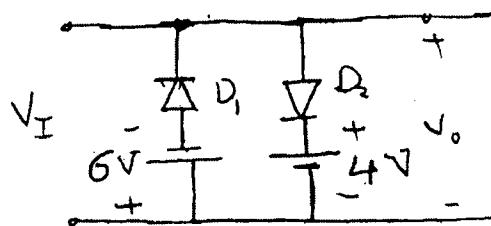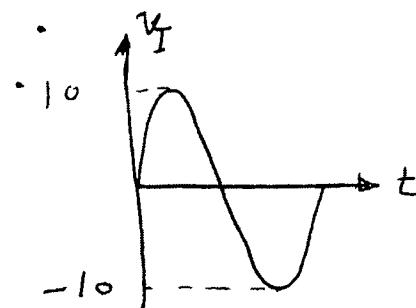

for +ve half cycle

- for $V_i < 4.7 \text{ V}$

D_1 and D_2 are off



$$\therefore V_o = V_i$$

- for $V_i > 4.7 \text{ V}$

(2)

D_1 off & D_2 on

$$\therefore V_o = 4.7 \text{ V}$$

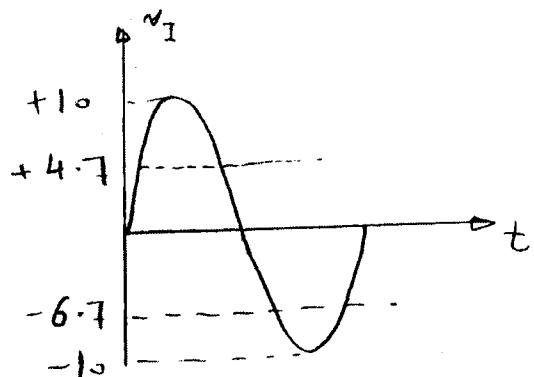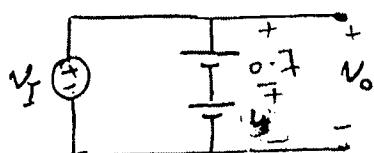

for -ve half cycle

- for $V_i > -6.7 \text{ V}$

D_1 off and D_2 off



$$\therefore V_o = V_i$$

- for $V_i < -6.7 \text{ V}$

(2)

D_1 on & D_2 off

$$\therefore V_o = -6.7 \text{ V}$$

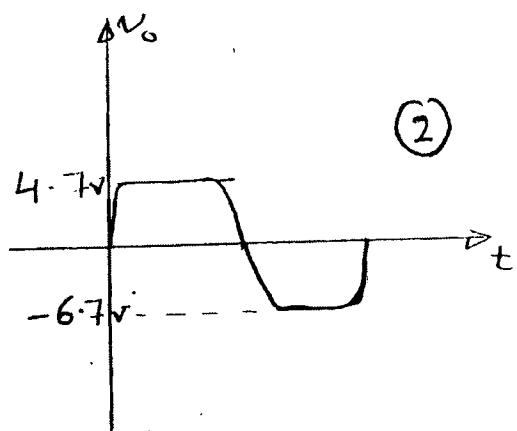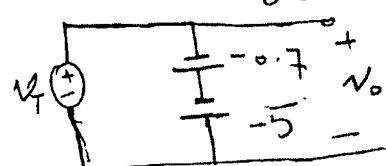

(3)

Q2(b)

Fig.(2) shows a simpler way to draw a Transistor circuit. What are collector emitter voltage and the Transistor power dissipation?

Solution

Let Transistor in ACTIVE Region

Loop (I)

$$5 = 470K I_B + V_{BE}$$

$$I_B = \frac{5 - 0.7}{470K} = 9.15 \text{ mA}$$

$$\therefore I_C = \beta I_B = 150 * 9.15 \text{ mA} = 1.3725 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C R_C = 15 - 1.3725 * 1.2 = 13.353 \text{ V}$$

$$V_E = 0 \text{ V} \quad , \quad \therefore V_{BE} = V_B - V_E$$

$$\therefore V_B = V_{BE} = 0.7 \text{ V} ; V_C = V_{CE} = 13.353 \text{ V}$$

$\because V_B > V_E \Rightarrow BE \downarrow$ Forward bias

$\therefore V_B < V_C \Rightarrow BC \downarrow$ Reverse bias


\therefore Transistor in ACTIVE Region

$$\therefore V_{CE} = 13.353 \text{ V} ; I_C = 1.3725 \text{ mA}$$

$$P_{diss} = I_{CQ} V_{CEQ}$$

$$= 1.3725 * 10^{-3} * 13.353 = 0.0183 \text{ W}$$

$$= 18.3 \text{ mW}$$

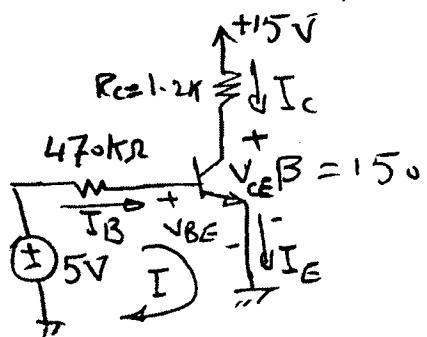


Q3: (15 points)

Q3: The Zener diode shown has breakdown voltage of 12 V. Determine:

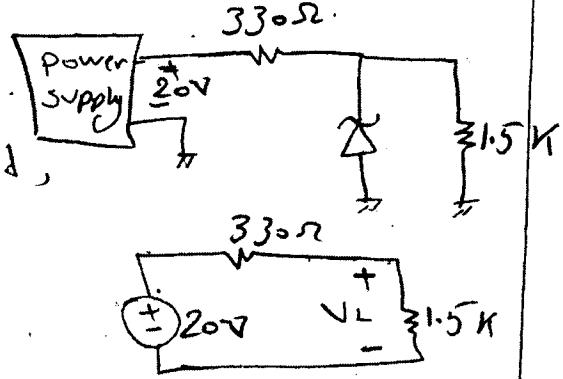- (i) If the Zener diode is disconnected, what is the load voltage.

Solution

$$V_L = \frac{20 \times 1.5K}{1.5K + 330} = 16.4 \text{ V}$$




(ii) Assume the supply voltage decreases from 20 to 0 V. At some point along the way, the Zener diode will stop regulating. Find the supply voltage where regulation is lost.

Solution

When Zener is operate

$$\therefore I_L = \frac{V_Z}{R_L} = \frac{12}{1.5K} = 8 \text{ mA}$$

$$I = I_Z + I_L$$

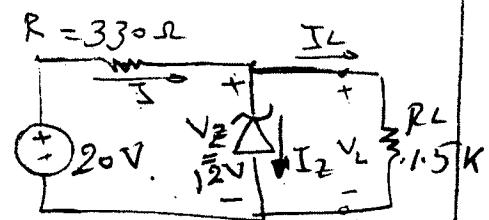

If regulation is lost $\Rightarrow I_Z = 0$

$$\therefore I = I_L = 8 \text{ mA}$$

$$\therefore V_{\text{Supply}} = I(330 + 150) = 8 \text{ mA} \times 483 \Omega = 14.64 \text{ V}$$

- Regulation is lost when supply voltage = 14.64 V

- (iii) Assuming a tolerance of ± 10 percent in both resistors, what is the max. Zener current?

Solution

$$I_Z^{\uparrow} = I^{\uparrow} - I_L^{\downarrow} \quad ; \quad I^{\uparrow} \text{ at } R \uparrow \quad ; \quad I_L^{\downarrow} \text{ at } R_L \uparrow$$


$$\therefore R_{\min} = R - 10\% R = R(1 - 0.1) = 330 \times 0.9 = 297 \Omega$$

$$R_L^{\max} = R_L + 10\% R_L = R_L(1 + 0.1) = 1.5 \times 1.1 = 165 \Omega$$

$$I_Z^{\max} = \left(\frac{20 - 12}{297} \right) - \left(\frac{12}{165} \right) = 19.7 \text{ mA}$$

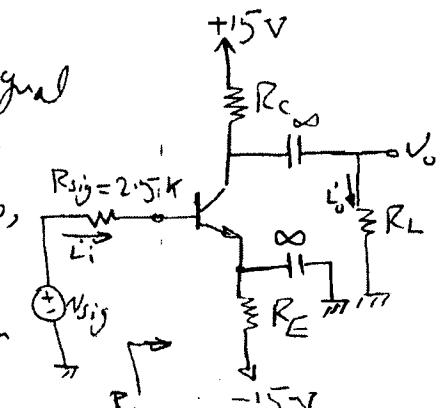Q4: (15 points)

For the amplifier shown in Fig. (1), the signal source is directly coupled to the transistor base. If the dc component of v_{sig} is zero, and $R_{sig} = 2.5 \text{ k}\Omega$. For $R_E = 14.1 \text{ k}\Omega$, $R_C = 10 \text{ k}\Omega$, $R_L = 5 \text{ k}\Omega$ find the dc emitter current. Assume $\beta = 100$, and $V_A = 100 \text{ V}$.



Find R_{in} , the voltage gain v_o/v_{sig} , the current gain α_{oi}/α_{ii} , and the output resistance R_{out} .

Solution

DC Analysis

All capacitors are o.c.

Reduce AC sources i.e. $v_{sig} = 5 \text{ mV}$

Loop ①

$$I_B R_{sig} + V_{BE} + I_E R_E - 15 = 0$$

$$\therefore I_E = (1 + \beta) I_B$$

$$\frac{I_E}{(1 + \beta)} R_{sig} + V_{BE} + I_E R_E - 15 = 0$$

$$I_E \left(\frac{R_{sig}}{1 + \beta} + R_E \right) = 15 - V_{BE}$$

$$I_E = \frac{15 - 0.7}{\frac{R_{sig}}{1 + \beta} + R_E} = \frac{15 - 0.7}{2.5k + 14.1k} = 1.012 \text{ mA}$$

$$I_C = \alpha I_E = \frac{100}{101} \times 1.012 \text{ mA} \approx 1 \text{ mA}$$

$$g_m = \frac{I_C}{V_T} = \frac{1 \text{ mA}}{25 \text{ mV}} = 0.04 \text{ A/V}$$



$$r_{\pi} = \frac{\beta}{g_m} = \frac{100}{0.04} = 2.5 \text{ k}\Omega$$

$$R_o = \frac{V_A}{I_C} = \frac{100}{1 \text{ mA}} = 100 \text{ k}\Omega$$

AC Analysis


- ALL cap. = s.c.

- reduce DC sources

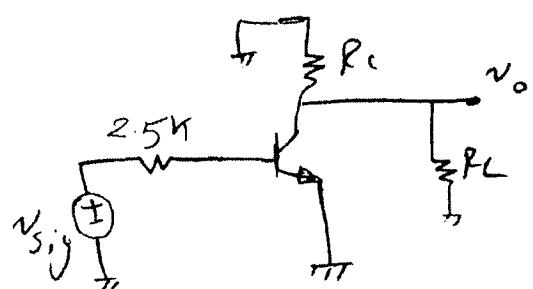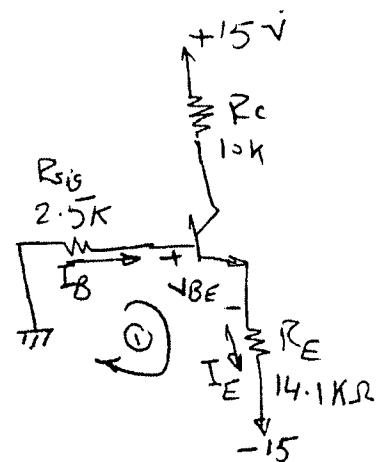

(6)

Q₄: (Cont.)

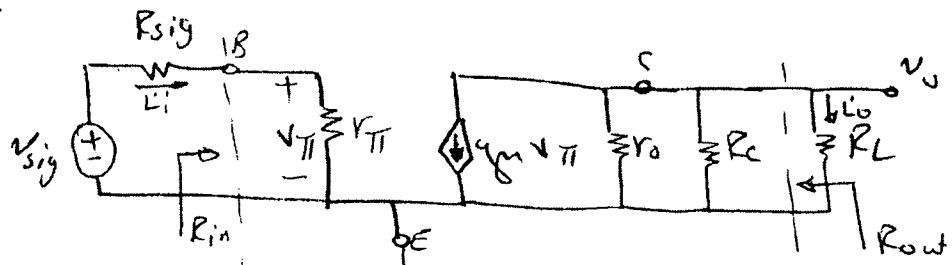

$$R_{in} = R_{pi} = 2.5 \text{ k}\Omega \rightarrow (1)$$

$$R_{out} = R_o \parallel R_c = (100 \text{ k}\Omega \parallel 10 \text{ k}\Omega) = 9.1 \text{ k}\Omega \rightarrow (2)$$

$$\text{To find } A_v = \frac{v_o}{v_{sig}}$$

$$v_o = -g_m R_{pi} (R_o \parallel R_c \parallel R_L) \rightarrow (3)$$

$$v_{pi} = v_{sig} \frac{R_{pi}}{R_{sig} + R_{pi}} \rightarrow (4)$$

$$v_o = -g_m v_{sig} \frac{R_{pi}}{R_{sig} + R_{pi}} (R_o \parallel R_c \parallel R_L)$$

$$\therefore A_v = \frac{v_o}{v_{sig}} = -g_m \frac{R_{pi}}{R_{sig} + R_{pi}} (R_o \parallel R_c \parallel R_L)$$

$$= -0.04 \frac{2.5k}{2.5k + 2.5k} (100k \parallel 10k \parallel 5k)$$

$$= -0.04 * 0.5 + 3.226 \text{ V/V} = -64.5 \text{ V/V} \rightarrow (5)$$

$$\text{To find } A_L = \frac{L_o}{L_i}$$

$$L_o = -g_m R_{pi} \frac{R_{out}}{R_{out} + R_L} \rightarrow (6)$$

$$\therefore v_{pi} = L_i R_{pi} \rightarrow (7)$$

$$L_o = -g_m L_i R_{pi} \frac{R_{out}}{R_{out} + R_L}$$

$$A_L = \frac{L_o}{L_i} = -g_m R_{pi} \frac{R_{out}}{R_{out} + R_L}$$

$$= -g_m \frac{B}{g_m} \frac{R_{out}}{R_{out} + R_L} = -B \frac{R_{out}}{R_{out} + R_L}$$


$$A_L = -100 \frac{0.1k}{0.1k + 5k}$$

$$A_L = -64.5 \text{ A/A} \rightarrow (8)$$

(7) -

Q5: (15 points)

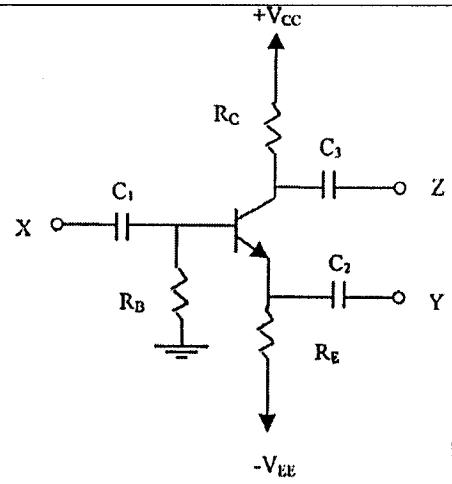Q5: For the universal BJT amplifier configuration as shown in fig. (7), let $R_B = 100 \text{ k}\Omega$, $R_C = R_E = 10 \text{ k}\Omega$, $V_{CC} = V_{EE} = 10\text{V}$, $\beta = 100$, and $I_C = 0.838 \text{ mA}$. If the amplifier is connected in the common base configuration draw the complete circuit of the amplifier and then find using T-model the values of R_i , R_o , A_v , and A_i for $R_S = R_L = 10 \text{ k}\Omega$.




Solution

For $I_C = 0.838 \text{ mA}$ then

$$\gamma_m = \frac{\gamma_c}{\sqrt{T}} = \frac{0.838 \text{ mA}}{25 \text{ m}} = 33.52 \text{ mA/V}$$

$$r_e = \frac{\alpha}{\gamma_m} \approx \frac{1}{\gamma_m} = \frac{1}{33.52 \text{ m}} = 29.8 \text{ m}\Omega$$

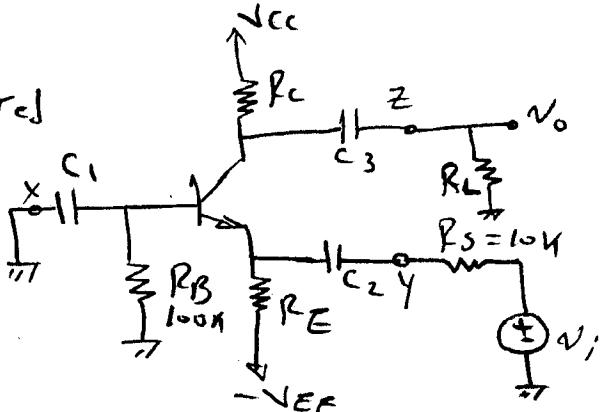- If The amplifier is connected in C-B configuration
 $R_S = R_L = 10 \text{ k}\Omega$
 the complete circuit is as shown →





Q4: cont

Ac Analysis

- ALL capacitor are s-c
- reduce DC sources

Using T-model

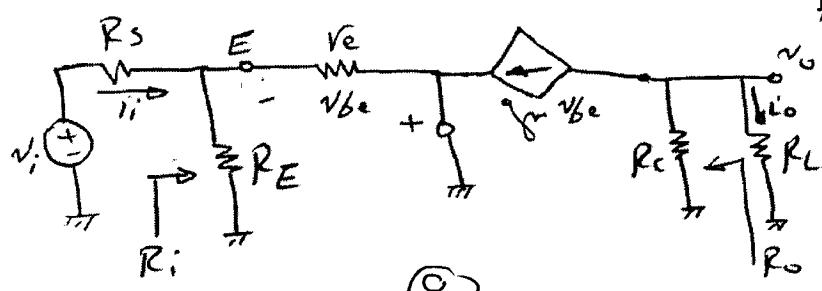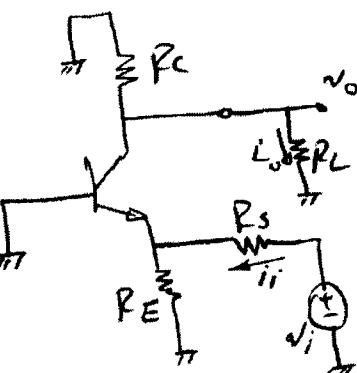

(8)

$$R_i = R_E \parallel R_e = 29.8 \parallel 10K \approx 29.7 \approx R_e$$

$$R_o \Big|_{V_i=0} = R_C = 10 K\Omega$$

$$\text{To find } A_v = \frac{V_o}{V_i}$$

$$V_o = -g_m V_{be} (R_C \parallel R_L)$$

$$V_{be} = -V_i \left(\frac{R_E \parallel R_e}{R_E \parallel R_e + R_s} \right) = -V_i \frac{R_i}{R_i + R_s}$$

$$V_o = +g_m V_i \frac{R_i}{R_i + R_s} (R_C \parallel R_L)$$

$$A_v = \frac{V_o}{V_i} = g_m \frac{R_i}{R_i + R_s} (R_C \parallel R_L)$$

$$= 33.52 \times 10^3 \frac{29.7}{29.7 + 10K} (10K \parallel 10K) \approx 0.5 \text{ V/V}$$

$$\text{To find } A_L = \frac{L_o}{L_i}$$

$$L_o = -g_m V_{be} \left(\frac{R_C}{R_C + R_L} \right)$$

$$V_{be} = -L_i R_i$$

$$L_o = +g_m L_i R_i \left(\frac{R_C}{R_C + R_L} \right)$$

$$A_L = \frac{L_o}{L_i} = g_m R_i \frac{R_C}{R_C + R_i}$$

$$= 33.52 \times 10^3 \times 29.7 \frac{10K}{10K + 10K} -$$

$$= 0.5 \cdot A / A$$

(9)