



Model Answer

Question (1): [12 Marks]

- Find the resistance seen by the ideal voltage source in the circuit in Fig.1.
- If v_{ab} equals 400 V, how much power is dissipated in the 31 Ω resistor?

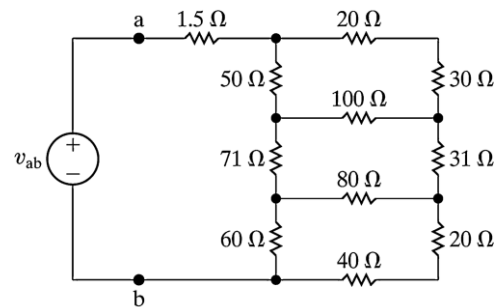


Fig.1

[a] Convert the upper delta to a wye.

$$R_1 = \frac{(50)(50)}{200} = 12.5 \Omega$$

$$R_2 = \frac{(50)(100)}{200} = 25 \Omega$$

$$R_3 = \frac{(100)(50)}{200} = 25 \Omega$$

Convert the lower delta to a wye.

$$R_4 = \frac{(60)(80)}{200} = 24 \Omega$$

$$R_5 = \frac{(60)(60)}{200} = 18 \Omega$$

$$R_6 = \frac{(80)(60)}{200} = 24 \Omega$$

Now redraw the circuit using the wye equivalents.


$$R_{ab} = 1.5 + 12.5 + \frac{(120)(80)}{200} + 18 = 14 + 48 + 18 = 80 \Omega$$

[b] When $v_{ab} = 400$ V

$$i_g = \frac{400}{80} = 5 \text{ A}$$

$$i_{31} = \frac{48}{80}(5) = 3 \text{ A}$$


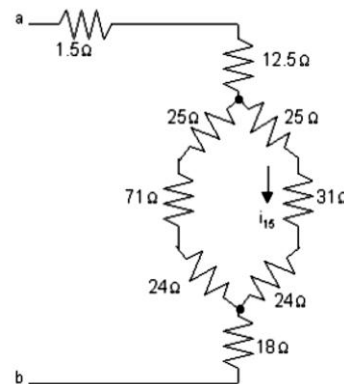
$$p_{31\Omega} = (31)(3)^2 = 279 \text{ W}$$



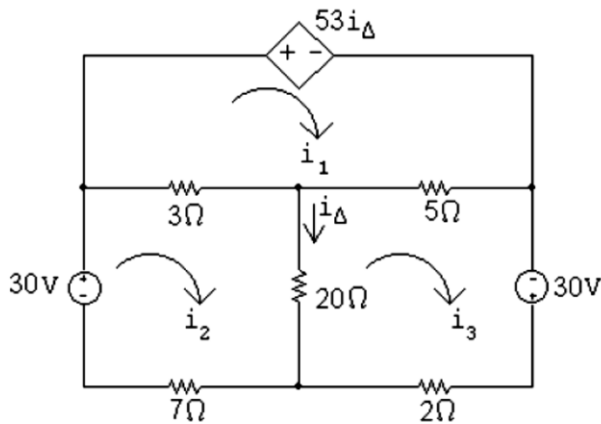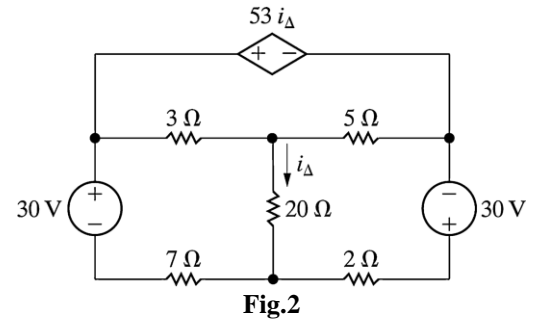Question (2): [12 Marks]

For the circuit shown in Fig.2.

- Write the node voltage equations needed to find the current i_{Δ} . (*Write both the main and the auxiliary equations*).
 - Write the mesh current equations needed to find the current i_{Δ} . (*Write both the main and the auxiliary equations*).
- Solve by yourself.
 -



Mesh equations:

$$53i_{\Delta} + 8i_1 - 3i_2 - 5i_3 = 0$$

$$0i_{\Delta} - 3i_1 + 30i_2 - 20i_3 = 30$$

$$0i_{\Delta} - 5i_1 - 20i_2 + 27i_3 = 30$$

Constraint equations:

$$i_{\Delta} = i_2 - i_3$$

Question (3): [12 Marks]

- Find the Norton equivalent circuit with respect to the terminals a,b for the circuit seen in Fig.3.
- Find the maximum power that could be transferred to the load connected across the terminals a,b.


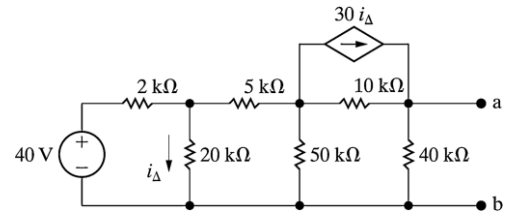


Fig.3

- Norton equivalent circuit

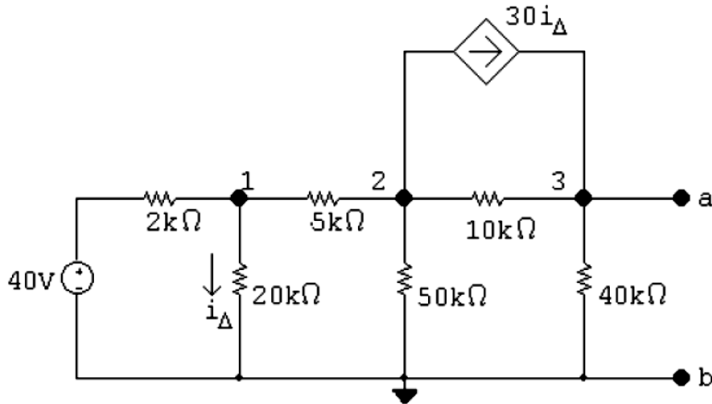

The node voltage equations are:

$$\frac{v_1 - 40}{2000} + \frac{v_1}{20,000} + \frac{v_1 - v_2}{5000} = 0$$

$$\frac{v_2 - v_1}{5000} + \frac{v_2}{50,000} + \frac{v_2 - v_3}{10,000} + 30 \frac{v_1}{20,000} = 0$$

$$\frac{v_3 - v_2}{10,000} + \frac{v_3}{40,000} - 30 \frac{v_1}{20,000} = 0$$

In standard form:


$$v_1 \left(\frac{1}{2000} + \frac{1}{20,000} + \frac{1}{5000} \right) + v_2 \left(-\frac{1}{5000} \right) + v_3(0) = \frac{40}{2000}$$

$$v_1 \left(-\frac{1}{5000} + \frac{30}{20,000} \right) + v_2 \left(\frac{1}{5000} + \frac{1}{50,000} + \frac{1}{10,000} \right) + v_3 \left(-\frac{1}{10,000} \right) = 0$$

$$v_1 \left(-\frac{30}{20,000} \right) + v_2 \left(-\frac{1}{10,000} \right) + v_3 \left(\frac{1}{10,000} + \frac{1}{40,000} \right) = 0$$

Solving, $v_1 = 24 \text{ V}$; $v_2 = -10 \text{ V}$; $v_3 = 280 \text{ V}$

$V_{Th} = v_3 = 280 \text{ V}$

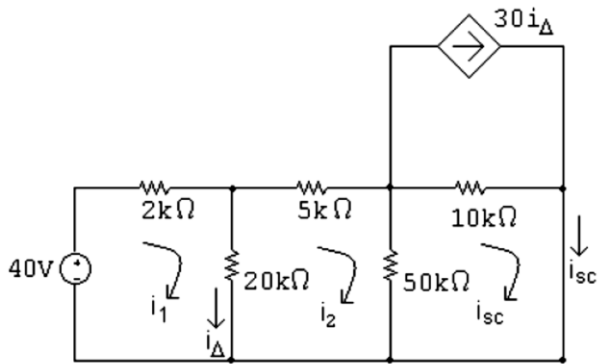

The mesh current equations are:

$$-40 + 2000i_1 + 20,000(i_1 - i_2) = 0$$

$$5000i_2 + 50,000(i_2 - i_{sc}) + 20,000(i_2 - i_1) = 0$$

$$50,000(i_{sc} - i_2) + 10,000(i_{sc} - 30i_{\Delta}) = 0$$

The constraint equation is:

$$i_{\Delta} = i_1 - i_2$$

Put these equations in standard form:

$$i_1(22,000) + i_2(-20,000) + i_{sc}(0) + i_{\Delta}(0) = 40$$


$$i_1(-20,000) + i_2(75,000) + i_{sc}(-50,000) + i_{\Delta}(0) = 0$$

$$i_1(0) + i_2(-50,000) + i_{sc}(60,000) + i_{\Delta}(-300,000) = 0$$

$$i_1(-1) + i_2(1) + i_{sc}(0) + i_{\Delta}(1) = 0$$

Solving, $i_1 = 13.6 \text{ mA}$; $i_2 = 12.96 \text{ mA}$; $i_{sc} = 14 \text{ mA}$; $i_{\Delta} = 640 \mu\text{A}$
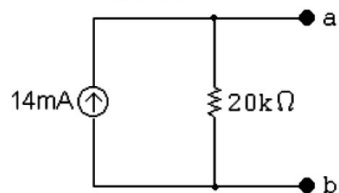
$$R_{Th} = \frac{280}{0.014} = 20 \text{ k}\Omega$$



b) The maximum power transferred to the load = $(V_{th})^2/4R_{th} = 0.98 \text{ Watt}$

Question (4): [12 Marks]

The two op-amps in the circuit in Fig.4 are ideal, calculate v_{o1} and v_{o2} .


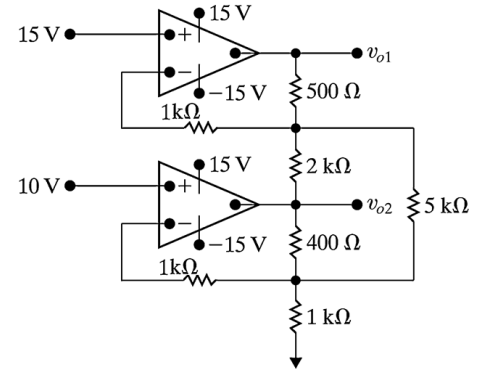


Fig.4

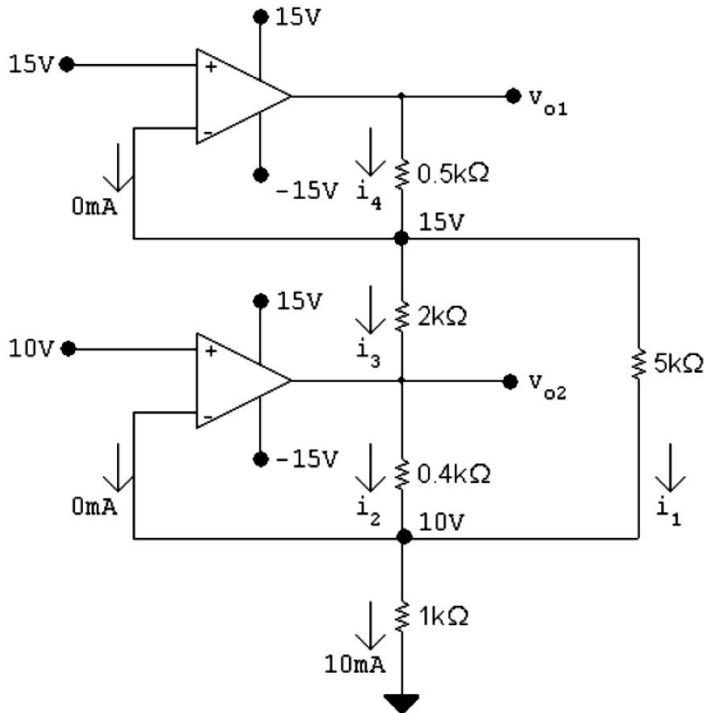No current flows in the resistors in the feedback, so they are neglected.



$$i_1 = \frac{15 - 10}{5000} = 1 \text{ mA}$$

$$i_2 + i_1 + 0 = 10 \text{ mA}; \quad i_2 = 9 \text{ mA}$$

$$v_{o2} = 10 + (400)(9) \times 10^{-3} = 13.6 \text{ V}$$

$$i_3 = \frac{15 - 13.6}{2000} = 0.7 \text{ mA}$$

$$i_4 = i_3 + i_1 = 1.7 \text{ mA}$$

$$v_{o1} = 15 + 1.7(0.5) = 15.85 \text{ V}$$

Question (5): [12 Marks]

The switch in the circuit of Fig.5 has been in position **a** for a long time. At $t = 0$, it moves instantaneously to position **b**. For $t \geq 0^+$, find:


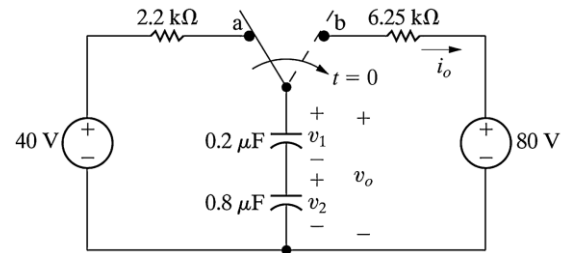



Fig.5

- $v_o(t)$.
- $i_o(t)$.
- $v_1(t)$.
- $v_2(t)$.
- The energy trapped in the capacitors as $t \rightarrow \infty$.

[a] $t < 0$

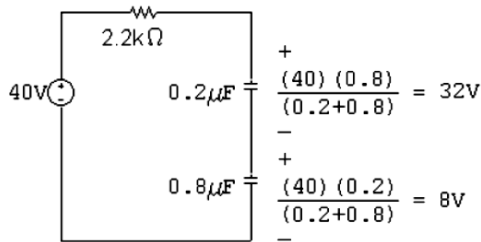

$t > 0$

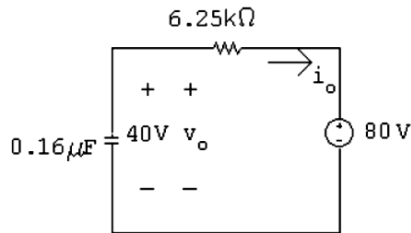

$$v_o(0^-) = v_o(0^+) = 40\text{V}$$

$$v_o(\infty) = 80\text{V}$$

$$\tau = (0.16 \times 10^{-6})(6.25 \times 10^3) = 1\text{ms}; \quad 1/\tau = 1000$$

$$v_o = 80 - 40e^{-1000t}\text{V}, \quad t \geq 0$$

$$\begin{aligned}
 \text{[b]} \quad i_o &= -C \frac{dv_o}{dt} = -0.16 \times 10^{-6} [40,000e^{-1000t}] \\
 &= -6.4e^{-1000t}\text{mA}; \quad t \geq 0^+
 \end{aligned}$$

$$\begin{aligned}
 \text{[c]} \quad v_1 &= \frac{-1}{0.2 \times 10^{-6}} \int_0^t -6.4 \times 10^{-3} e^{-1000x} dx + 32 \\
 &= 64 - 32e^{-1000t}\text{V}, \quad t \geq 0
 \end{aligned}$$

$$\begin{aligned}
 \text{[d]} \quad v_2 &= \frac{-1}{0.8 \times 10^{-6}} \int_0^t -6.4 \times 10^{-3} e^{-1000x} dx + 8 \\
 &= 16 - 8e^{-1000t}\text{V}, \quad t \geq 0
 \end{aligned}$$

$$\text{[e]} \quad w_{\text{trapped}} = \frac{1}{2}(0.2 \times 10^{-6})(64)^2 + \frac{1}{2}(0.8 \times 10^{-6})(16)^2 = 512\mu\text{J}.$$

With best wishes