

Question 1 (10 marks)

In the circuit in Fig.1. Use the $Y \Leftrightarrow \Delta$ transformations to find the total resistance between a and b terminals.



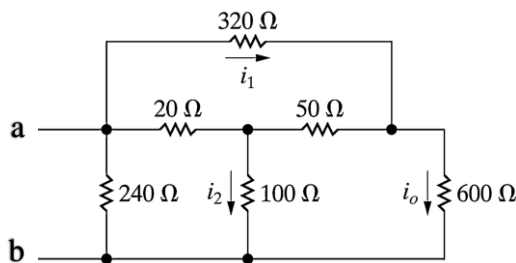


Fig.1

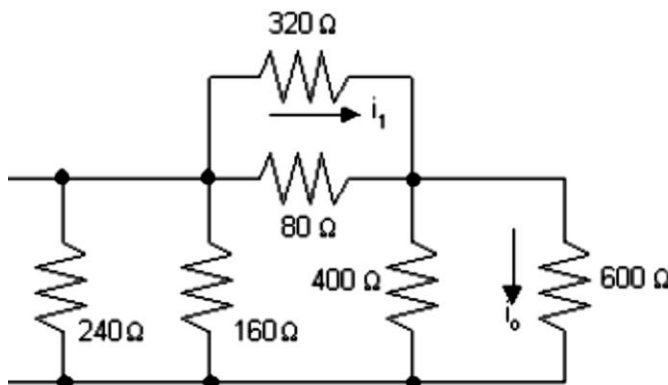After the $20\ \Omega - 100\ \Omega - 50\ \Omega$ wye is replaced by its equivalent delta, the circuit reduces to



Now the circuit can be reduced to

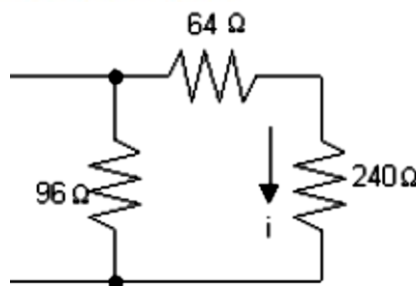


Then the equivalent circuit is the 96 ohm in parallel with $(64+240)$

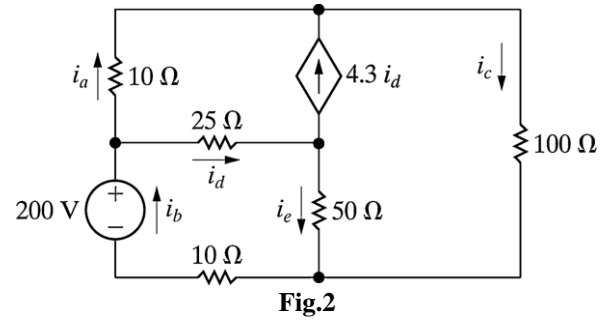
Question 2 (20 marks)

For the circuit shown in Fig.2,

- Write the node voltage equations needed to find the currents i_a to i_e . (*Write both the main equations and the auxiliary equations*).
- Write the mesh current equations needed to find the currents i_a to i_e . (*Write both the main equations and the auxiliary equations*).



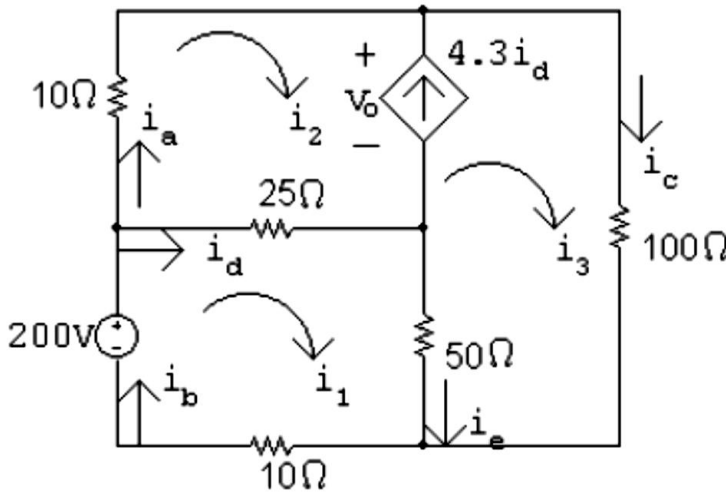- Write the node equations by yourself.
- Only needed the mesh equations



$$200 = 85i_1 - 25i_2 - 50i_3$$

$$0 = -75i_1 + 35i_2 + 150i_3 \quad (\text{supermesh})$$

$$i_3 - i_2 = 4.3(i_1 - i_2)$$

$$\text{Solving, } i_1 = 4.6 \text{ A; } \quad i_2 = 5.7 \text{ A; } \quad i_3 = 0.97 \text{ A}$$

$$i_a = i_2 = 5.7 \text{ A; } \quad i_b = i_1 = 4.6 \text{ A}$$


$$i_c = i_3 = 0.97 \text{ A; } \quad i_d = i_1 - i_2 = -1.1 \text{ A}$$

$$i_e = i_1 - i_3 = 3.63 \text{ A}$$

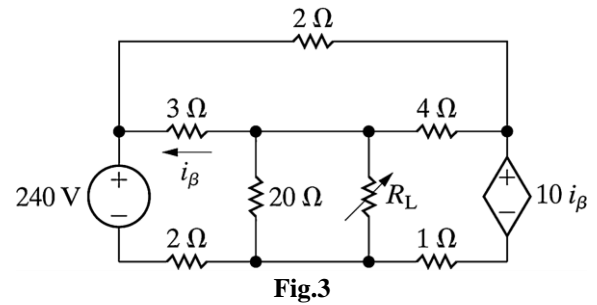Question 3 (20 marks)


The variable resistor R_L in the circuit shown in Fig.3 is adjusted for maximum power transfer to R_L .

- Find the numerical value of R_L .
- Find the maximum power transferred to R_L .
- Find the value of R_L if the power transferred to it is 24 Watt.



[a] Find the Thévenin equivalent with respect to the terminals of R_L .

Open circuit voltage:

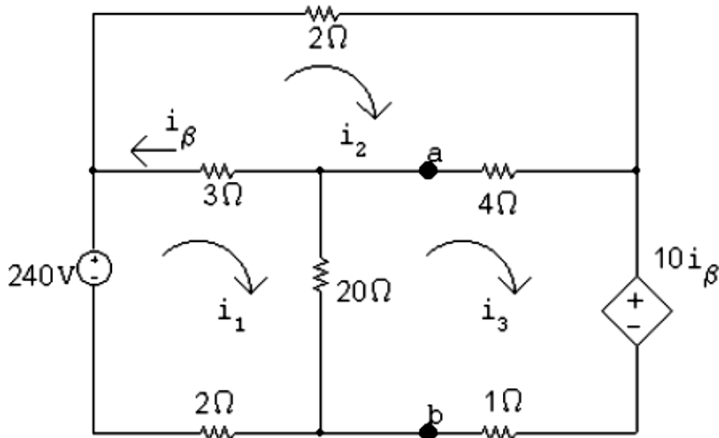

The mesh current equations are:

$$-240 + 3(i_1 - i_2) + 20(i_1 - i_3) + 2i_1 = 0$$

$$2i_2 + 4(i_2 - i_3) + 3(i_2 - i_1) = 0$$

$$10i_β + 1i_3 + 20(i_3 - i_1) + 4(i_3 - i_2) = 0$$

The dependent source constraint equation is:

$$i_β = i_2 - i_1$$

Place these equations in standard form:

$$i_1(3 + 20 + 2) + i_2(-3) + i_3(-20) + i_β(0) = 240$$

$$i_1(-3) + i_2(2 + 4 + 3) + i_3(-4) + i_β(0) = 0$$


$$i_1(-20) + i_2(-4) + i_3(1 + 20 + 4) + i_β(10) = 0$$

$$i_1(-1) + i_2(1) + i_3(0) + i_β(-1) = 0$$

Solving, $i_1 = 99.6 \text{ A}$; $i_2 = 78 \text{ A}$; $i_3 = 100.8 \text{ A}$; $i_β = 21.6 \text{ A}$

$$V_{Th} = 20(i_1 - i_3) = -24 \text{ V}$$

Short-circuit current:

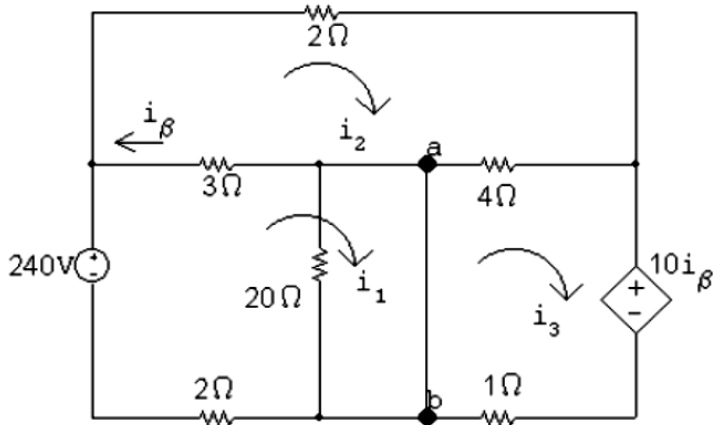

The mesh current equations are:

$$-240 + 3(i_1 - i_2) + 2i_1 = 0$$

$$2i_2 + 4(i_2 - i_3) + 3(i_2 - i_1) = 0$$

$$10i_\beta + 1i_3 + 4(i_3 - i_2) = 0$$

The dependent source constraint equation is:

$$i_\beta = i_2 - i_1$$

Place these equations in standard form:

$$i_1(3 + 2) + i_2(-3) + i_3(0) + i_\beta(0) = 240$$


$$i_1(-3) + i_2(2 + 4 + 3) + i_3(-4) + i_\beta(0) = 0$$

$$i_1(0) + i_2(-4) + i_3(4 + 1) + i_\beta(10) = 0$$

$$i_1(-1) + i_2(1) + i_3(0) + i_\beta(-1) = 0$$

Solving, $i_1 = 92 \text{ A}$; $i_2 = 73.33 \text{ A}$; $i_3 = 96 \text{ A}$; $i_\beta = 18.67 \text{ A}$
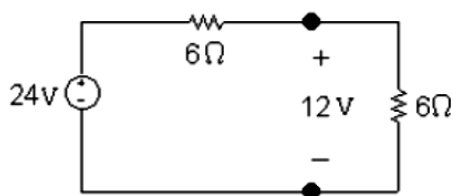
$$i_{sc} = i_1 - i_3 = -4 \text{ A}; \quad R_{Th} = \frac{V_{Th}}{i_{sc}} = \frac{-24}{-4} = 6 \Omega$$



$$R_L = R_{Th} = 6 \Omega$$

$$[b] p_{max} = \frac{12^2}{6} = 24 \text{ W}$$

[c] at $P_L = 24 \text{ Watt} = P_{max} \rightarrow R_L = R_{Th} = 6 \text{ ohms}$

Question 4 (8 marks) 10

The op amp in the circuit in Fig.4 is ideal. Using $V_{cc} = \pm 5V$,

- Find the range of values for σ in which the op amp does not saturate.
- Find i_o in microamperes when $\sigma = 0.272$


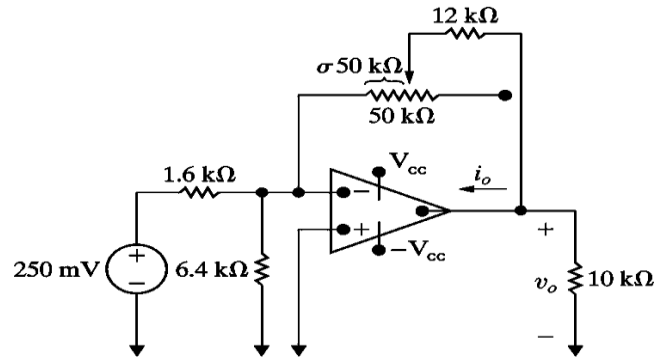


Fig.4

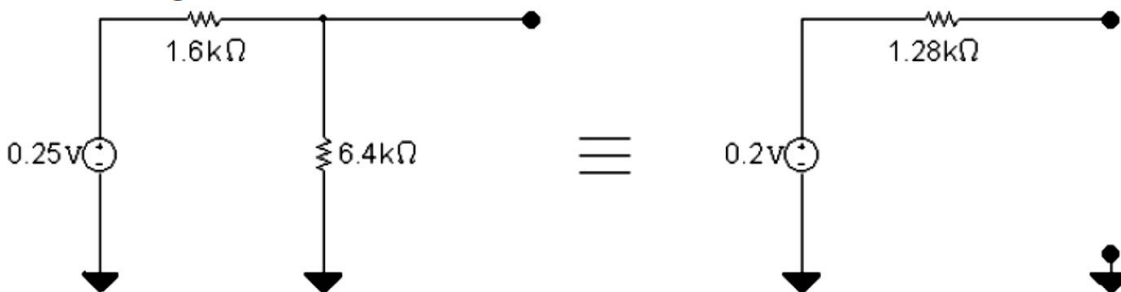- [a] Replace the combination of v_g , $1.6\text{ k}\Omega$, and the $6.4\text{ k}\Omega$ resistors with its Thévenin equivalent.



$$\text{Then } v_o = \frac{-(12 + \sigma 50)}{1.28} (0.20)$$

At saturation $v_o = -5\text{ V}$; therefore

$$-\left(\frac{12 + \sigma 50}{1.28}\right) (0.2) = -5, \text{ or } \sigma = 0.4$$

Thus for $0 \leq \sigma \leq 0.40$ the operational amplifier will not saturate.

[b] When $\sigma = 0.272$, $v_o = \frac{-(12 + 13.6)}{1.28} (0.20) = -4\text{ V}$

$$\text{Also } \frac{v_o}{10} + \frac{v_o}{25.6} + i_o = 0$$

$$\therefore i_o = -\frac{v_o}{10} - \frac{v_o}{25.6} = \frac{4}{10} + \frac{4}{25.6} \text{ mA} = 556.25 \mu\text{A}$$

Good Luck,