



**Question (1):**

Find the equivalent resistance  $R_{ab}$  for the circuits in Fig.1.


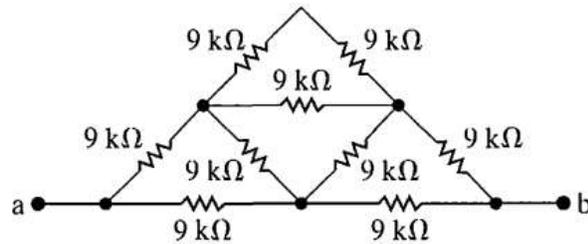


Fig.1

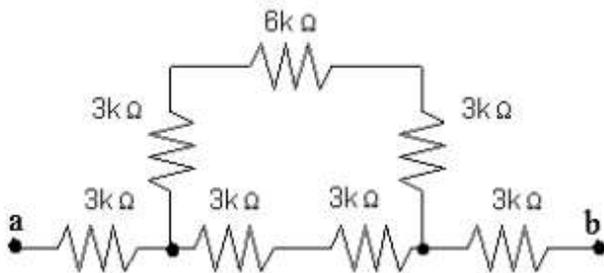**Ans:**

The top of the pyramid can be replaced by a resistor equal to  $R_1 = \frac{(18)(9)}{27} = 6 \text{ k}\Omega$

The lower left and right deltas can be replaced by wyes. Each resistance in the wye equals  $3 \text{ k}\Omega$ . Thus our circuit can be reduced to




Now the  $12 \text{ k}\Omega$  in parallel with  $6 \text{ k}\Omega$  reduces to  $4 \text{ k}\Omega$ .

$$\therefore R_{ab} = 3 \text{ k} + 4 \text{ k} + 3 \text{ k} = 10 \text{ k}\Omega$$

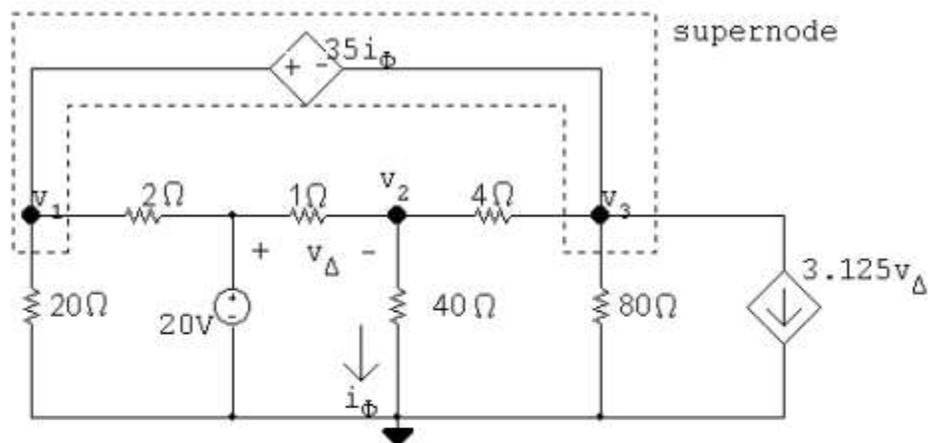**Question (2):**

Use the node-voltage method to find  $V_o$  in the circuit in Fig.2.



Node equations:

$$\frac{v_1}{20} + \frac{v_1 - 20}{2} + \frac{v_3 - v_2}{4} + \frac{v_3}{80} + 3.125v_\Delta = 0$$

$$\frac{v_2}{40} + \frac{v_2 - v_3}{4} + \frac{v_2 - 20}{1} = 0$$

Constraint equations:

$$v_\Delta = 20 - v_2$$

$$v_1 - 35i_\phi = v_3$$

$$i_\phi = v_2/40$$


Solving,  $v_1 = -20.25$  V;  $v_2 = 10$  V;  $v_3 = -29$  V

Let  $i_g$  be the current delivered by the 20 V source, then

$$i_g = \frac{20 - (20.25)}{2} + \frac{20 - 10}{1} = 30.125 \text{ A}$$

$$p_g \text{ (delivered)} = 20(30.125) = 602.5 \text{ W}$$

**Question (3): [a]**

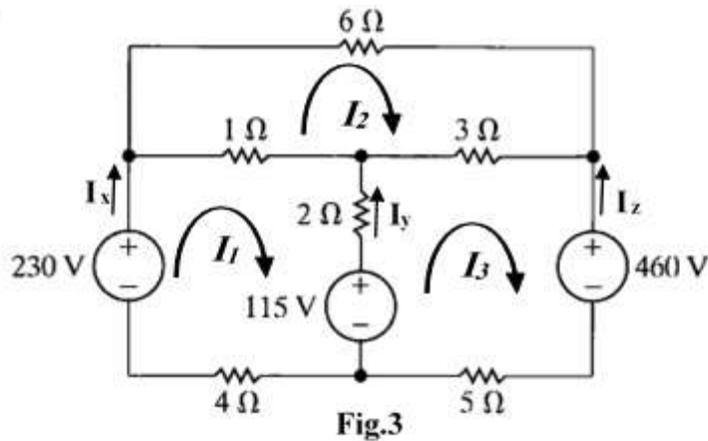

$$230 - 115 = 7i_1 - 1i_2 - 2i_3$$

$$0 = -1i_1 + 10i_2 - 3i_3$$

$$115 - 460 = -2i_1 - 3i_2 + 10i_3$$

Solving,  $i_1 = 4.4 \text{ A}$ ;  $i_2 = -10.6 \text{ A}$ ;  $i_3 = -36.8 \text{ A}$

$i_x = i_1 = 4.4 \text{ A}$ ,  $i_y = i_3 - i_1 = -41.2 \text{ A}$  and  $i_z = -i_3 = 36.8 \text{ A}$

$$p_{230} = -230i_1 = -1012 \text{ W (del)}$$

$$p_{115} = 115(i_1 - i_3) = 4738 \text{ W (abs)}$$

$$p_{460} = 460i_3 = -16,928 \text{ W (del)}$$

$$\therefore \sum p_{\text{dev}} = 17,940 \text{ W}$$

[b]  $p_{6\Omega} = (10.6)^2(6) = 674.16 \text{ W}$

$$p_{1\Omega} = (15)^2(1) = 225 \text{ W}$$

$$p_{3\Omega} = (26.2)^2(3) = 2059.32 \text{ W}$$

$$p_{2\Omega} = (41.2)^2(2) = 3394.88 \text{ W}$$

$$p_{4\Omega} = (4.4)^2(4) = 77.44 \text{ W}$$


$$p_{5\Omega} = (36.8)^2(5) = 6771.2 \text{ W}$$

$$\therefore \sum p_{\text{abs}} = 4738 + 674.16 + 225 + 2059.32 + 3394.88$$





$$+77.44 + 6771.2 = 17,940 \text{ W}$$

**Question (4):**


Q4  
a

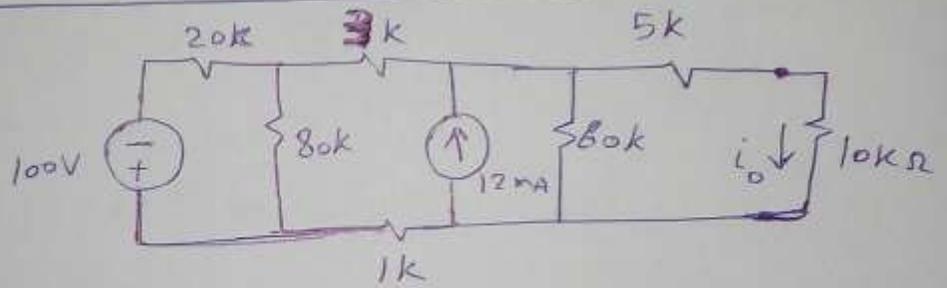

Source Transformation

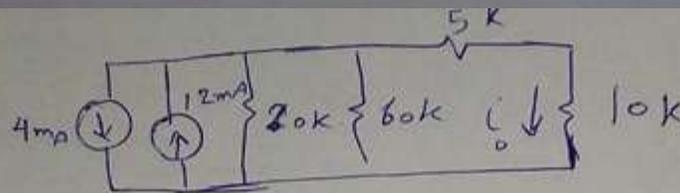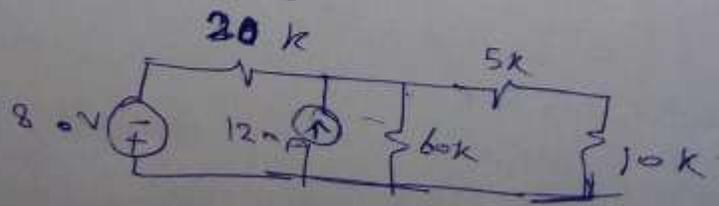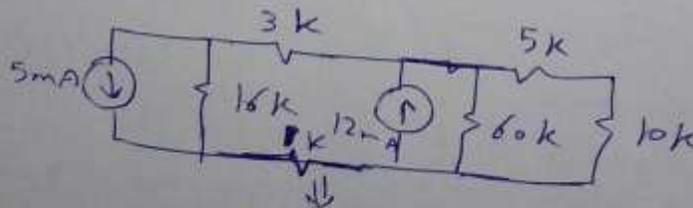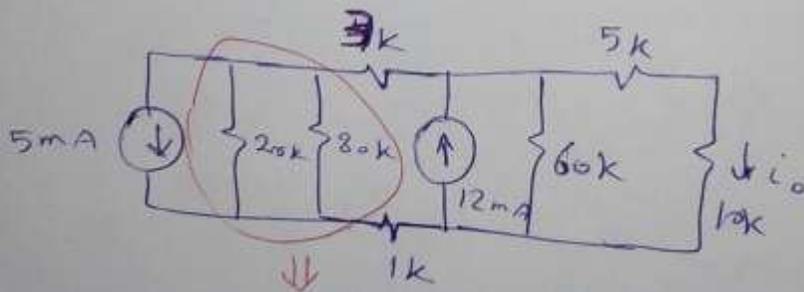


||

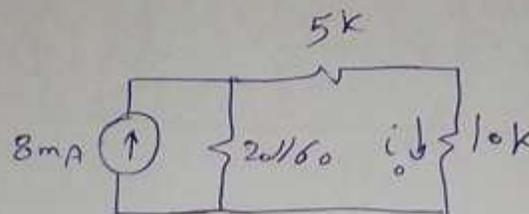

$$i_o = \frac{8\text{mA}}{2} = 4\text{mA}$$


4 (b)

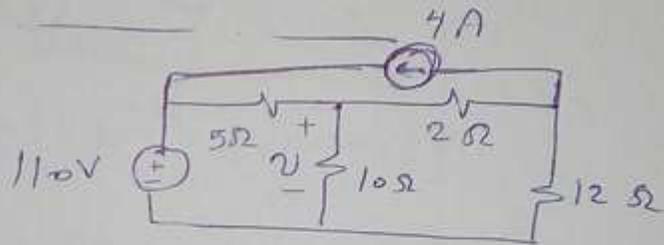

$$v = v_{110V} + v_{4A}$$

For 110V only active  $\Rightarrow$  4A open circuit
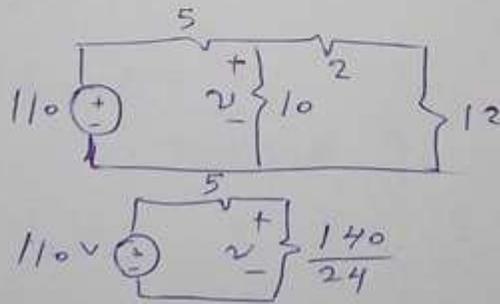
$$v_{10V} = \frac{140}{24} \times \frac{110}{\frac{140}{24} + 5} = 59.23 \text{ V}$$



For 4A only 110V short circuit

$$\frac{v}{5} + \frac{v - v_1}{2} + \frac{v}{10} = 0$$

$$\frac{v_1 - v}{2} + \frac{v_1}{12} + 4 = 0$$

$$6v_1 - 6v + v_1 = -48$$

$$7v_1 - 6v = -48 \rightarrow \textcircled{2}$$


Sub.  $\textcircled{1}$  in  $\textcircled{2}$

$$\frac{56}{5}v - 6v = -48$$

$$8v = 5v_1$$


$$\Rightarrow v_1 = \frac{8}{5}v \rightarrow \textcircled{1}$$

$$\Rightarrow v = -9.23$$

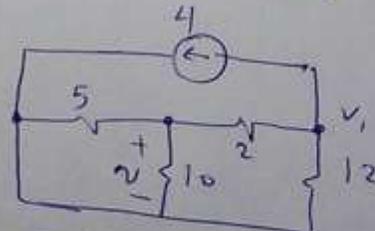


$$v = v_{4A} + v_{10V} = 50 \text{ V}$$

**Question (5):**

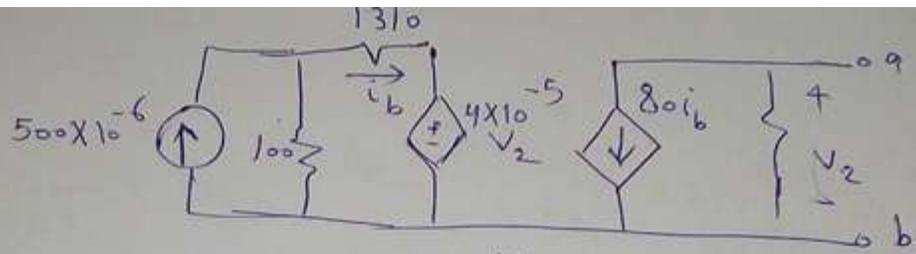

open circuit voltage

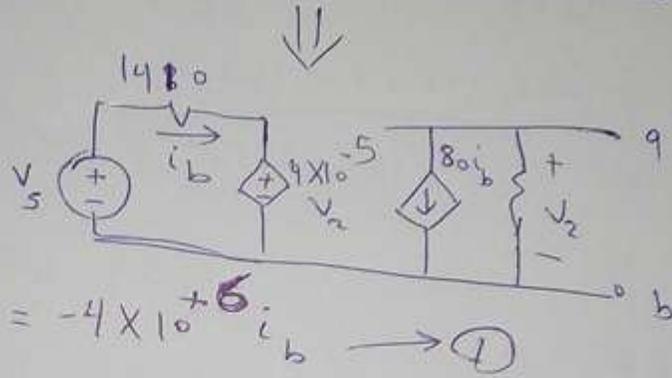

$$V_{ab} = V_2 = V_{OC}$$

$$V_{ab} = -80 i_b \times 50k = -4 \times 10^{-5} i_b \rightarrow \textcircled{1}$$


$$\therefore V_s = 500 \times 10^{-6} \times 100 = 5 \times 10^{-2} \text{ V (Source transformation)}$$

$$\text{So } 4 \times 10^{-5} V_2 = V_s - 1410 i_b$$

$$4 \times 10^{-5} V_{ab} = V_s - 1410 \left( \frac{-V_{ab}}{4 \times 10^5} \right)$$

$$10^{-5} \left( 4 - \frac{1410}{40} \right) V_{ab} = V_s$$
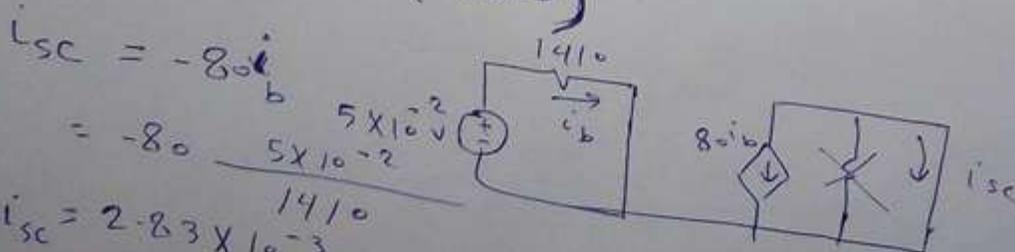
$$V_{ab} = \frac{-5 \times 10^{-2} \text{ (348.5)}}{10^{-5} \text{ (31.25)}} = -160 \text{ V} = V_{th}$$



$$I_{sc} = -80 i_b$$

$$= -80 \frac{5 \times 10^{-2}}{5 \times 10^{-2}}$$

$$I_{sc} = 2.83 \times 10^{-3}$$

$$R_{th} = \frac{V_{th}}{I_{sc}} = 56.4 \text{ k}\Omega$$


$$V_2 = V_T$$

$$i_T = \frac{V_T}{50 \times 10^3} + 80 i_b = \frac{V_T}{50 \times 10^3} + 80 \left( -\frac{4 \times 10^{-5}}{141 \Omega} V_T \right)$$

$$i_T = V_T \left[ \frac{141 - 8 \times 4 \times 50 \times 10^{-2}}{50 \times 10^3 \times 141 \Omega} \right]$$

$$\frac{V_T}{i_T} = R_{th} = 56.4 \text{ k}\Omega$$

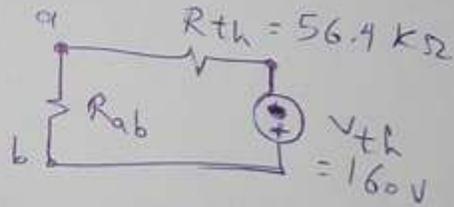© for max. power transfer  
 $R_{ab} = R_{th}$



$$\text{So } P_{max} = \frac{V_{th}^2}{4 R_{th}} = 0.1134 \text{ watt}$$

**Question (6):**

Q 6 (a)

$$V_x = V_c \times \frac{20}{50} = 0.4 V_c$$

$$\frac{V_x - V_b}{18 \text{ k}} + \frac{V_x - V_c}{20 \text{ k}} + \frac{V_x - V_o}{180 \text{ k}} = 0$$

$$\frac{0.4 V_c - V_b}{18 \text{ k}} + \frac{0.4 V_c - V_c}{20 \text{ k}} + \frac{0.4 V_c - V_o}{180 \text{ k}} = 0$$

$$4 V_c - 10 V_b + 3.6 V_c - 9 V_o = 0$$

$$8 V_c - 10 V_b - 9 V_o = 0$$

$$V_o = 8(3) - 10(2) - 9(1) = -5V$$

$$\textcircled{b} \quad 8V_c - 20 - 9 = V_o$$

$$8V_c = 29 + V_o$$

$$V_c = \frac{29 + V_o}{8}$$

$$-\frac{V_{cc}}{8} \leq V_o \leq V_{cc}$$

$$\frac{29 - \frac{V_{cc}}{8}}{8} \leq V_c \leq \frac{29 + V_{cc}}{8}$$

$$\frac{29 - \frac{V_{cc}}{8}}{8} \leq V_c \leq \frac{29 + \frac{20}{8}}{8}$$

$$1.125 \leq V_c \leq 6.125$$

$\textcircled{c}$  Mathematical eqn:-

$$Z = -9W - 10X + 8Y$$