



Answer the following questions:

Q1: Complete the following sentences:

- i. is the boundary between p-type and n-type semiconductors in a diode.
- ii. The PIV is the maximum voltage appearing across the diode in
- iii. The output frequency of a half-wave rectifier the input frequency.
- iv. Diode cut off voltage above or below specified levels.
- v. The DC value of a half wave rectifier voltage with a peak sinusoidal value of 10V is
- vi. The ripple factor can be decreased by increasing the value of the
- vii. The operates in reverse breakdown region.
- viii. The term refers to two types of current: electron current and current.
- ix. The bias methods for discrete BJT circuit are using , , and
- x. A capacitor placed across the emitter resistor of CE amplifier is known as
- xi. In amplifier, the input and output voltages are 180° out of phase.
- xii. amplifier is known as an emitter-follower.

Q2: (a) Determine and sketch the output waveform for the network of Fig. (1).

(b) The Si Darlington transistor pair of Fig.(2) has $\beta_1 = \beta_2 = 50$ and $R_2 = 100 \text{ k}\Omega$. Find the values of R_1 and V_{CE1} needed to bias the circuit so that $V_{CE2} = 6\text{V}$.

Q3: Consider the circuit shown in Figure (3). Let $V_S = 12 \text{ V}$, $V_{Z0} = 6.2 \text{ V}$, and $r_z = 3\Omega$. The maximum power rating of the diode is $P = 1 \text{ W}$.

- (a) Determine $I_Z(\max)$ and R_i for no load.
- (b) If $I_Z(\min) = 0.1 I_Z(\max)$, determine $R_L(\min)$.

Q4: For the amplifier shown in Fig.(4), $\beta = 200$. (a) Determine the dc values of I_E and V_E .

(b) Using the small signal hybrid π -model calculate the values of R_i , R_o , and the voltage gain (v_o/v_s).

Q5: Consider the ac equivalent circuit in Figure (5). The transistor parameters are $\beta_1 = 120$, $\beta_2 = 80$, $V_{A1} = V_{A2} = \infty$, and $I_{C1} = I_{C2} = 1 \text{ mA}$.

- (a) Calculate the input resistance R_i , and the output resistance R_o .
- (b) Find the small-signal voltage gain $A_{v1} = V_{o1}/V_i$.
- (c) Determine the small signal voltage gain $A_{v2} = V_{o2}/V_{o1}$.
- (d) Find the overall small-signal voltage gain $A_v = V_{o2}/V_i$.
- (e) Calculate the current gain $A_i = (i_o/i_s)$.

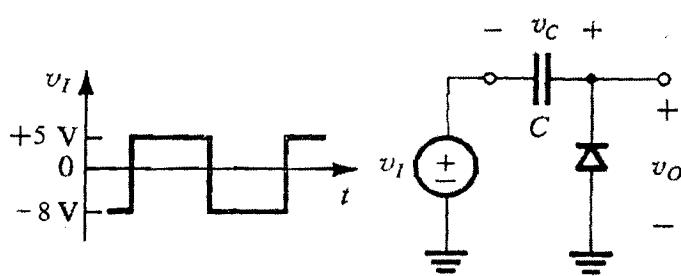


Fig.(1)

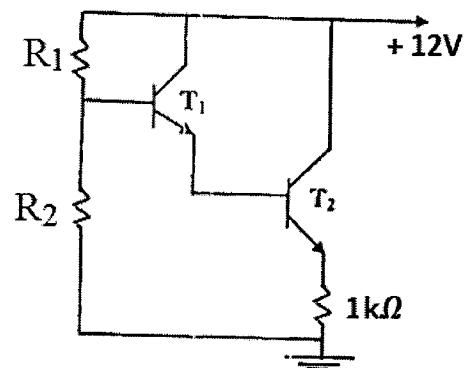


Fig.(2)

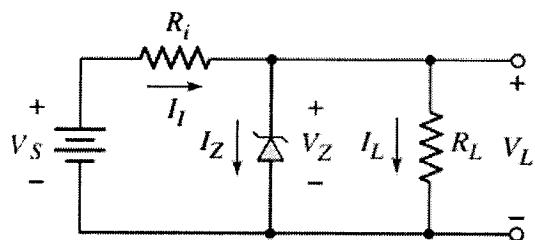


Fig.(3)

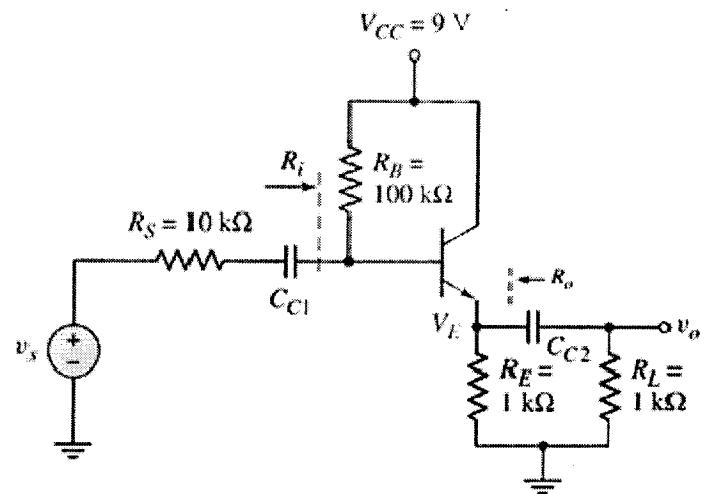


Fig.(4)

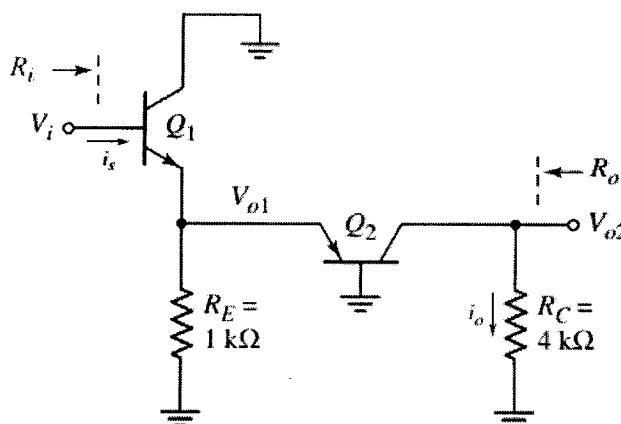


Fig.(5)

BEST WISHES

Hossam Labib



Answer the following questions:


Q1: Complete the following sentences:

- i. A pn junction is the boundary between p-type and n-type semiconductors in a diode.
- ii. The PIV is the maximum voltage appearing across the diode in reverse bias.
- iii. The output frequency of a half-wave rectifier equals the input frequency.
- iv. Diode limiters cut off voltage above or below specified levels.
- v. The DC value of a half wave rectifier voltage with a peak sinusoidal value of 10V is $10/\pi=3.1831V$.
- vi. The ripple factor can be decreased by increasing the value of the filter capacitor.
- vii. The zener diode operates in reverse breakdown region.
- viii. The term bipolar refers to two types of current: electron current and hole current.
- ix. The bias methods for discrete BJT circuit are using single power supply (voltage divider bias), using two power supplies, and using a collector-to- base feedback resistor, OR using constant current source.
- x. A capacitor placed across the emitter resistor of CE amplifier is known as bypass capacitor.
- xi. In common emitter amplifier, the input and output voltages are 180 out of phase.
- xii. A common-collector amplifier is known as an emitter-follower.

Q₂(a)

Determine and sketch the output waveform for the network of Fig. (1).


Solution:

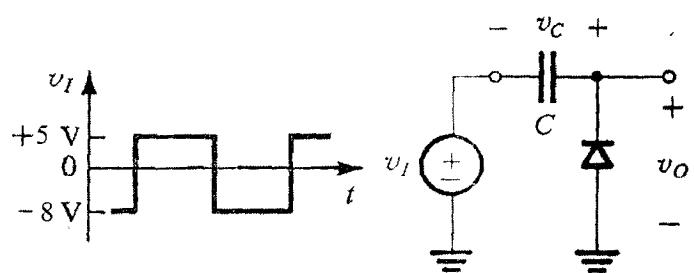

$$v_c = 8\text{ V}$$

$v_o = v_i + v_c$
i.e. $v_o = v_i$ shifted by $-ve$ half cycle.

$$\therefore v_o = v_i + 8\text{ V}$$

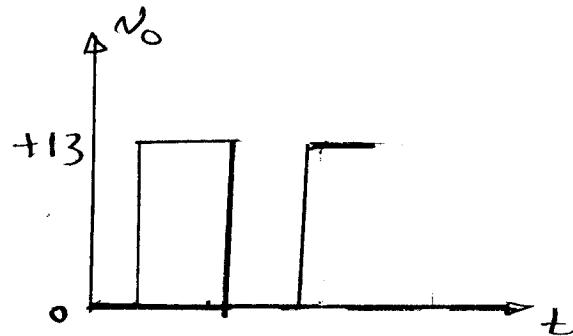

Q2(b)

The Si Darlington transistor pair of Fig.(2) has $\beta_1 = \beta_2 = 50$ and $R_2 = 100 \text{ k}\Omega$. Find the values of R_1 , and V_{CE1} needed to bias the circuit so that $V_{CE2} = 6V$.

Solution:

$$V_{C_1} = V_{C_2} = V_{CC} = 12 \text{ V}$$

$$\therefore V_{CE_2} = 6 \text{ V}$$

$$\therefore V_{CE_2} = V_{C_2} - V_{E_2}$$

$$\begin{aligned} \therefore V_{E_2} &= V_{C_2} - V_{CE_2} \\ &= 12 - 6 = 6 \text{ V} \end{aligned}$$

$$I_{E_2} = \frac{V_{E_2}}{R_{E_2}} = \frac{6}{1\text{K}} = 6 \text{ mA}$$

$$\begin{aligned} V_{B_1} &= V_{BE_1} + V_{BE_2} + V_{E_2} \\ &= 0.7 + 0.7 + 6 = 7.4 \text{ V} \end{aligned}$$

$$I_2 = \frac{V_{B_1}}{R_2} = \frac{7.4}{100\text{k}} = 74 \text{ mA}$$

$$I_{B_2} = I_{E_1} = \frac{I_{E_2}}{1+\beta_2} = \frac{6\text{mA}}{1+50} = 0.1176 \text{ mA}$$

$$I_{B_1} = \frac{I_{E_1}}{1+\beta_1} = \frac{0.1176\text{mA}}{51} = 2.306 \text{ mA}$$

$$\therefore I_1 = I_{B_1} + I_2 = 2.306 \text{ mA} + 74 \text{ mA} = 76.306 \text{ mA}$$

$$R_1 = \frac{V_{CC} - V_{B_1}}{I_1}$$



$$= \frac{12 - 7.4}{76.306 \text{ mA}} = 60.284 \text{ k}\Omega$$

$$V_{E_1} = V_{B_1} - V_{BE_1}$$

$$= 7.4 - 0.7 = 6.7 \text{ V}$$


$$\therefore V_{CE_1} = V_{C_1} - V_{E_1}$$

$$= 12 - 6.7 = 5.3 \text{ V}$$

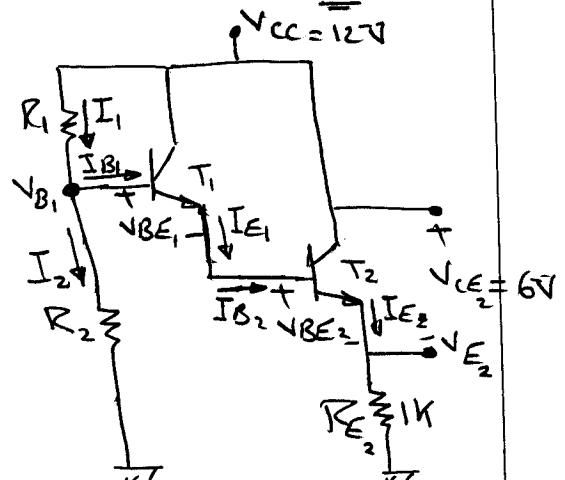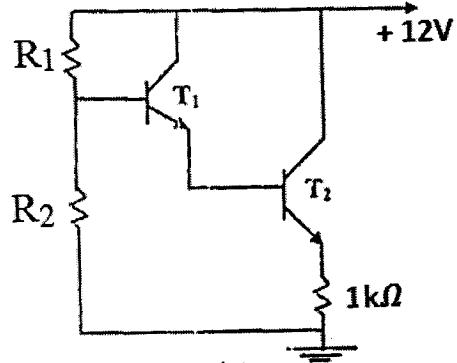

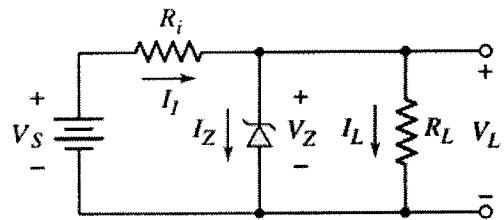Q3

Consider the circuit shown in Figure (). Let $V_S = 12 \text{ V}$, $V_{Z_0} = 6.2 \text{ V}$, and $r_Z = 3 \Omega$. The maximum power rating of the diode is $P_Z = 1 \text{ W}$. (a) Determine $I_Z(\max)$ and R_i for no load. (b) If $I_Z(\min) = 0.1 I_Z(\max)$, determine $R_L(\min)$



Solution:

$$V_S = 12 \text{ V} ; V_{Z_0} = 6.2 \text{ V} ; r_Z = 3 \Omega ; P_{Z\max} = 1 \text{ W}$$

(a) find $I_Z(\max)$ and R_i for no load


$$V_Z = V_{Z_0} + I_Z r_Z$$

$$V_Z = 6.2 + 3I_Z \quad \dots \textcircled{1}$$

$$\therefore P_Z = I_Z V_Z$$

$$1 = I_Z(6.2 + 3I_Z)$$
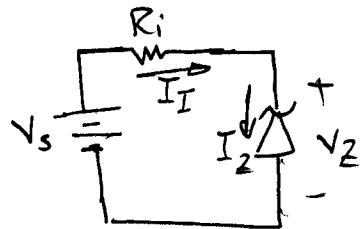
$$1 = 6.2I_Z + 3I_Z^2 \Rightarrow 3I_Z^2 + 6.2I_Z - 1 = 0$$



$$\therefore I_Z = \frac{-6.2 \pm \sqrt{(6.2)^2 + 4 \times 3 \times 1}}{2 \times 3} = -1.0333 \pm 1.1834$$

$$\therefore I_Z = -1.0333 + 1.1834 = 150 \text{ mA}$$

$$\text{or } I_Z = -1.0333 - 1.1834 = -2.217 \times \text{Rejected}$$

$$\therefore |I_Z|_{\max} = 150 \text{ mA} = |I_I|$$

$$V_Z = 6.2 + 3 \times 150 \text{ m} = 6.65 \text{ V} = V_L \mid_{\text{no load}}$$

$$R_i = \frac{V_S - V_Z}{I_I} = \frac{12 - 6.65}{150 \text{ m}} = 35.7 \Omega$$

(b) If $|I_Z|_{\min} = 0.1 |I_Z|_{\max}$ find $R_L|_{\min}$ and Load Regulation.

$$|I_Z|_{\min} = 0.1 \times 150 \text{ m} = 15 \text{ mA}$$


$$V_Z = V_L = V_{Z_0} + |I_Z|_{\min} r_Z \\ = 6.2 + 15 \text{ m} \times 3 = 6.245 \text{ V}$$

$$R_L|_{\min} = \frac{V_L}{I_L} = \frac{V_Z}{I_L}$$

$$\therefore I_L = I_I - |I_Z|_{\min}$$

$$\therefore I_L = 161.2 \text{ m} - 15 \text{ m} = 146.2 \text{ mA}$$

$$\therefore R_L|_{\min} = \frac{6.245}{146.2 \text{ m}} = 42.7 \Omega$$

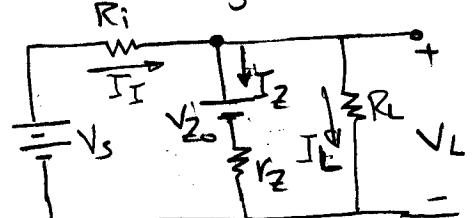

$$|I_I| = \frac{V_S - V_Z}{R_i} = \frac{12 - 6.245}{35.7} = 161.2 \text{ mA}$$

Q4

For the amplifier shown in Fig.(4), $\beta = 200$.

(a) Determine the dc values of I_E and V_E .

(b) Using the small signal hybrid π -model calculate the values of R_i , R_o , and the voltage gain (v_o/v_s).

Solution:

DC Analysis

- ALL capacitors are o.c

- Reduce AC sources

Loop (I)

$$-V_{CC} + I_B R_B + V_{BE} + I_E R_E = 0$$

$$\therefore I_B = \frac{I_E}{1+\beta}$$

$$-V_{CC} + \frac{I_E}{1+\beta} R_B + V_{BE} + I_E R_E = 0$$

$$-V_{CC} + I_E \left(\frac{R_B}{1+\beta} + R_E \right) + V_{BE}$$

$$I_E = \frac{V_{CC} - V_{BE}}{\frac{R_B}{1+\beta} + R_E} = \frac{9 - 0.7}{\frac{100k}{201} + 1k} = 5.543 \text{ mA}$$

$$V_E = I_E R_E = 5.543 \text{ mA} * 1k = 5.543 \text{ V}$$

$$I_C = \alpha I_E = \frac{200}{201} * 5.543 \text{ mA} = 5.515 \text{ mA}$$


$$\alpha_m = \frac{I_C}{V_T} = \frac{5.515 \text{ mA}}{25 \text{ mV}} = 220.6 \text{ mA/V}$$

$$r_{\pi} = \frac{\beta}{\alpha_m} = \frac{200}{220.6 \text{ mA}} = 906.62 \Omega$$

AC Analysis


- ALL capacitors are s.c

- Reduce DC sources

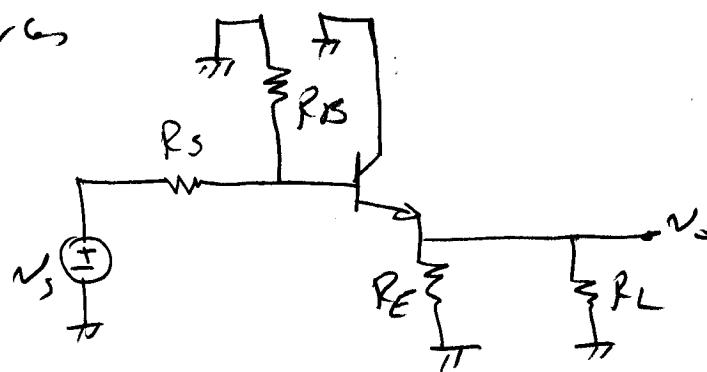

(5)

Q4 (cont.)

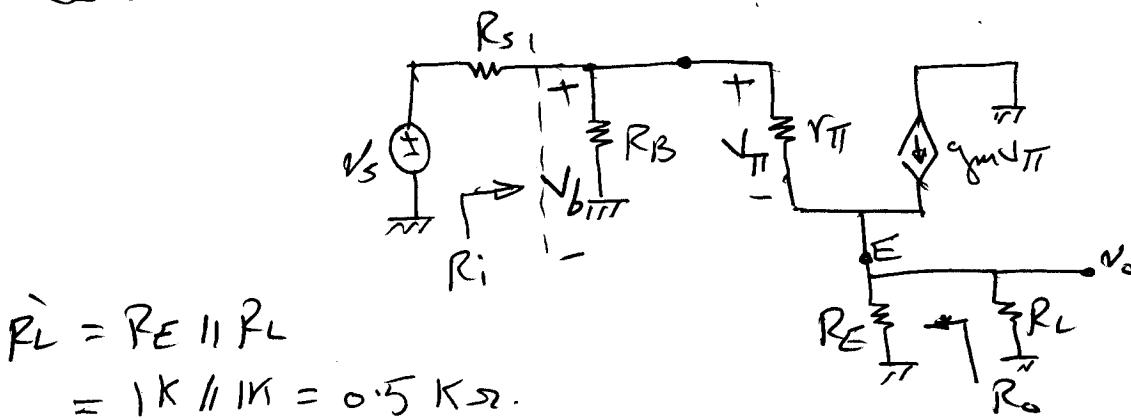

$$\bar{R_L} = R_E \parallel R_L$$

$$= 1K \parallel 1K = 0.5 K\Omega.$$

$$R_i = R_B \parallel [r_{pi} + (1+B)\bar{R_L}]$$

$$= 100K \parallel [906.62 + (1+200) \times 0.5K]$$

$$= 100K \parallel 101.41 K = 50.35 K\Omega.$$

$$R_{in} = \left[\frac{(R_S \parallel R_B + r_{pi})}{1+B} \right] \parallel R_E$$

$$N_b = \left[\frac{(10K \parallel 100K) + 906.62}{201} \right] \parallel 1K$$

$$= 49.74 \parallel 11K = 47.38 \Omega$$

To find $A_v = \frac{V_o}{V_s}$



$$N_b = \frac{V_s R_i}{R_i + R_s}$$

$$V_o = V_b \frac{(1+B)\bar{R_L}}{r_{pi} + (1+B)\bar{R_L}} = \frac{V_s R_i}{R_i + R_s} \times \frac{(1+B)\bar{R_L}}{r_{pi} + (1+B)\bar{R_L}}$$

$$\therefore A_v = \frac{V_b}{V_s} = \frac{R_i}{R_i + R_s} \frac{(1+B)\bar{R_L}}{r_{pi} + (1+B)\bar{R_L}}$$

$$= \frac{50.35K}{50.35K + 10K} \frac{201 \times 0.5K}{906.62 + 201 \times 0.5K}$$
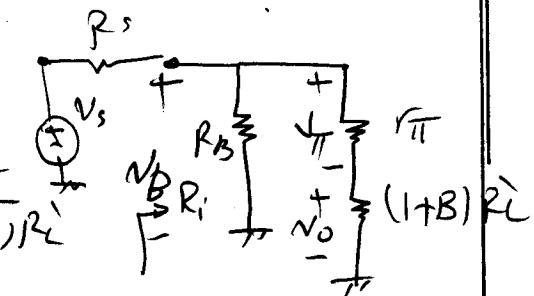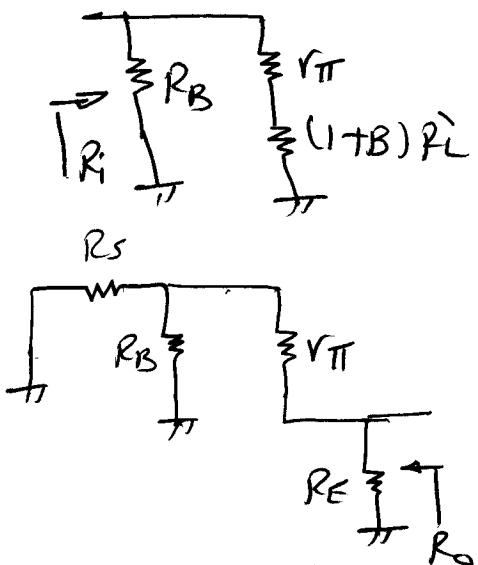
$$= 1.002 \times 0.9911 = 0.993 \text{ V/V}$$




Q5

Consider the ac equivalent circuit in Figure (5).

The transistor parameters are $\beta_1 = 120$, $\beta_2 = 80$, $V_{A1} = V_{A2} = \infty$, and $I_{C1} = I_{C2} = 1 \text{ mA}$.

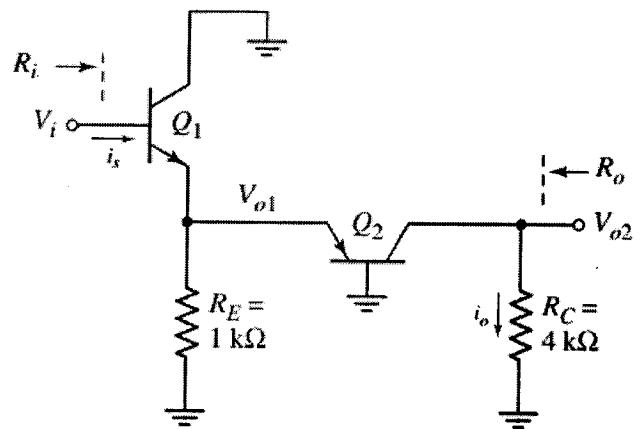- Calculate the input resistance R_i , and the output resistance R_o .
- Find the small-signal voltage gain $A_{V1} = V_{o1}/V_i$.
- Determine the small signal voltage gain $A_{V2} = V_{o2}/V_{o1}$.
- Find the overall small-signal voltage gain $A_v = V_{o2}/V_i$.
- Calculate the current gain $A_i = (i_o/i_s)$.



Solution:


$$\therefore I_{C1} = I_{C2} = 1 \text{ mA} = I_C \text{ (given)}$$

$$\therefore \alpha_{gm1} = \alpha_{gm2} = \frac{I_C}{\sqrt{T}} = \frac{1 \text{ mA}}{25 \text{ m}} = 40 \text{ mA/V}$$

$$r_{\pi 1} = \frac{\beta_1}{\alpha_{gm1}} = \frac{120}{40 \text{ m}} = 3 \text{ k}\Omega$$

$$r_{e2} = \frac{\alpha_2}{\alpha_{gm2}} \approx \frac{1}{\alpha_{gm2}} = \frac{1}{40 \text{ m}} = 25 \text{ }\Omega$$

Ac Analysis

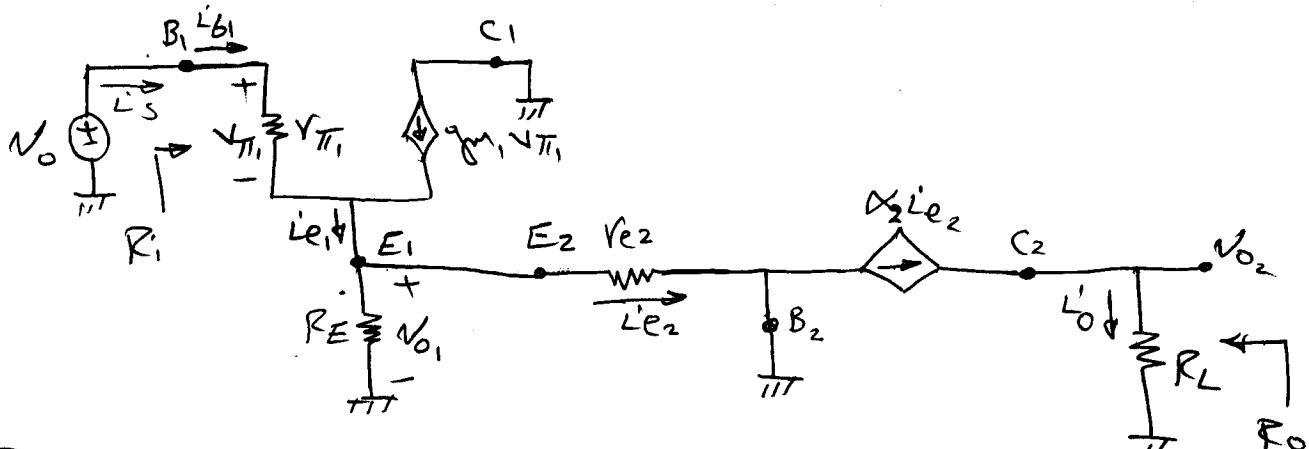

$$(a) R_{ET} = R_E \parallel r_{e2} = 1 \text{ k} \parallel 25 = 24.39 \text{ }\Omega$$

$$R_i = r_{\pi 1} + (1 + \beta_1) R_{ET}$$

$$= 3 \text{ k} + (1 + 120) * 24.39 = 5.95 \text{ k}\Omega$$


$$R_o|_{V_i=0} = R_C = 4 \text{ k}\Omega$$

Q5 (cont.)

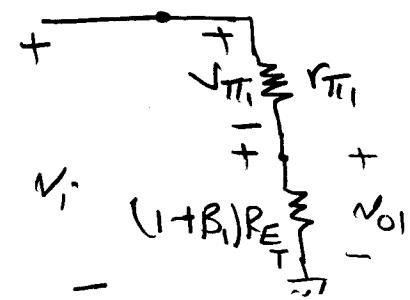(b) To find $A_{V_1} = \frac{V_{o_1}}{V_i}$

$$V_{o_1} = V_i \frac{(1+\beta_1) R_E}{r_{T_1} + (1+\beta_1) R_E}$$

$$\begin{aligned} \therefore A_{V_1} &= \frac{V_{o_1}}{V_i} = \frac{(1+\beta_1) R_E}{r_{T_1} + (1+\beta_1) R_E} \\ &= \frac{(1+12) * 24.39}{3K + 12 * 24.39} = 0.496 \text{ V/V} \end{aligned}$$



(c) To find $A_{V_2} = \frac{V_{o_2}}{V_{o_1}}$

$$V_{o_2} = \alpha_2 i_{e_2} R_C$$

$$i_{e_2} = \frac{V_{o_1}}{r_{e_2}}$$

$$\therefore V_{o_2} = \alpha_2 \frac{V_{o_1}}{r_{e_2}} R_C$$

$$\therefore A_{V_2} = \frac{V_{o_2}}{V_{o_1}} = \frac{\alpha_2}{r_{e_2}} R_C = \alpha_2 R_C$$

$$= 40m * 4K = 160 \text{ V/V}$$

$$(d) A_V = \frac{V_{o_2}}{V_i} = \frac{V_{o_1}}{V_i} * \frac{V_{o_2}}{V_{o_1}} = A_{V_1} * A_{V_2}$$

$$= 0.496 * 160 = 79.36 \text{ V/V}$$

(e) To find $A_L = \frac{L_o}{L_s}$

$$L_o = \alpha_2 L_{e_2}$$

$$L_{e_2} = L_{e_1} \frac{R_E}{R_E + r_{e_2}} \quad \therefore L_{e_1} = (1+\beta_1) L_{b_1}$$

$$\therefore L_{b_1} = L_s \Rightarrow L_{e_1} = (1+\beta_1) L_s$$

$$\therefore L_{e_2} = (1+\beta_1) L_s \frac{R_E}{R_E + r_{e_2}}$$

$$\therefore L_o = \alpha_2 (1+\beta_1) L_s \frac{R_E}{R_E + r_{e_2}}$$

$$\therefore A_L = \frac{L_o}{L_s} = \alpha_2 (1+\beta_1) \frac{R_E}{R_E + r_{e_2}}$$

$$= 1 * 121 \frac{1K}{1K + 25} = 118.05 \text{ A/A}$$