



Answer the following questions:

Q1: (a) Find the values of I and V in the circuits shown in Fig. (1).

(b) Fig.(2) shows a simpler way to draw a transistor circuit. What are collector-emitter voltage and the transistor power dissipation?

Q2: (a) In fig.(3), $V_i = 20\sin(\omega t)$ V. Sketch the output waveform. Assume the diode is actual.

(b) The transistor parameters for the circuit in Figure (4) are $\beta_1 = 120$, $\beta_2 = 80$, $V_{BE1(on)} = V_{BE2(on)} = 0.7$ V. Determine the quiescent collector current in each transistor.

Q3: The 6.8V zener diode in the circuit of Fig. (5) is specified to have $V_z = 6.8$ V at $I_z = 5$ mA, $r_z = 20\Omega$, and $I_{zk} = 0.2$ mA. The supply voltage V^+ is nominally 10V but can vary by ± 1 V.

- (a) Find V_0 with no load and with V^+ at its nominal value.
- (b) Find the change in V_0 resulting from the ± 1 V change in V^+ .
- (c) Find the change in V_0 when $R_L = 2$ k Ω .
- (d) What is the minimum value of R_L for which the diode still operates in the breakdown region?

Q4: For the circuit shown in Fig. (6), draw a complete small-signal equivalent circuit utilizing an appropriate T- model for the BJT. Your circuit should show the values of all components, including the model parameters. Find R_{in} , R_o , the voltage gain (v_o/v_{sig}) and the current gain (i_o/i_i). Assume that the transistor $\beta = 100$.

Q5: The parameters of the circuit shown in Fig.(7), are $V^+ = 3.3$ V, $V^- = -3.3$ V, $R_B = 100$ k Ω , $R_E = 15$ k Ω , $R_c = 10$ k Ω , $R_L = 2$ k Ω , and $R_S = 2$ k Ω . The transistor parameters are $\beta = 120$, and $V_A = \infty$. Determine the dc emitter current I_E and V_{CE} . Find using hybrid- π -model the values of R_i , the output resistance R_o , the voltage gain (v_o/v_s), and the current gain (i_o/i_i).

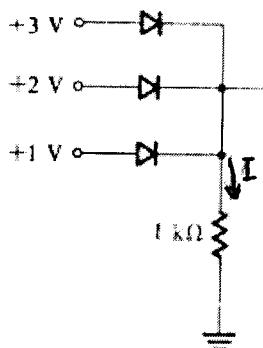


Fig.(1)

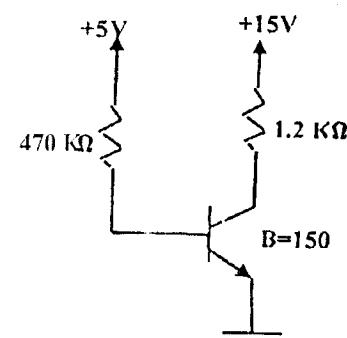
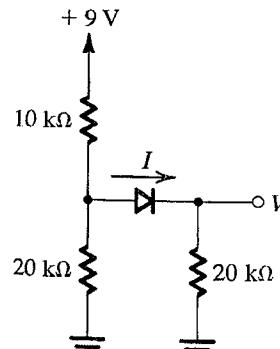


Fig.(2)

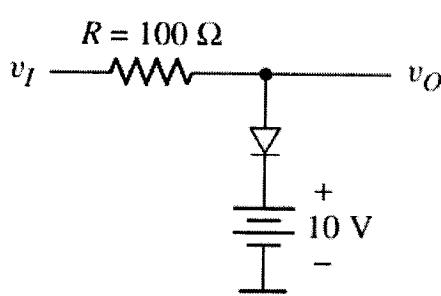


Fig.(3)

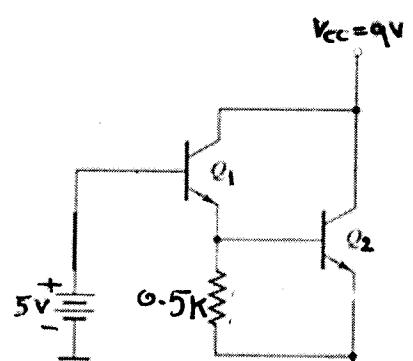


Fig.(4)

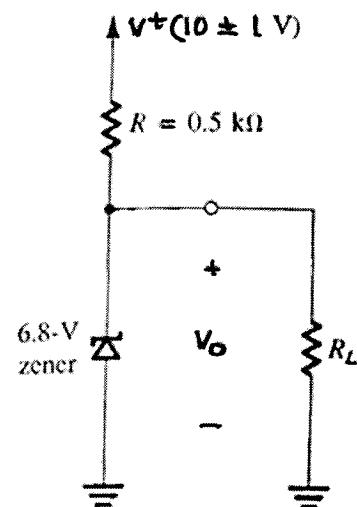


Fig.(5)

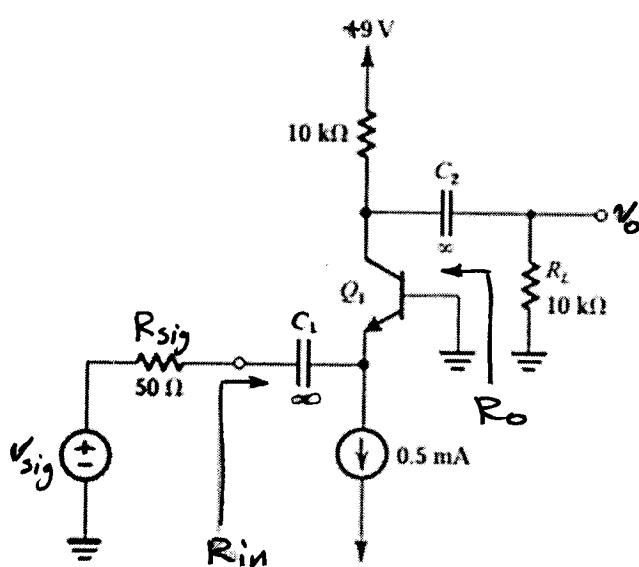


Fig.(6)

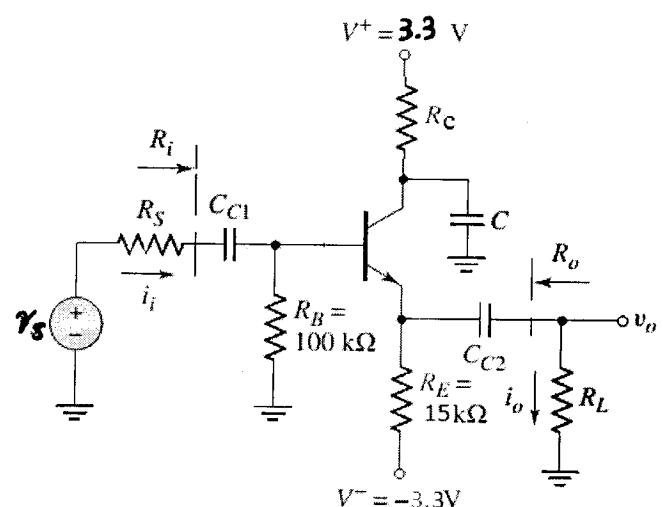


Fig.(7)

BEST WISHES
Hossam Labib


Q1 (a) Find the values of I and V in the circuits shown in Fig. (1).

For Fig. (a))

for D_1 on $V = 3V$, D_2 and D_3 are off

$$\therefore V = 3V$$
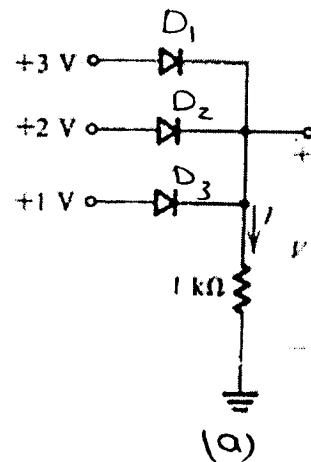
$$I = \frac{V}{R} = \frac{3}{1k\Omega} = 3mA$$



For Fig. (b)

$$V_p = \frac{9 * 20k}{10k + 20k} = 6V$$

Then diode is on and replaced by s.c

$$V = \frac{9 * (20k // 20k)}{10 + (20k // 20k)}$$

$$= \frac{9 * 10k}{20k} = 4.5V$$

$$I = \frac{V}{20k} = \frac{4.5}{20k} = 0.225mA$$

Another Solution




Using Thevenin The circuit becomes

$$V_{TH} = \frac{9 * 20k}{10k + 20k} = 6V ; R_{TH} = 10k // 20k = 6.67k$$

$\therefore V_p > V_n \Rightarrow$ Diode on

$$\therefore V = \frac{6 * 20k}{6.67k + 20k} = 4.5V$$

$$I = \frac{6}{6.67k + 20k} = 0.225mA$$

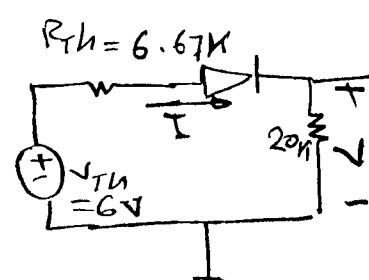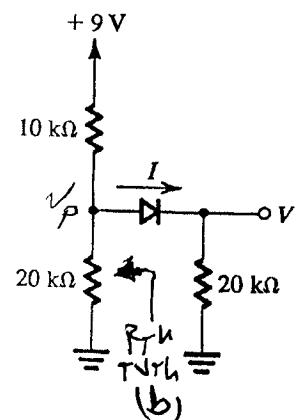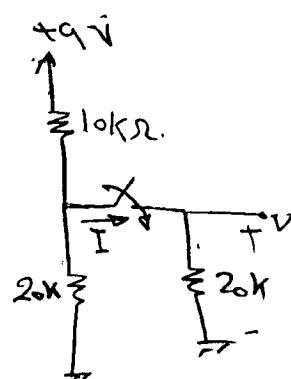

Q₁(b) (points)

Fig.(2) shows a simpler way to draw a Transistor circuit. What are collector emitter voltage and the Transistor power dissipation?

Solution

Let Transistor in ACTIVE Region

Loop (I)

$$5 = 470K I_B + V_{BE}$$

$$I_B = \frac{5 - 0.7}{470K} = 9.15 \text{ mA}$$

$$\therefore I_C = \beta I_B = 150 * 9.15 \text{ mA} = 1.3725 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C R_C = 15 - 1.3725 * 1.2 = 13.353 \text{ V}$$

$$\therefore V_E = 0 \text{ V} \quad , \quad \therefore V_{BE} = V_B - V_E$$

$$\therefore V_B = V_{BE} = 0.7 \text{ V} \quad ; \quad V_C = V_{CE} = 13.353 \text{ V}$$

$\because V_B > V_E \Rightarrow BE \text{ J Forward bias}$


$\because V_B < V_C \Rightarrow BC \text{ J Reverse bias}$

\therefore Transistor in ACTIVE Region

$$\therefore V_{CE} = 13.353 \text{ V} \quad ; \quad I_C = 1.3725 \text{ mA}$$

$$P_{diss} = I_{CQ} V_{CEQ}$$



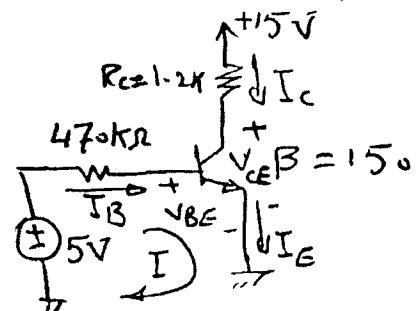
$$= 1.3725 * 10^{-3} * 13.353 = 0.0183 \text{ W}$$
$$= 18.3 \text{ mW}$$



Q2: (a)

In Fig. (3) $v_i = 20 \sin(\omega t)$ V. sketch the OIP waveform. Assume the diode is actual.

Solution

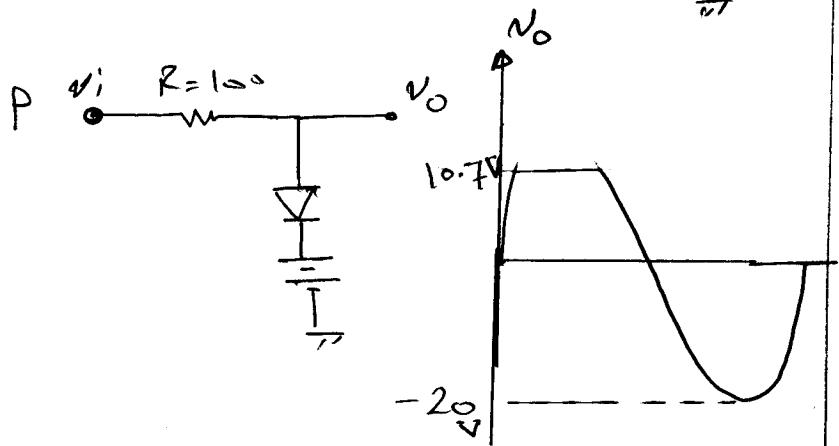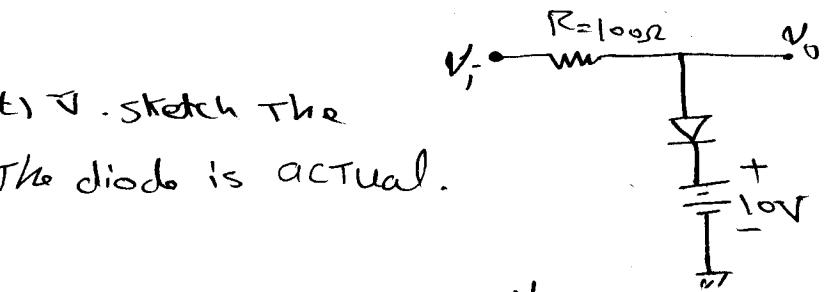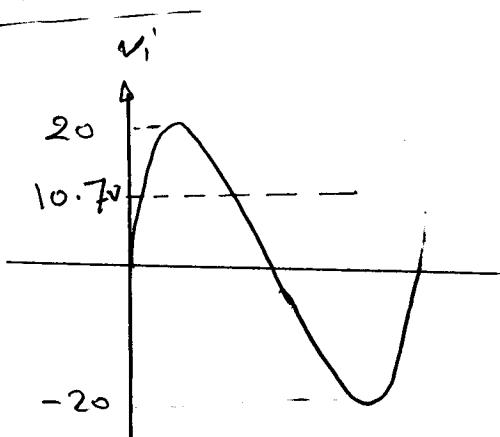

For +ve half cycle


for $v_i > 10.7 \Rightarrow$ diode is on

Then $v_o = 10.7$

for $v_i < 10.7 \Rightarrow$ diode is off

$$\therefore v_o = v_i$$

for -ve half cycle

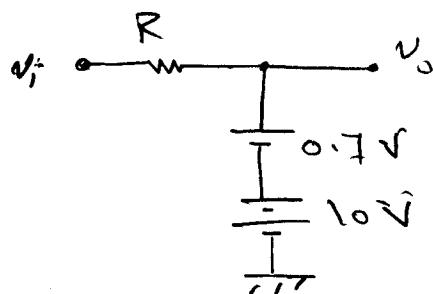

diode is off


$$\therefore v_o = v_i$$



(3)

Q2:

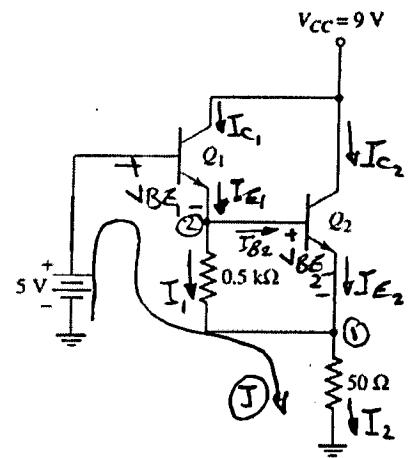- (b) The transistor parameters for the circuit in Figure (2) are $\beta_1 = 120$, $\beta_2 = 80$, $V_{BE1(on)} = V_{BE2(on)} = 0.7$ V. Determine the quiescent collector current in each transistor.



Solution

Loop P(I)

$$-5 + V_{BE1} + V_{BE2} + 50 \times I_2 = 0$$

$$I_2 = \frac{5 - V_{BE1} - V_{BE2}}{50}$$

$$= \frac{5 - 0.7 - 0.7}{50} = \frac{3.6}{50} = 72 \text{ mA}$$

$$I_1 = \frac{V_{BE2}}{0.5 \text{ k}\Omega} = \frac{0.7}{0.5 \text{ k}\Omega} = 1.4 \text{ mA}$$

at node (1)

$$I_1 + I_{E2} = I_2 \Rightarrow I_{E2} = I_2 - I_1$$

$$I_{E2} = (72 - 1.4) \text{ mA} = 70.6 \text{ mA}$$

$$I_{B2} = \frac{I_{E2}}{1 + \beta_2} = \frac{70.6 \text{ mA}}{81} = 871.605 \text{ mA}$$

$$I_{C2} = \beta_2 I_{B2} = 871.605 \mu \times 80 = 69.728 \text{ mA}$$

at node (2)

$$I_{E1} = I_{B2} + I_1 = 871.605 \mu + 1.4 \text{ mA} = 2.272 \text{ mA}$$

$$I_{C1} = \alpha_1 I_{B1}, I_{E1} = \frac{\beta_1}{1 + \beta_1} I_{E1}$$

$$= \frac{120}{121} \times 2.272 \text{ mA} = 2.253 \text{ mA}$$

Q3:- (12 points)

The 6.8 V Zener diode in the circuit shown is specified to have $V_Z = 6.8 \text{ V}$ at $I_Z = 5 \text{ mA}$, $r_Z = 20 \Omega$, and $I_{ZK} = 0.2 \text{ mA}$. The supply voltage V^+ is nominally 10 V but can vary by $\pm 1\text{V}$.

(a) Find V_0 with no load and with V^+ at its nominal value.

$$\therefore V_Z = V_{Z0} + V_Z I_Z$$

$$6.8 = V_{Z0} + 20 * 5 * 10^{-3}$$

$$\therefore V_{Z0} = 6.8 - 0.1 = 6.7 \text{ V}$$

With no load i.e. $R_L = \infty$

$$I = I_Z = \frac{V^+ - V_{Z0}}{R + r_Z}$$

$$= \frac{10 - 6.7}{0.5K + 20} = 6.35 \text{ mA}$$

$$\therefore V_0 = V_{Z0} + I_Z r_Z$$

$$= 6.7 + 6.35 * 20 = 6.83 \text{ V}$$

(b) Find the change in V_0 resulting from the $\pm 1\text{V}$ change in V^+ . The change in V_0 can be found from

$$\Delta V_0 = \Delta V^+ \frac{r_Z}{R + r_Z}$$

$$= \pm 1 * \frac{20}{0.5K + 20} = \pm 38.5 \text{ mV}$$

(c) Find the change in V_0 when $R_L = 2K\Omega$




If $R_L = 2K\Omega$ is connected

$$\therefore I_L \leq \frac{V_Z}{R_L} = \frac{6.8}{2K} = 3.4 \text{ mA}$$

$$I = \frac{10 - 6.8}{0.5K} = 6.4 \text{ mA}$$

$$\therefore I = I_Z + I_L \Rightarrow I_Z|_{\text{loaded}} = I - I_L =$$

$$I_Z|_{\text{loaded}} = 6.4 \text{ mA} - 3.4 \text{ mA} = 3 \text{ mA}$$

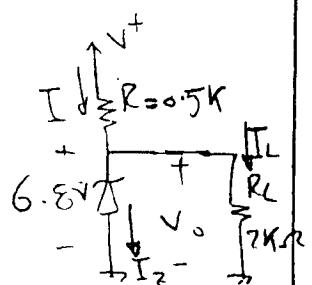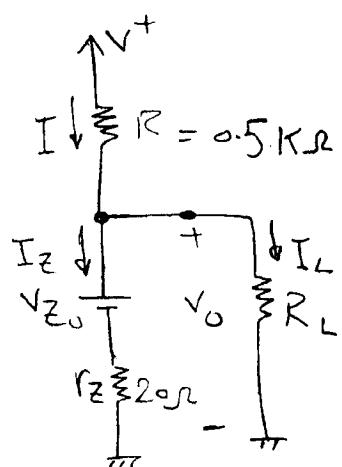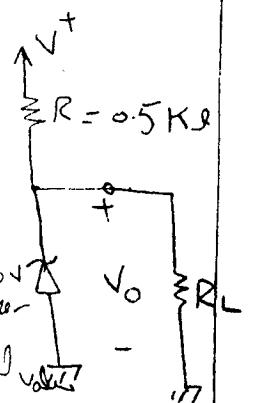

Q3: (Cont.)

$$\text{Change in Zener current } \Delta I_Z = I_Z|_{\text{Load}} - I_Z|_{\text{No-Load}}$$

$$\Delta I_Z = 3 - 6.35 = -3.4 \text{ mA}$$

$$\therefore \text{Change in } V_o \Rightarrow \Delta V_o = \Delta I_Z V_Z$$

$$\Delta V_o = -3.4 \text{ mA} \times 20 = -68 \text{ mV}$$

(d) What is the min. value of R_L for which the diode still operates in the breakdown region?

For the Zener at edge of the breakdown region then
 $I_Z = I_{ZK} = 0.2 \text{ mA}$ and $V_Z = V_{ZK} = 6.7 \text{ V}$

$$\therefore \text{AT This point The lowest current supplied through } R \text{ is } I = \frac{V_o - V_{ZK}}{R}$$

$$= \frac{9 - 6.7}{0.5 \text{ k}\Omega} = 4.6 \text{ mA}$$

$$\therefore I_L = I - I_Z = 4.6 - 0.2 = 4.4 \text{ mA}$$

$$R_L|_{\min} = \frac{V_o}{I_L} \approx \frac{V_Z}{I_L}$$

$$= \frac{6.7}{4.4 \text{ mA}} = 1.5 \text{ k}\Omega$$

Q4: For the circuit shown in Fig. (5), draw a complete small-signal equivalent circuit utilizing an appropriate T-model for the BJT (use $\alpha = 0.99$). Your circuit should show the values of all components, including the model parameters. Find R_{in} , R_o , the voltage gain (v_o/v_{sig}) and the current gain (i_o/i_i).

Solution

DC Analysis

- ALL capacitors are o.c

- Reduce AC sources


$$I_E = 0.5 \text{ mA}$$

$$r_e = \frac{V_T}{I_E} = \frac{25 \text{ mV}}{0.5 \text{ mA}} = 50 \Omega$$

AC Analysis

- ALL capacitors are s.c \Rightarrow Reduce DC sources i.e. V.S = S.C & C.S = o.c

Using T-model

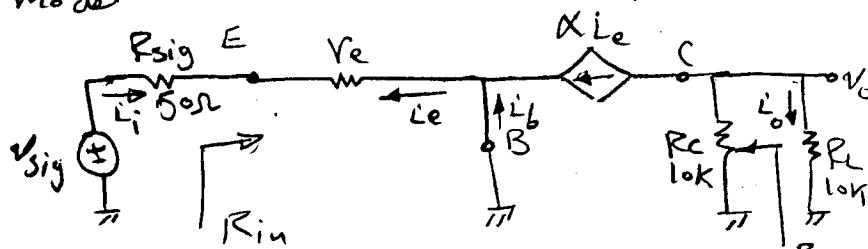

$$R_{in} = r_e = 50 \Omega$$

$$R_o = R_C = 10 \text{ k}\Omega$$

$$v_{sig} = 0$$




$$v_o = -\alpha i_e (R_C || R_L)$$

$$i_e = -i_i = \frac{-v_{sig}}{R_{sig} + r_e}$$

$$\therefore v_o = \frac{+\alpha v_{sig} (R_C || R_L)}{R_{sig} + r_e}$$

$$\therefore Av = \frac{v_o}{v_{sig}} = \frac{\alpha (R_C || R_L)}{R_{sig} + r_e}$$

$$Av = \frac{0.99 (10 \text{ k}\Omega || 10 \text{ k}\Omega)}{50 + 50} = \frac{0.99 + 5}{100} = 49.5 \text{ V/V}$$

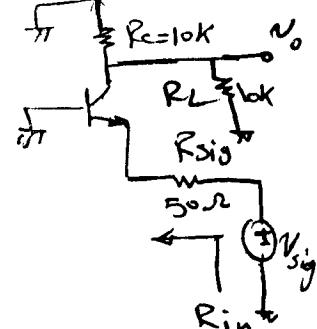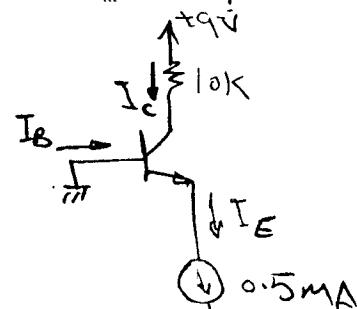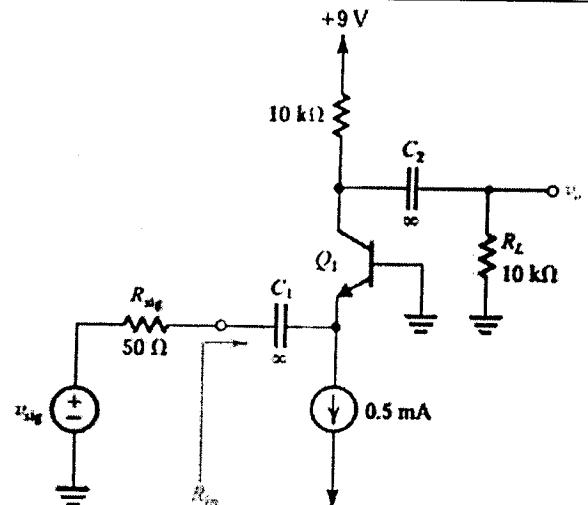

Q4: (Contd.)

To find $A_L = \frac{i_o}{i_i}$

$$i_o = -\alpha i_e \frac{R_c}{R_c + R_L}$$

$$i_i = -i_e$$

$$\therefore A_L = \frac{i_o}{i_i} = \frac{\alpha R_c}{R_c + R_L}$$

$$= \frac{0.99 * 10k}{10k + 10k} = \frac{0.99}{2} = 0.495 \text{ A/A}$$

Q5: (15 points)

The parameters of the circuit shown are

$$V^+ = 3.3 \text{ V}, V^- = -3.3 \text{ V}, R_B = 100 \text{ k}\Omega$$

$$R_E = 15 \text{ k}\Omega, R_L = 2 \text{ k}\Omega, R_S = 2 \text{ k}\Omega$$

and $R_C = 10 \text{ k}\Omega$. The Transistor

parameters are $\beta = 120$ and

$$\sqrt{A} = \infty \quad \text{(a) Determine } I_{EQ} \text{ and } V_{CEQ}.$$

$$\text{(b) Find } R_i, R_o \text{ if } A_v = \frac{V_o}{V_s}, \text{ and } A_i = \frac{I_o}{I_s}$$

Solution:-

DC Analysis

All capacitor are o.c and reduce AC sources

Loop ①

$$I_B R_B + V_{BE} + I_E R_E + V^- = 0$$

$$\therefore I_B = \frac{I_E}{1 + \beta}$$

$$\therefore \frac{I_E R_B}{1 + \beta} + V_{BE} + I_E R_E + V^- = 0$$

$$I_E \left(\frac{R_B}{1 + \beta} + R_E \right) = -V^- - V_{BE}$$

$$I_{EQ} = \frac{-V^- - V_{BE}}{R_E + \frac{R_B}{1 + \beta}} = \frac{3.3 - 0.7}{15 \text{ k} + \frac{100 \text{ k}}{121}} = 0.164 \text{ mA}$$

$$V_E = I_E R_E + V^- = 0.164 * 15 - 3.3 \text{ V} = -0.84 \text{ V}$$

$$V_{CEQ} = V_C - V_E \quad ; \quad V_C = V^+ - I_C R_C = 1.674 \text{ V}$$

$$V_{CEQ} = 1.674 - (-0.84) = 2.514 \text{ V}$$

$$I_C = \alpha I_E = \left(\frac{\beta}{1 + \beta} \right) I_E = \frac{120}{121} * 0.164 \text{ mA} = 0.1626 \text{ mA}$$



$$g_m = \frac{I_C}{V_T} = \frac{0.1626 \text{ mA}}{25 \text{ m}} = 6.504 \text{ mA/V}$$

$$r_e = \frac{V_T}{I_E} = \frac{25 \text{ m}}{0.164 \text{ mA}} = 152.44 \Omega$$

$$\therefore V_A = \infty \Rightarrow r_o = \infty$$



$$r_{\pi} = \frac{\beta}{g_m} = \frac{120}{6.504 \text{ mA}} = 18.45 \text{ k}\Omega$$

⑨ -

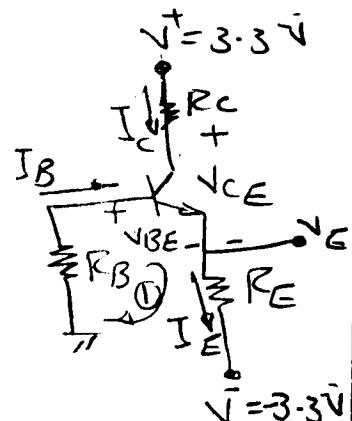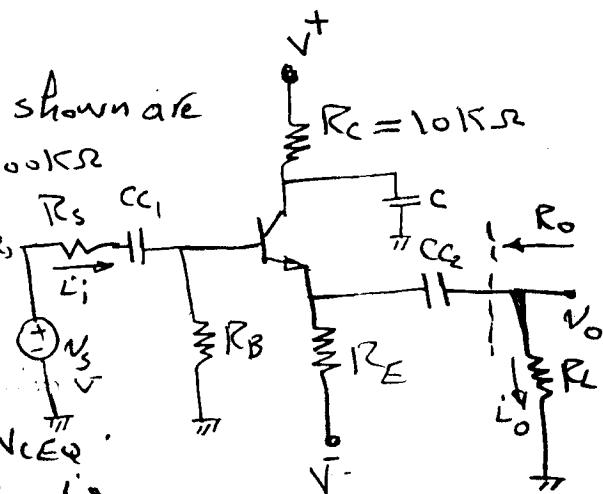

AC Analysis

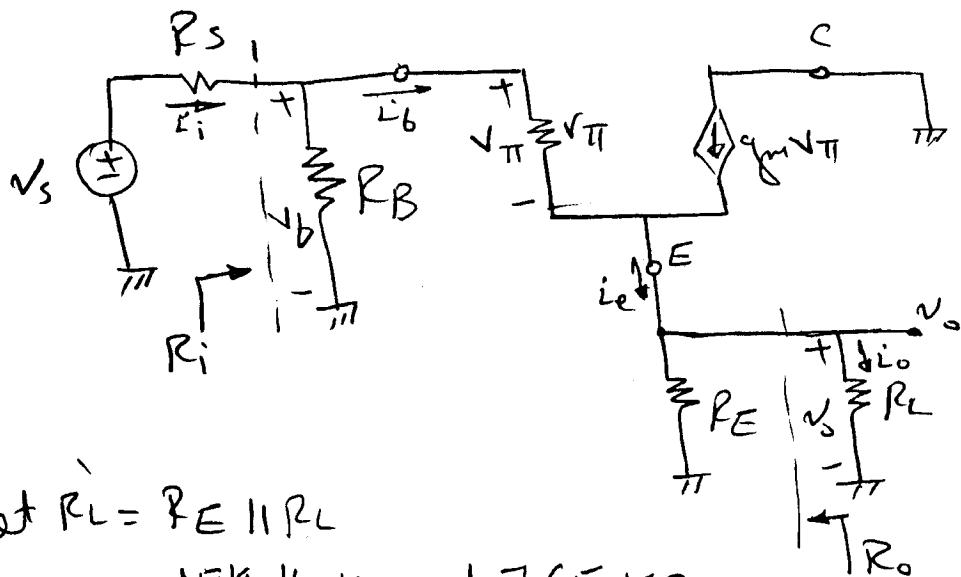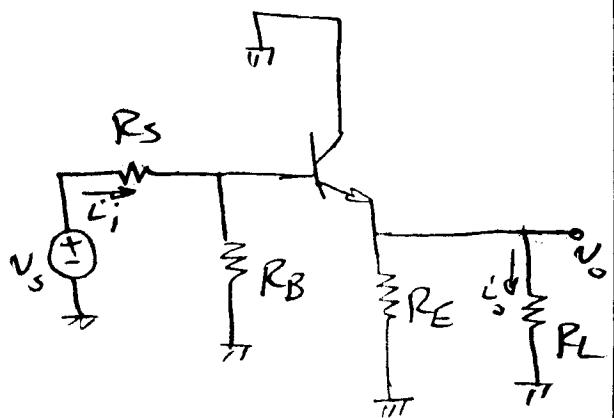- ALL capacitors are s.c.
- Reduce DC sources using π -model





$$\text{let } R_L = R_E \parallel R_L \\ = 15\text{k} \parallel 2\text{k} = 1.765 \text{ k}\Omega.$$

To find R_i

$$R_i = R_B \parallel [r_\pi + (1+B)R_L] \\ = 100\text{k} \parallel [18.45\text{k} + (121) * 1.765\text{k}] \\ = 100\text{k} \parallel (232.015\text{k}) = 69.88 \text{ k}\Omega$$

To find R_o
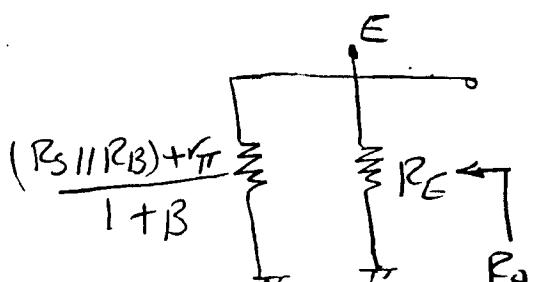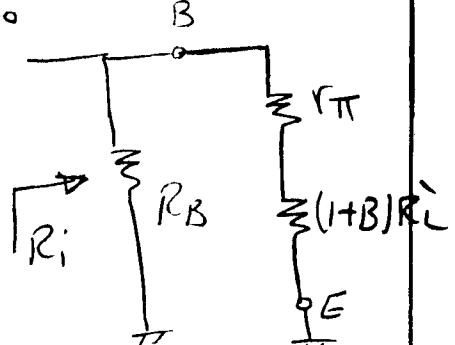
$$R_o = R_E \parallel \left[\frac{(R_s \parallel R_B) + r_\pi}{1+B} \right] \\ = 15\text{k} \parallel \left[\frac{(2\text{k} \parallel 100\text{k}) + 18.45\text{k}}{121} \right] \\ = 15\text{k} \parallel 168.68 = 166.8 \Omega$$



To find $A_v = \frac{V_o}{V_s}$

$$V_b = V_s \frac{R_i}{R_s + R_i}$$

$$V_o = V_b \frac{(1+B)R_L}{r_\pi + (1+B)R_L}$$


$$\therefore V_o = V_s \frac{R_i}{R_s + R_i} * \frac{(1+B)R_L}{r_\pi + (1+B)R_L}$$

$$\therefore A_v = \frac{V_o}{V_s} = \frac{R_i}{R_s + R_i} * \frac{(1+B)R_L}{r_\pi + (1+B)R_L}$$

$$= \frac{69.88k}{2k + 69.88k} * \frac{121 * 1.765k}{18.45k + 121 * 1.765k}$$

$$= 0.9722 * 0.9205$$

$$= 0.895 \text{ V/V}$$

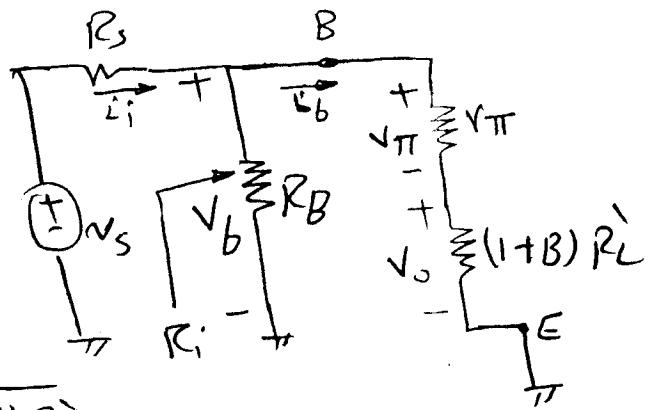

To find $A_L = \frac{I_o}{I_i}$

$$I_o = I_e \frac{R_E}{R_E + R_L}$$

$$I_e = (1+\beta)I_b$$

$$I_b = I_i \frac{R_B}{R_B + r_\pi + (1+\beta)R_L}$$

$$\therefore I_o = (1+\beta)I_i \cdot \frac{R_E}{R_B + r_\pi + (1+\beta)R_L} \cdot \frac{R_E}{R_E + R_L}$$

$$\therefore A_L = \frac{I_o}{I_i} = (1+\beta) \frac{R_E}{R_B + r_\pi + (1+\beta)R_L} * \frac{R_E}{R_E + R_L}$$

$$= (1+120) \frac{100k}{100k + 18.45k + 121 * 1.765k} * \frac{15k}{15k + 2k}$$

$$= 121 * 0.3012 * 0.8824$$

$$= 32.17 \text{ A/A}$$

