



Answer the following questions:

Q1: (a) Assuming that the diodes in the circuit of Fig. (1) are ideal, find the values of the labeled voltage, V , and current, I .

(b) Analyze the circuit of Fig. (2), to determine the voltages at all nodes and the currents through all branches. Assume that the transistor $\beta = 100$.

Q2: (a) Determine and sketch the output waveform for the network of Fig. (3).

(b) The Si Darlington transistor pair of Fig.(4) has $\beta_1 = \beta_2 = 50$. Let $R_2 \rightarrow \infty$ Find the values of R_1 , and V_{CE1} needed to bias the circuit so that $V_{CE2} = 6V$.

Q3: The 6.8V zener diode in the circuit of Fig. (5) is specified to have $V_z = 6.8V$ at $I_z = 5mA$, $r_z = 20\Omega$, and $I_{zk} = 0.2 mA$. The supply voltage V^+ is nominally 10V but can vary by $\pm 1 V$.

- Find V_0 with no load and with V^+ at its nominal value.
- Find the change in V_0 resulting from the $\pm 1 V$ change in V^+ .
- Find the change in V_0 when $R_L = 2 k\Omega$.
- What is the minimum value of R_L for which the diode still operates in the breakdown region?

Q4: For the amplifier shown in Fig.(6), let $V_{CC} = 12V$, $R_1 = 22 k\Omega$, $R_2 = 6.8 k\Omega$, $R_E = 560 \Omega$, and $R_C = 1 k\Omega$. The transistor has $\beta = 100$. Calculate the dc bias current I_E . If the amplifier operates between a source for which $R_{sig} = 600 \Omega$ and a load of $2 k\Omega$, replace the transistor with its hybrid- π model, and find the values of R_{in} , R_o , and the voltage gain v_o/v_{sig} .

Q5: The transistor in the circuit shown in fig. (7) is biased to operate in the active mode. Replace the transistor with small-signal equivalent circuit T –model and then find R_{in} , the voltage gain (v_o/v_{sig}), the current gain (i_o/i_i), and the output resistance R_{out} . Assuming that $\beta=100$.

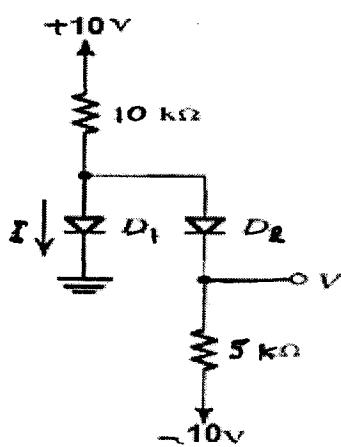


Fig.(1)

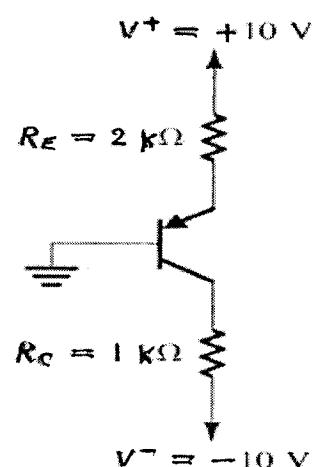


Fig.(2)

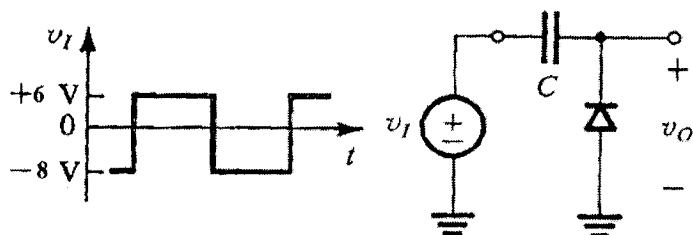


Fig.(3)

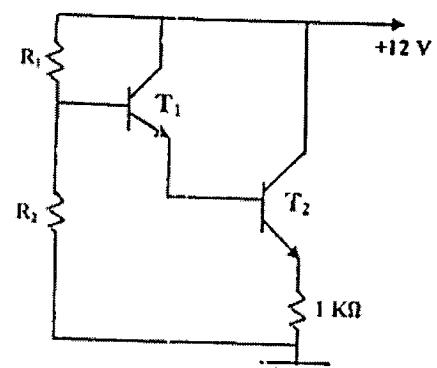


Fig.(4)

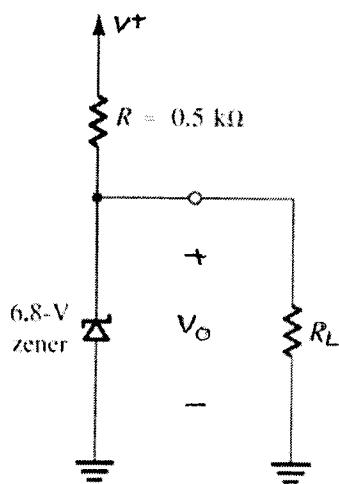


Fig.(5)

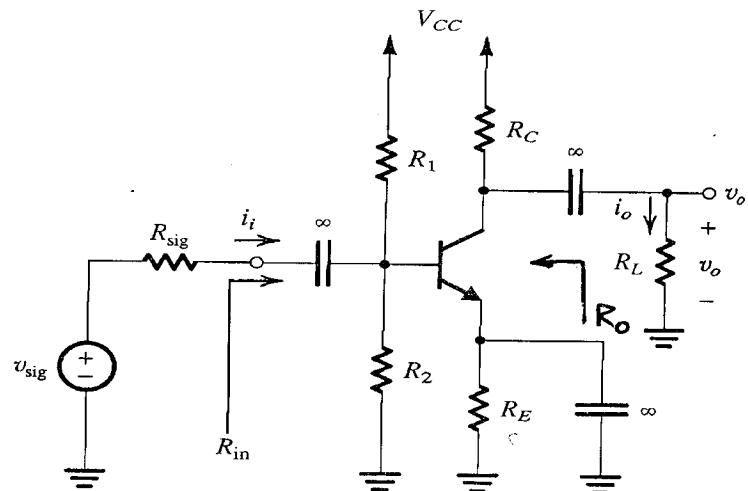


Fig.(6)

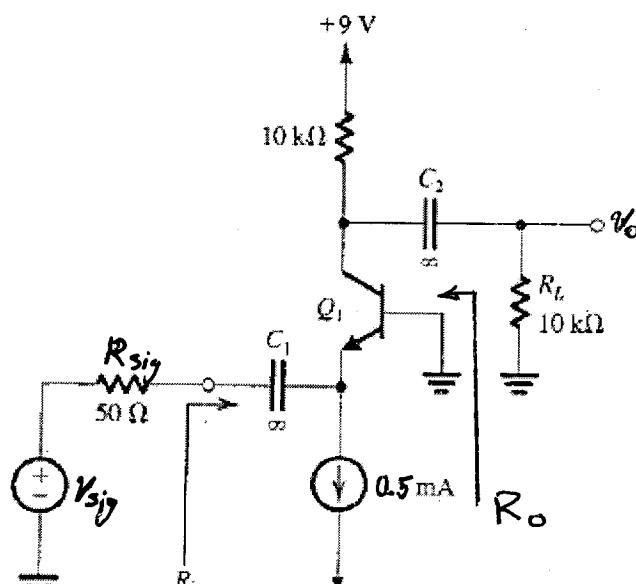


Fig.(7)

BEST WISHES
Hossam Labib

Q1 (12 points)

Q1(a) (6 points)

Assuming that the diodes in the circuit of Fig.(2) are ideal, find the values of the labeled voltage, V , and current, I .

Solution


$$\text{let } I = I_{D_1}$$

let D_1 and D_2 are on

For D_1 on $\Rightarrow V_1 = 0 \Rightarrow V = 0$ for D_2 on

$$\therefore I_1 = \frac{10 - V_1}{10k} = \frac{10 - 0}{10k} = 1 \text{ mA}$$
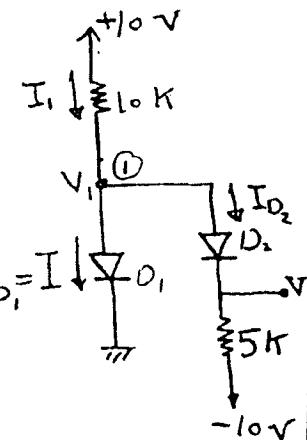
$$I_{D_2} = \frac{V_1 - (-10)}{5k} = \frac{0 + 10}{5k} = 2 \text{ mA}$$



$$\text{From Node ①} \Rightarrow I_1 = I_{D_1} + I_{D_2}$$

$$I_{D_1} = I_1 - I_{D_2} = 1 \text{ mA} - 2 \text{ mA} = -1 \text{ mA}$$

$\therefore I_{D_1}$ -ve \therefore NOT True

i.e. The assumption NOT correct

Let D_1 off and D_2 on

$$\text{For } D_1 \text{ off} \Rightarrow I_{D_1} = 0 \therefore I_1 = I_{D_2}$$

$$\text{For } D_2 \text{ on} \Rightarrow I_1 = \frac{10 - (-10)}{10k + 5k} = \frac{20}{15k} = 1.333 \text{ mA}$$

$$V = I_{D_2} * 5k - 10 = 1.333 * 5 - 10 = -3.335 \text{ V}$$

$$\text{For } V = -3.335 \text{ V} ; \therefore V_1 = V = V_{p1} = -3.335 ; V_{n1} = 0$$

i.e. $V_{p1} < V_{n1} \Rightarrow D_1 \text{ off}$

\therefore The assumption is True (D_1 off & D_2 on)

$$\therefore V = -3.335 \text{ V and } I = I_{D_1} = 0 \text{ A}$$

Analyze the circuit of Fig. (2), to determine the voltages at all nodes and the currents through all branches. Assume that the transistor $\beta = 100$.

Solution:

let Transistor operate in Active Region

Loop (I)

$$-V^+ + I_E R_E + V_{EB} = 0$$

$$I_E = \frac{V^+ - V_{EB}}{R_E} = \frac{10 - 0.7}{2k} = 4.65 \text{ mA}$$

$$I_C = \alpha I_E = \frac{\beta I_E}{1 + \beta} = \frac{100}{1 + 100} * 4.65 \text{ mA} = 4.604 \text{ mA}$$


$$\therefore I_B = I_E - I_C = 4.65 - 4.604 = 0.046 \text{ mA}$$

$$V_B = 0$$


$$\therefore V_{EB} = V_E - V_B \Rightarrow V_E = V_{EB} + V_B = 0.7 \text{ V}$$

$$V_C = I_C R_C + V^-$$
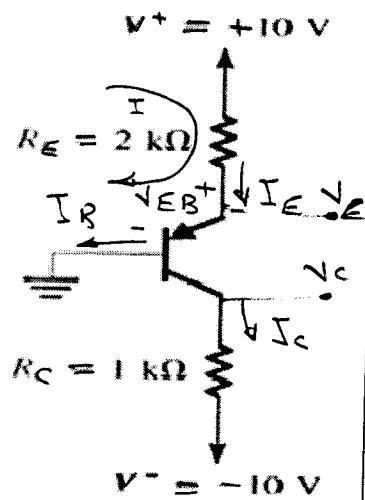
$$= 4.604 \text{ mA} * 1k - 10 = -5.396 \text{ V}$$



$V_E > V_B \Rightarrow EBJ$ Forward

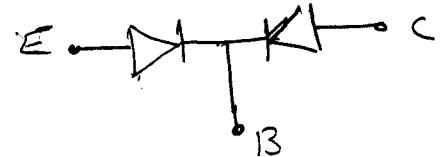

$V_C < V_B \Rightarrow CBJ$ Reverse

\therefore Transistor in ACTIVE region

\therefore assumption is True


Q2: (12 points)

Q2:(a) Determine and sketch the output waveform for the network shown

$$V_C = 8 \text{ V}$$

$$V_o = V_i + V_C \quad \text{i.e. } V_o = V_i + \text{shifted by -ve half cycle}$$

$$= V_i + 8$$

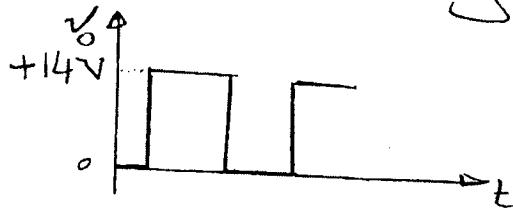

Q2:(b)

The Si Darlington Transistor pair shown has $B_1 = B_2 = 50$. Let $R_2 \rightarrow \infty$.

Find the values of R_1 , and V_{CE_1} needed to bias the circuit so that $V_{CE_2} = 6 \text{ V}$

Solution

For $R_2 \rightarrow \infty \Rightarrow I_2 = 0$

$$\therefore I_1 = I_{B1}$$

$$\therefore I_{E1} = I_{B2}$$

$$\therefore V_{CE_2} = 6 = V_{C_2} - V_{E_2}$$

$$\therefore V_{E_2} = V_{C_2} - 6$$

$$V_{C_2} = V_{C_1} = V_{CC} = 12 \text{ V}$$




$$\therefore V_{E_2} = 12 - 6 = 6 \text{ V}$$

$$\therefore I_{E2} = \frac{V_{E2}}{R_E} = \frac{6}{1K} = 6 \text{ mA}$$

$$\therefore I_{B2} = I_{E1} = \frac{I_{E2}}{1+B_2} = \frac{6 \text{ mA}}{1+50} = 0.118 \text{ mA}$$

$$I_{B1} = \frac{I_{E1}}{1+B_1} = \frac{0.118 \text{ mA}}{1+50} = 2.314 \text{ mA}$$

(3)

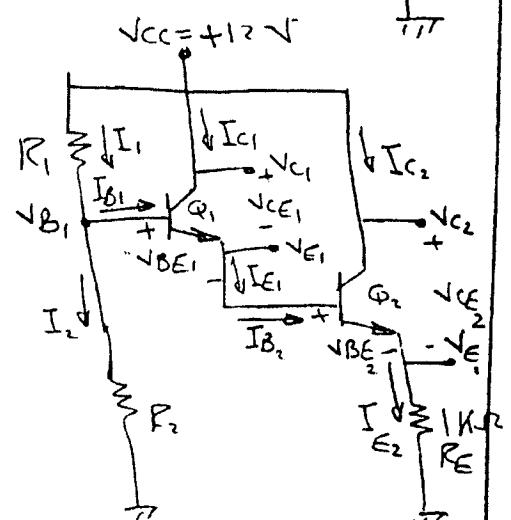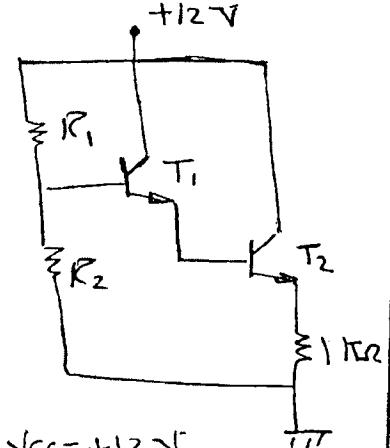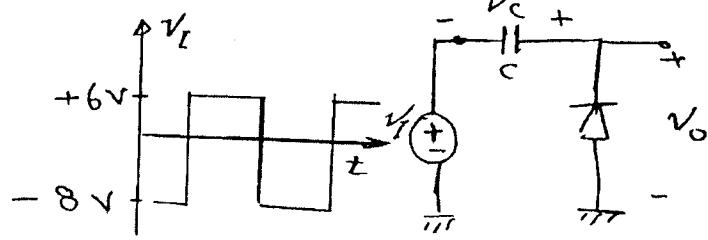


Q2: (12 points)

Q2:(a) Determine and sketch the output waveform for the network shown

$$V_C = 8 \text{ V}$$

$$V_o = V_i + V_C \quad \text{i.e. } V_o = V_i + \text{shift Td by -ve half cycle}$$

$$= V_i + 8$$

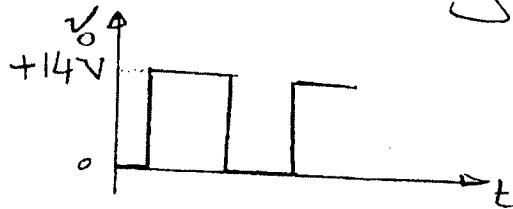

Q2:(b)

The Si Darlington Transistor pair shown has $B_1 = B_2 = 50$. Let $R_2 \rightarrow \infty$.

Find the values of R_1 , and V_{CE_1} needed

To bias the circuit so that $V_{CE_2} = 6 \text{ V}$

Solution

For $R_2 \rightarrow \infty \Rightarrow I_2 = 0$

$$\therefore I_1 = I_{B_1}$$

$$\therefore I_{E_1} = I_{B_2}$$

$$\therefore V_{CE_2} = 6 = V_{C_2} - V_{E_2}$$

$$\therefore V_{E_2} = V_{C_2} - 6$$



$$V_{C_2} = V_{C_1} = V_{CC} = 12 \text{ V}$$

$$\therefore V_{E_2} = 12 - 6 = 6 \text{ V}$$

$$\therefore I_{E_2} = \frac{V_{E_2}}{R_E} = \frac{6}{1K} = 6 \text{ mA}$$

$$\therefore I_{B_2} = I_{E_1} = \frac{I_{E_2}}{1+B_2} = \frac{6 \text{ mA}}{1+50} = 0.118 \text{ mA}$$
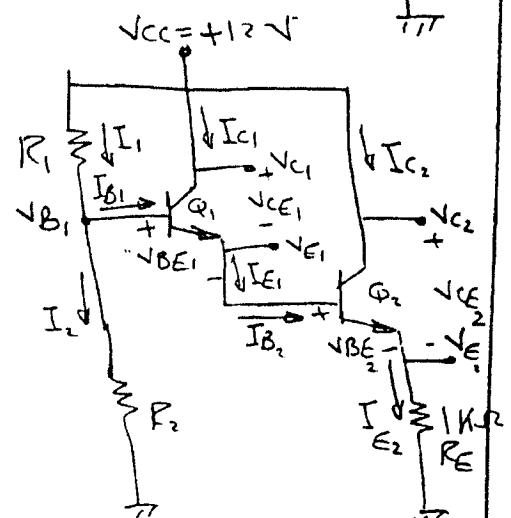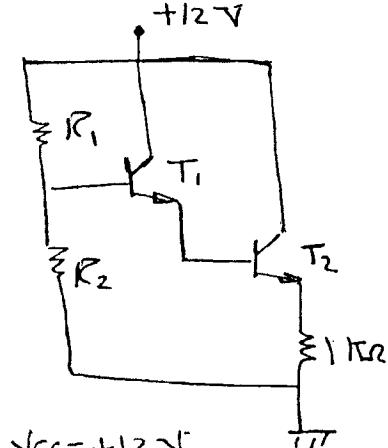
$$I_{B_1} = \frac{I_{E_1}}{1+B_1} = \frac{0.118 \text{ mA}}{1+50} = 2.314 \text{ mA}$$



(3)

Q2: (b) (cont.)

$$R_1 = \frac{V_{CC} - V_{B1}}{I_1}$$

$$\begin{aligned}V_{B1} &= V_{BE1} + V_{BE2} + V_{E1} \\&= 0.7 + 0.7 + 6 = 7.4 \text{ V}\end{aligned}$$

$$\therefore R_1 = \frac{12 - 7.4}{2.314 \text{ mA}} = 1.99 \text{ k}\Omega$$

$$\begin{aligned}\therefore V_{E1} &= V_{BE2} + V_{E2} \\&= 0.7 + 6 = 6.7 \text{ V}\end{aligned}$$

$$\begin{aligned}\therefore V_{CE1} &= V_C - V_{E1} \\&= 12 - 6.7 = 5.3 \text{ V}\end{aligned}$$

Q3:- (12 points)

The 6.8V Zener diode in the circuit shown is specified to have $V_Z = 6.8V$ at $I_Z = 5mA$, $r_Z = 2\Omega$, and $I_{ZK} = 0.1mA$. The supply voltage V^+ is nominally 10V but can vary by $\pm 1V$.

(a) Find V_o with no load and with V^+ at its nominal value.

$$\therefore V_Z = V_{Z_0} + r_Z I_Z$$

$$6.8 = V_{Z_0} + 2 \times 5 \times 10^{-3}$$

$$\therefore V_{Z_0} = 6.8 - 0.1 = 6.7V$$

With no load i.e. $R_L = \infty$

$$I = I_Z = \frac{V^+ - V_{Z_0}}{R + r_Z}$$

$$= \frac{10 - 6.7}{0.5k + 2} = 6.35mA$$

$$\therefore V_o = V_{Z_0} + I_Z r_Z$$

$$= 6.7 + 6.35 \times 2 = 6.83V$$

(b) Find the change in V_o resulting from the $\pm 1V$ change in V^+ .
The change in V_o can be found from

$$\Delta V_o = \Delta V^+ \frac{r_Z}{R + r_Z}$$

$$= \pm 1 \times \frac{2}{0.5k + 2} = \pm 38.5mV$$




(c) Find the change in V_o when $R_L = 2k\Omega$

If $R_L = 2k\Omega$ is connected

$$\therefore I_L \leq \frac{V_Z}{R_L} = \frac{6.8}{2k} = 3.4mA$$

$$I = \frac{10 - 6.8}{0.5k} = 6.4mA$$

$$\therefore I = I_Z + I_L \Rightarrow |I_Z|_{\text{loaded}} = I - I_L = \\ |I_Z|_{\text{loaded}} = 6.4mA - 3.4mA = 3mA$$

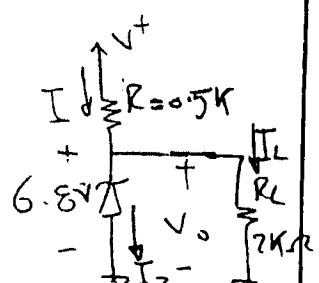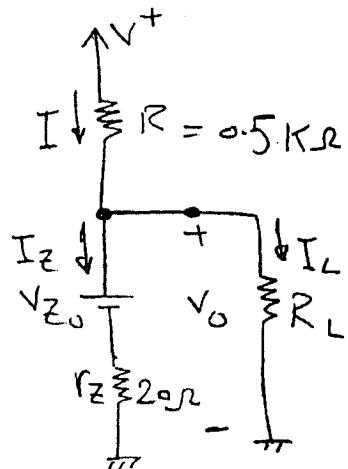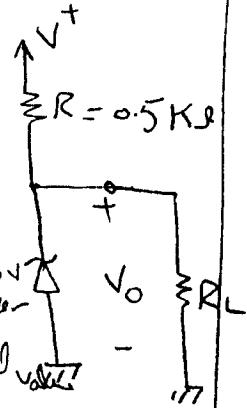

Q3: (cont.)

$$\text{change in Zener current } \Delta I_Z = I_Z|_{\text{Load}} - I_Z|_{\text{No-Load}}$$

$$\Delta I_Z = 3 - 6.35 = -3.4 \text{ mA}$$

$$\therefore \text{change in } V_o \Rightarrow \Delta V_o = \Delta I_Z V_Z$$

$$\Delta V_o = -3.4 \text{ mA} \times 20 = -68 \text{ mV}$$

(d) What is the min. value of R_L for which the diode still operates in the breakdown region?

For the Zener at edge of the breakdown region Then
 $I_Z = I_{ZK} = 0.2 \text{ mA}$ and $V_{Zo} \approx V_{ZK} \approx 6.7 \text{ V}$

\therefore AT This point the lowest current supplied through R is $I = \frac{V_o - V_{ZK}}{R}$

$$= \frac{9 - 6.7}{0.5 \text{ k}\Omega} = 4.6 \text{ mA}$$

$$\therefore I_L = I - I_Z = 4.6 - 0.2 = 4.4 \text{ mA}$$

$$R_L|_{\min} = \frac{V_o}{I_L} \approx \frac{V_Z}{I_L}$$

$$= \frac{6.7}{4.4 \text{ mA}} = 1.5 \text{ k}\Omega$$

(Q4) (12 Points)

For the amplifier shown in Fig.(3), let $V_{CC} = 12V$, $R_1 = 22\text{ k}\Omega$, $R_2 = 6.8\text{ k}\Omega$, $R_E = 560\Omega$, and $R_C = 1\text{ k}\Omega$. The transistor has $\beta = 100$. Calculate the dc bias current I_E . If the amplifier operates between a source for which $R_{sig} = 600\Omega$ and a load of $2\text{ k}\Omega$, replace the transistor with its hybrid- π model, and find the values of R_{in} , R_o , and the voltage gain v_o/v_{sig} .

Solution

DC Analysis

- ALL capacitor are o.c

- Reduce AC sources

$$R_{Th} = R_1 \parallel R_2 = 22\text{ k} \parallel 6.8\text{ k}$$

$$R_{Th} = 5.19\text{ k}\Omega$$

$$V_{Th} = V_{CC} \frac{R_2}{R_1 + R_2}$$

$$V_{Th} = 12 \frac{6.8\text{ k}}{22\text{ k} + 6.8\text{ k}} = 2.833\text{ V}$$

Loop (I)

$$-V_{Th} + I_B R_{Th} + V_{BE} + I_E R_E = 0 \quad \therefore I_E = (1+B) I_B$$

$$\frac{I_E}{1+B} R_{Th} + I_E R_E = V_{Th} - V_{BE}$$

$$I_E = \frac{V_{Th} - V_{BE}}{R_E + \frac{R_{Th}}{1+B}} = \frac{2.833 - 0.7}{560 + \frac{5.19\text{k}}{101}} = 3.489\text{ mA} \quad \textcircled{5}$$

$$I_C = \alpha I_E = \frac{\beta}{1+B} I_E = \frac{100}{101} * 3.489\text{ mA} = 3.454\text{ mA}$$




$$g_m = \frac{I_C}{V_T} = \frac{3.454\text{ mA}}{25\text{ mV}} = 0.138\text{ A/V} \xrightarrow{-0.5} \textcircled{6}$$

$$r_{pi} = \frac{\beta}{g_m} = \frac{100}{0.138} = 724.64\Omega \xrightarrow{-0.5} R_{sig}$$

AC Analysis

- ALL capacitor are s.c


- Reduce DC sources

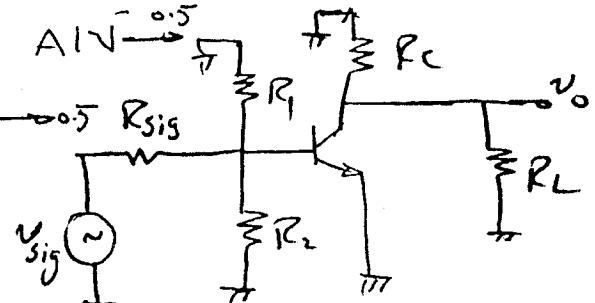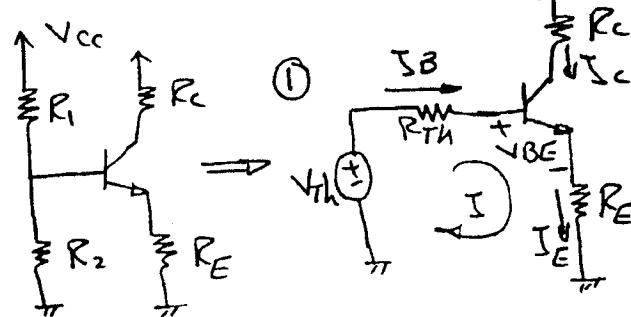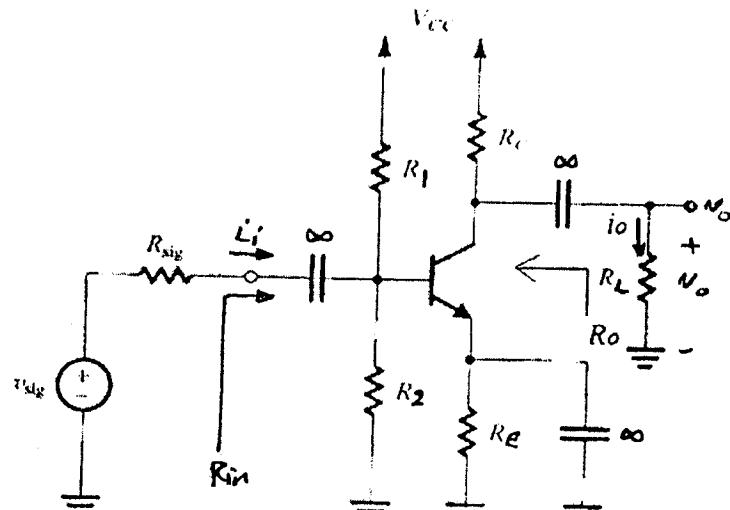

(7)

Q4 (cont.)

Using π -model

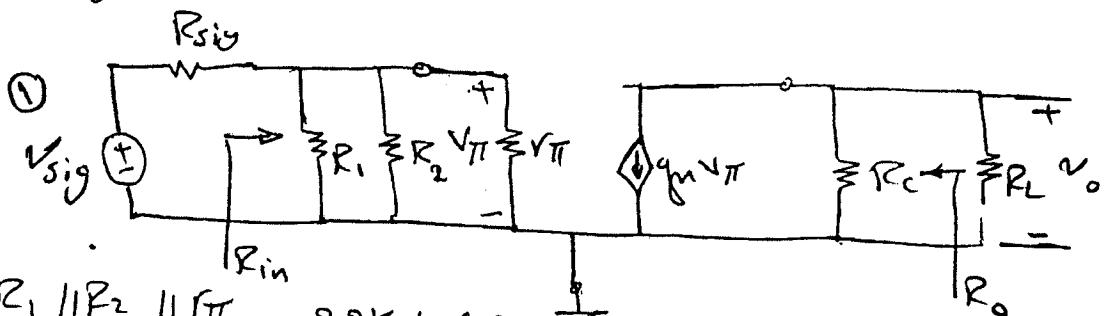

$$R_{in} = R_1 \parallel R_2 \parallel V_{\pi} = 22k \parallel 6.8k \parallel 724.61 \\ = 635.93 \approx 636 \Omega$$

$$R_0 = R_c = 1 \text{ k}\Omega.$$

To find $\frac{V_o}{V_{sig}}$:-

$$V_o = -g_m \frac{V_o}{R_{in}} (R_c \parallel R_L)$$

$$V_{\pi} = V_{sig} \frac{R_{in}}{R_{in} + R_{sig}}$$

$$V_o = -g_m V_{sig} \frac{R_{in}}{R_{in} + R_{sig}} (R_c \parallel R_L) \rightarrow ②$$

$$\frac{V_o}{V_{sig}} = -g_m \frac{R_{in}}{R_{in} + R_{sig}} (R_c \parallel R_L)$$

$$= -0.138 \frac{636}{636 + 600} (1k \parallel 2k)$$

$$= -0.138 * 0.515 * 666.667 = -47.34 \text{ V/V} \rightarrow ①$$

⑧

Q5: (12 points)

The transistor in the circuit shown is biased to operate in the Active mode. Replace the transistor with small-signal equivalent circuit T-mode and then find R_{in} , the voltage gain (V_o/V_{sig}), the current gain (I_o/I_i) and the o/p resistance R_{out} . Assuming that $\beta = 100$.

Solution

DC Analysis

- Reduce AC sources

- All capacitors are o.c.

$$I_E = I = 0.5 \text{ mA}$$

$$I_C = \alpha I_E = \frac{\beta}{1+\beta} I_E = \frac{10}{101} * 0.5 \text{ mA} \\ = 0.495 \text{ mA} = 0.495 \text{ mA}$$



$$g_m = \frac{I_C}{V_T} = \frac{0.495 \text{ mA}}{25 \text{ m}} = 19.8 \text{ mA/V}$$

$$r_e = \frac{V_T}{I_E} = \frac{25 \text{ m}}{0.5 \text{ mA}} = 50 \Omega$$

AC Analysis

- Reduce DC sources

- All capacitors are s.c.

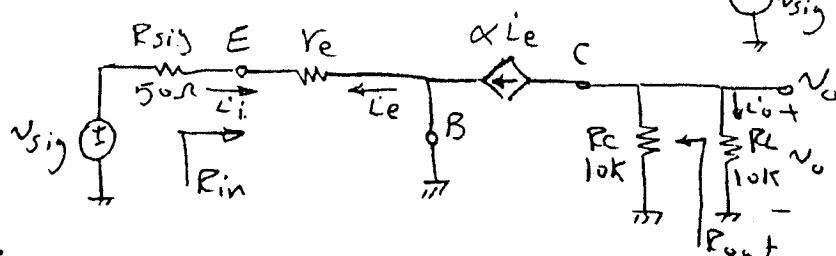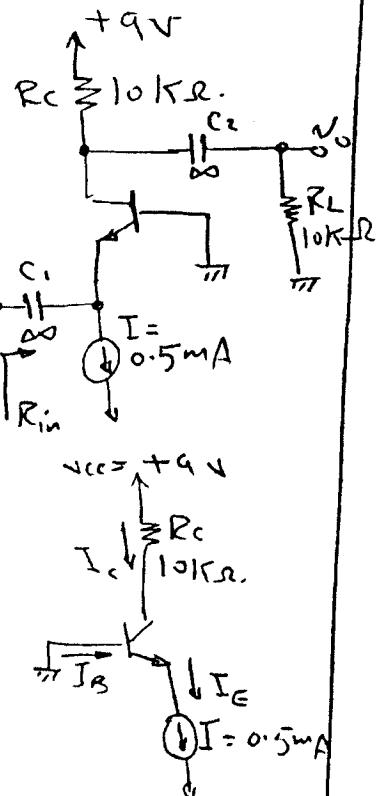

$$R_{in} = r_e = 50 \Omega$$

$$\left. R_{out} \right|_{V_{sig}=0} = R_C = 10 \text{ k}\Omega$$

(9)

Q5 : (Cont.)

$$\text{To find } A_v = \frac{V_o}{V_{sig}}$$

$$V_o = -\alpha L_e (R_C \parallel R_L)$$

$$L_e = -\frac{V_{sig}}{R_{sig} + r_e}$$

$$V_o = +\alpha \frac{V_{sig}}{R_{sig} + r_e} (R_C \parallel R_L)$$

$$\begin{aligned} \frac{V_o}{V_{sig}} &= \alpha \frac{(R_C \parallel R_L)}{R_{sig} + r_e} \\ &= (0.99) \frac{(10k \parallel 10k)}{50 + 50} \end{aligned}$$

$$= (0.99) \frac{5k}{100} = 49.5 \text{ V/V}$$

$$\text{To find } A_L = \frac{L_o}{L_i}$$

$$L_o = -\alpha L_e \frac{R_C}{R_C + R_L}$$

$$L_e = -L_i$$

$$L_o = +\alpha L_i \frac{R_C}{R_C + R_L}$$

$$\begin{aligned} A_L &= \frac{L_o}{L_i} = \alpha \frac{R_C}{R_C + R_L} \\ &= (0.99) \frac{10k}{10k + 10k} = 0.495 \text{ A/A} \end{aligned}$$
