

Answer the following questions:

Q1:(a) The JFET in the circuit of fig.(1) has $V_p = -3V$, $I_{DSS} = 9mA$ and $\lambda = 0$. Find the values of all resistors so that $V_G = 5V$, $I_D = 4 mA$ and $V_D = 11V$. Design for 0.05 mA in the voltage divider.

(b) The basic op amp in fig.(2) is ideal. Find V_o and determine what mathematical operation is performed by the amplifier circuit.



Q2: The MOSFET amplifier circuit of fig.(3) has $K=1 \text{ mA/V}^2$ and $V_t = 2V$. Also, $V_{GS} = 5V$, $R_D = 1.33 \text{ K}\Omega$ and $V_{DD} = 20V$. Find the dc current I_D , the dc voltage V_D and g_m . If $v_{gs} = 0.5 \sin \omega t V$, find v_d and what are the minimum and maximum values of v_D .

Q3: Consider the common gate amplifier shown in fig.(4) with transistor parameter $g_m = 2 \text{ mA/V}$. If $I = 1 \text{ mA}$, $V_{DD} = V_{SS} = 5V$, $R_G = 1 \text{ M}\Omega$, $R_D = R_L = 3k\Omega$ using T-model determine the small signal voltage gain $A_v = (v_o/v_i)$, the input resistance R_{in} , and the output resistance R_{out} .

Q4: The circuit in Fig. (5) utilizes an ideal op amp.

- (a) Find I_1 , I_2 , I_3 , I_L , and V_x .
- (b) If V_o is not to be lower than $-13V$, find the maximum allowed value for R_L .

Q5: Find the voltage gain v_o/v_i and the differential input resistance of the amplifier shown in fig. (6). Assuming $\beta = 100$.

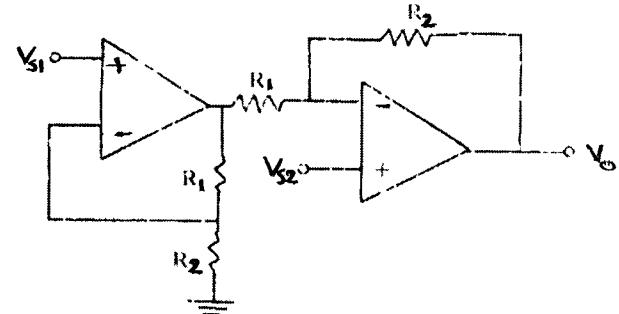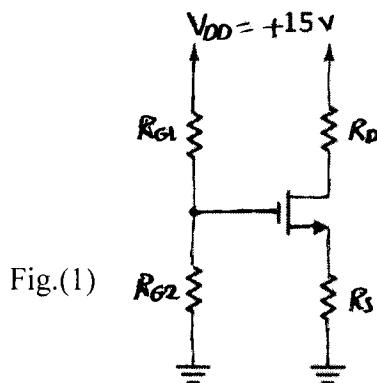

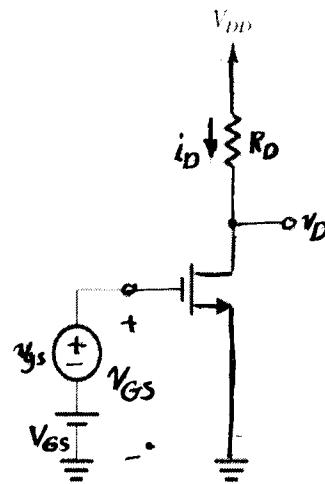


Fig.(3)

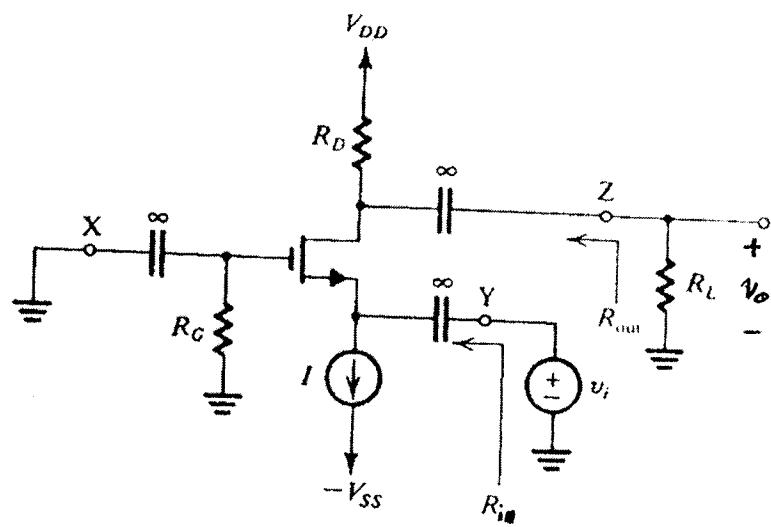


Fig.(4)

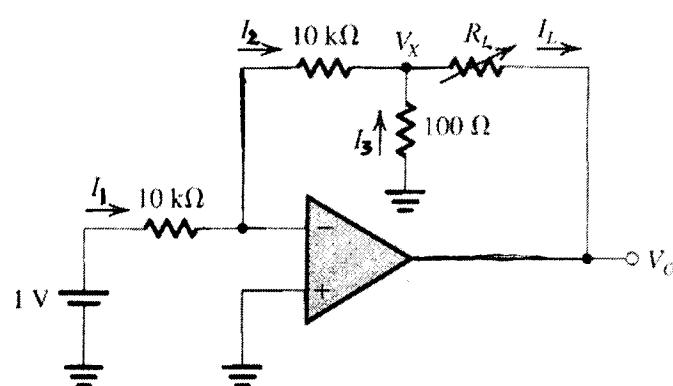


Fig.(5)

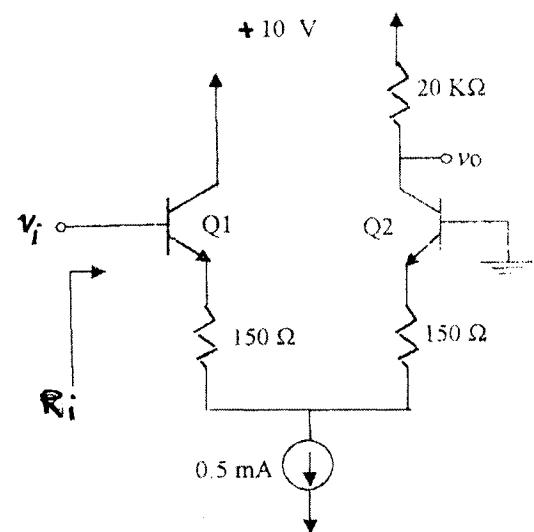


Fig.(6)

BEST WISHES

Hossam Labib

Q1(a) The JFET in the circuit shown has $V_p = -3 \text{ V}$, $I_{DSS} = 9 \text{ mA}$ and $\lambda = 0$. Find the values of all resistors so that $V_G = 5 \text{ V}$, $I_D = 4 \text{ mA}$ and $V_O = 11 \text{ V}$, Design for 0.05 mA in the voltage divider.

Solution

$$\because I_G = 0 \quad \& \quad V_G = 5 \text{ V}$$

$$R_{G1} = \frac{15 - 5}{0.05 \text{ mA}} = 200 \text{ k}\Omega$$

$$R_{G2} = \frac{5 - 0}{0.05 \text{ mA}} = 100 \text{ k}\Omega$$

$$R_D = \frac{15 - 11}{4 \text{ mA}} = 1 \text{ k}\Omega$$

$$V_{DS\text{sat}} = V_{GS} - V_p = V_G - V_S - V_p = 5 - V_S + 3 \\ = 8 - V_S$$

$$V_{DS} = V_O - V_S = 11 - V_S$$

$\therefore V_{DS} > V_{DS\text{sat}}$ \therefore Tr. In saturation region

$$\therefore I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p} \right)^2$$

$$4 \text{ mA} = 9 \text{ mA} \left(1 + \frac{V_{GS}}{3} \right)^2 \Rightarrow \frac{4}{9} = \left(1 + \frac{V_{GS}}{3} \right)^2$$

$$\pm \frac{2}{3} = \left(1 + \frac{V_{GS}}{3} \right) \xrightarrow{\times 3} \pm 2 = 3 + V_{GS}$$



$$V_{GS} = \pm 2 - 3 \Rightarrow V_{GS} = -1 \quad \& \quad V_{GS} = -5$$

for $V_{GS} = -5 \text{ V} < V_p \Rightarrow$ Neglected


$$\text{Then } V_{GS} = -1 \text{ V}$$

$$\therefore V_{GS} = V_G - V_S \Rightarrow V_S = V_G - V_{GS} = 5 + 1 = 6 \text{ V}$$
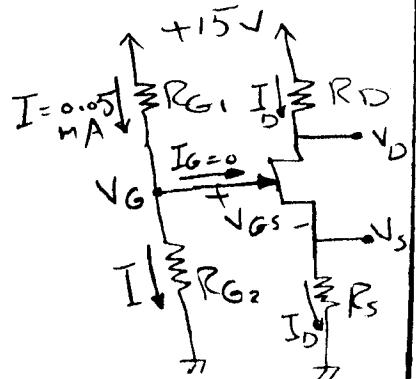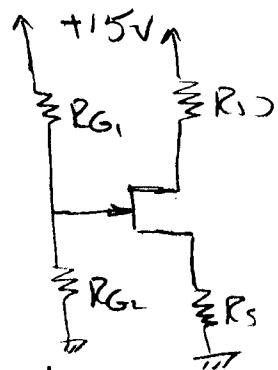
$$\therefore R_S = \frac{V_S}{I_D} = \frac{6}{4 \text{ mA}} = 1.5 \text{ k}\Omega$$



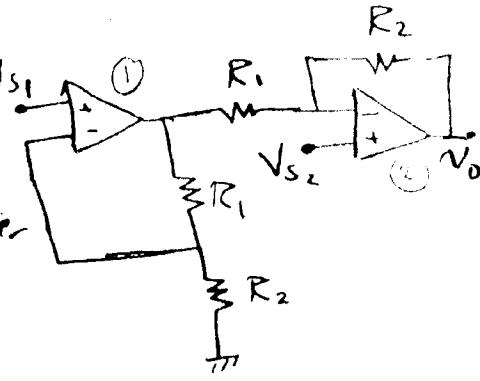Q1(b) The basic op Amp. shown is ideal. V_{S1} and V_{S2} are the inputs. Find V_o and determine what mathematical operation is performed by the amplifier circuit.





Solution

For op Amp ①

$$V_{o1} = \left(1 + \frac{R_1}{R_2}\right) V_{S1}$$

For op Amp ②
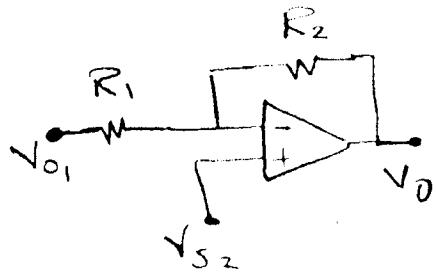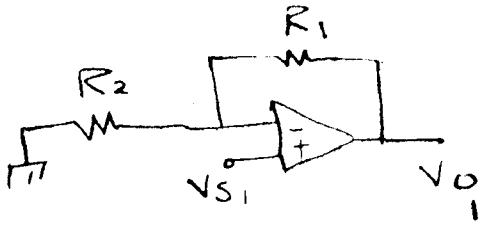
$$V_o = \left(1 + \frac{R_2}{R_1}\right) V_{S2} + \left(-\frac{R_2}{R_1}\right) V_{o1}$$



$$V_o = \left(1 + \frac{R_2}{R_1}\right) V_{S2} - \left(\frac{R_2}{R_1}\right) \left(1 + \frac{R_1}{R_2}\right) V_{S1}$$

$$= \left(1 + \frac{R_2}{R_1}\right) V_{S2} - \left(\frac{R_2}{R_1} + 1\right) V_{S1}$$

$$= \left(1 + \frac{R_2}{R_1}\right) (V_{S2} - V_{S1})$$

The operation is difference (subtractor) op Amp.

(Q2) The MOSFET of amplifier circuit shown has

$$K = 1 \text{ mA/V}^2 \text{ and } V_t = 2 \text{ V ALSO,}$$

$$V_{GS} = 5 \text{ V}, R_D = 1.33 \text{ k}\Omega \text{ and } V_{DD} = 20 \text{ V}$$

Find The dc current I_D , The dc voltage

$$V_O \text{ and } g_m. \text{ If } V_{GS} = 0.5 \sin \omega t$$

find V_d and what are The min. and max. value of V_D .

Solution

DC analysis $\Rightarrow V_{GS} = 0$

\therefore Tr. in saturation region (Amplifier..)

$$I_D = K(V_{GS} - V_t)^2 ; \lambda = 0$$

$$V_S = 0 \text{ & } V_G = 5 \text{ V} \Rightarrow V_{GS} = 5 \text{ V}$$

$$\therefore I_D = 1 \text{ mA} (5 - 2)^2 = 9 \text{ mA}$$

$$V_O = V_{DD} - I_D R_D = 20 - 9 * 1.33 = 8.03 \text{ V}$$

$$g_m = 2K(V_{GS} - V_t) = 2 * 1(5 - 2) = 6 \text{ mA/V}$$

AC Analysis

$$V_{GS} = 0 \text{ & } V_{DD} = 0$$

$$r_o = \infty \quad V_d = -I_D R_D$$

$$V_o = V_d = -g_m V_{GS} R_D$$

$$V_d = -6 * 1.33 (0.5 \sin \omega t) \\ = -3.99 \sin \omega t \text{ V}$$

Note

$$A_v = \frac{V_o}{V_{GS}} = -g_m R_D = -6 * 1.33 = -7.98 \frac{\text{V}}{\text{V}}$$






$$V_d = V_o \Rightarrow \frac{V_d}{V_{GS}} = -7.98 \Rightarrow V_d = -7.98 V_{GS} = -7.98 * 0.5 \sin \omega t$$

$$V_d = -3.99 \sin \omega t \text{ V}$$

$$V_D = V_o + V_d = 8.03 - 3.99 \sin \omega t$$

$$V_D|_{\text{max}} = 8.03 + 3.99 = 12.02 \text{ V}$$

$$\text{&} V_D|_{\text{min}} = 8.03 - 3.99 = 4.04 \text{ V}$$

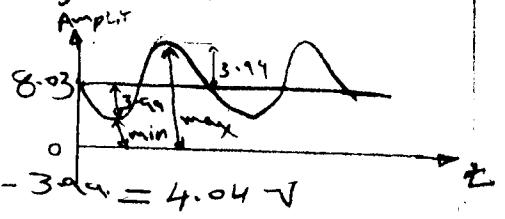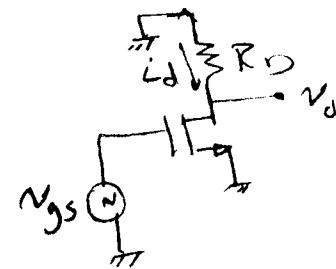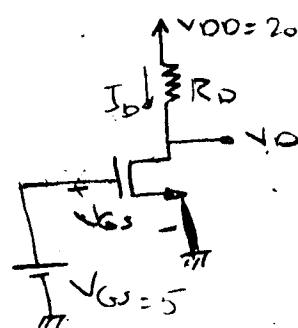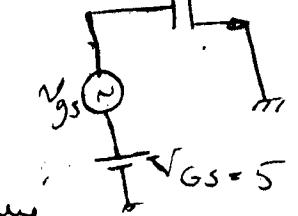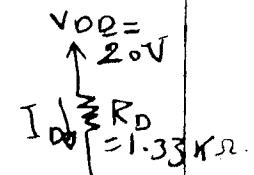


Q3: Consider the common gate amplifier shown in fig. (3) with transistor parameter $g_m = 2 \text{ mA/V}$. If $I = 1 \text{ mA}$, $V_{DD} = V_{SS} = 5 \text{ V}$, $R_G = 1 \text{ M}\Omega$, $R_D = R_L = 3 \text{ k}\Omega$ using T-model determine the small signal voltage gain $A_v = (v_o/v_i)$, the input resistance R_{in} , and the output resistance R_{out} .

Solution

$$g_m = 2 \text{ mA/V}$$

AC Analysis

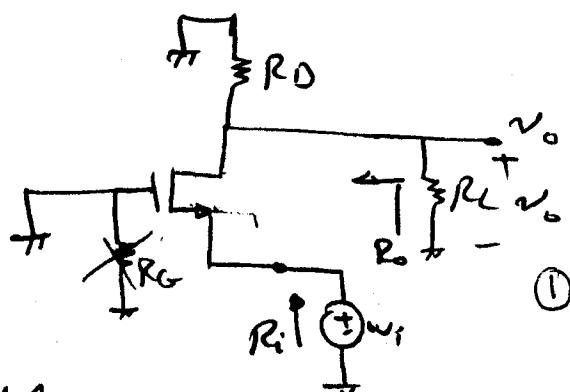

Using - T-model

$$R_i = \frac{1}{g_m} = \frac{1}{2 \times 10^{-3}} = 0.5 \text{ k}\Omega \rightarrow ②$$

$$R_o = R_D = 3 \text{ k}\Omega \rightarrow ①$$



$$v_o = - g_m v_{gs} (R_D \parallel R_L) \rightarrow ①$$

$$v_{gs} = - v_i \rightarrow ①$$

$$v_o = + g_m v_i (R_D \parallel R_L)$$

$$A_v = \frac{v_o}{v_i} = g_m (R_D \parallel R_L) \rightarrow ①$$
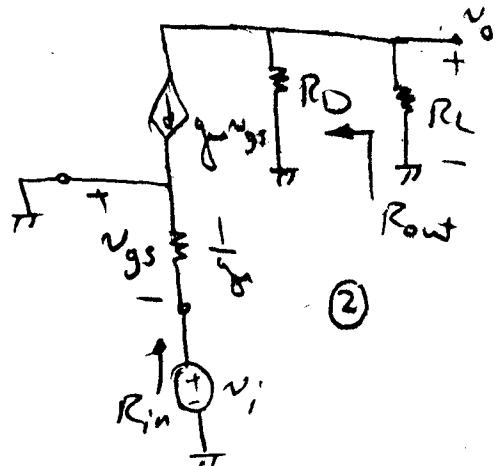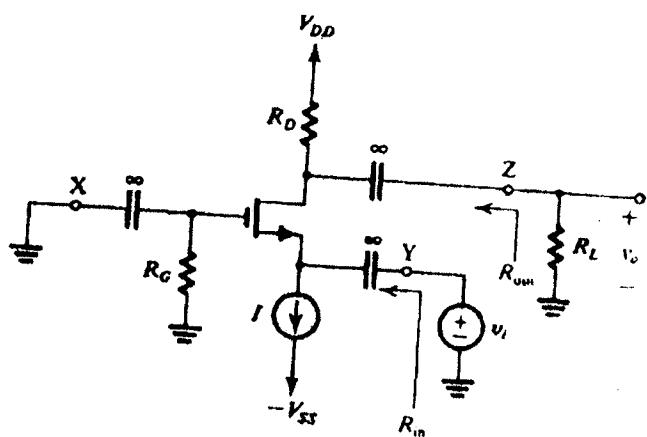
$$= 2 \times 10^{-3} (3 \text{ k} \parallel 3 \text{ k}) = 3 \text{ V/V} \rightarrow ②$$



Q4: The circuit in Fig.(5) utilizes an ideal op amp.

(a) Find I_1 , I_2 , I_3 , I_L , and V_x .

(b) If V_o is not to be lower than -13 V, find the maximum allowed value for R_L .

Solution

(a) for ideal opamp.

$$I_4 = I_5 = 0 \because v^+ = v^- \therefore v^+ = 0 \Rightarrow v = 0 \\ I_1 = \frac{1 - v}{10k} = \frac{1}{10k\Omega} = 0.1 \text{ mA}$$

at node (1)

$$I_1 = I_2 + I_4 \Rightarrow I_1 = I_2 = 0.1 \text{ mA} \\ \therefore I_2 = \frac{v - v_x}{10k\Omega} \Rightarrow 0.1 \text{ mA} = \frac{0 - v_x}{10k\Omega}$$

$$V_x = -0.1 * 10 = -1 \text{ V}$$


$$I_3 = \frac{0 - v_x}{100} = \frac{-1}{100} = 10 \text{ mA}$$

at node (2)

$$I_L = I_2 + I_3 = 0.1 \text{ mA} + 10 \text{ mA} = 10.1 \text{ mA}$$

(b)
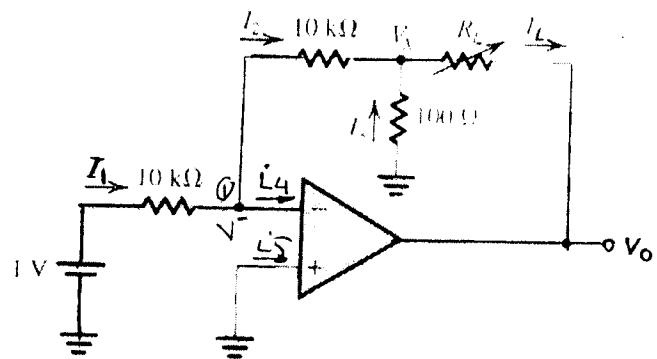
$$R_L = \frac{V_x - V_o}{I_L} = \frac{V_x - V_{o\min}}{I_L} \\ = \frac{-1 + 13}{10.1 \text{ mA}} = \frac{12}{10.1 \text{ mA}} = 1.188 \text{ k}\Omega \approx 1.2 \text{ k}\Omega$$



Q5: Find the voltage gain v_o/v_i and the differential input resistance of the amplifier shown in figure. Assuming $\beta = 100$.

Solution:

DC Analysis

$$I_E = I_{E1} = I_{E2} = \frac{I}{2}$$

$$I_E = \frac{0.5 \text{ mA}}{2} = 0.25 \text{ mA}$$

$$I_C = \alpha I \approx I_E = 0.25 \text{ mA} \quad ; \quad \alpha = 1$$

$$r_e = \frac{V_T}{I_E} = \frac{25 \text{ mV}}{0.25 \text{ mA}} = 100 \Omega$$

$$g_m = \frac{I_C}{V_T} = \frac{0.25 \text{ mA}}{25 \text{ mV}} = 0.01 \text{ A/V}$$

AC Analysis

$$\begin{aligned} R_{id} &= (1 + \beta) (2R_E + 2r_e) \\ &= (1 + 100) (2 \times 150 + 2 \times 100) \\ &= 101 \times 500 = 50.5 \text{ k}\Omega. \end{aligned}$$

$$\begin{aligned} \left| \frac{v_o}{v_i} \right| &= \frac{R_C}{2r_e + 2R_E} \\ &= \frac{20 \text{ k}}{2 \times 100 + 2 \times 150} = 40. \end{aligned}$$

