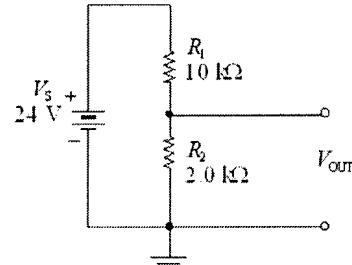


**Answer the following questions:**

**Q1:Chose the correct answer :**


1. If the current in a  $330\ \Omega$  resistor is 15 mA, the applied voltage is approximately is  
 a. 5.0 V      b. 22 V      c. 46 V      d. 60 V

2. The output voltage from the voltage divider is  
 a. 2 V  
 b. 4 V  
 c. 12 V  
 d. 20 V




3. In a closed loop, the algebraic sum of all voltages (both sources and drops)  
 a. is 0      b. is equal to the smallest voltage in the loop  
 c. is equal to the largest voltage in the loop      d. depends on the source voltage

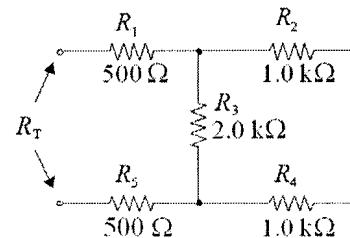4. The total resistance,  $R_T$ , of the group of resistors is  
 a. 1.0 kΩ  
 b. 2.0 kΩ  
 c. 3.0 kΩ  
 d. 4.0 kΩ



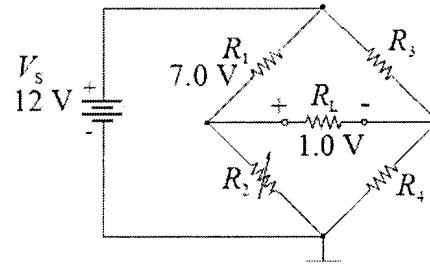5. An unbalanced Wheatstone bridge has the voltages shown. The voltage across  $R_4$  is  
 a. 4.0 V  
 b. 5.0 V  
 c. 6.0 V  
 d. 7.0 V



6. If a  $0.015\ \mu\text{F}$  capacitor is in series with a  $6800\ \text{pF}$  capacitor, the total capacitance is  
 a.  $1568\ \text{pF}$       b.  $4678\ \text{pF}$       c.  $6815\ \text{pF}$       d.  $0.022\ \mu\text{F}$
7. Maximum power is transferred from a fixed source when  
 a. the load resistor is  $\frac{1}{2}$  the source resistance      b. the load resistor is equal to the source resistance  
 c. the load resistor is twice the source resistance      d. none of the above
8. When forward biased, a diod  
 a. blocks current      b. conducts current      c. has a high resistance      d. drops a large voltage
9. The output frequency of the half wave rectifier is .....the input frequency.  
 a. half      b. same      c. twice      d. quadrupl
10. The average value of a half wave rectifier voltage with a peak value of 100 is  
 a.  $100/\pi$       b.  $200/\pi$       c.  $50/\pi$       d.  $300/\pi$

**Q2(a)** Determine the current through a  $200\text{-}\mu\text{F}$  capacitor whose voltage is shown in Fig.(1).

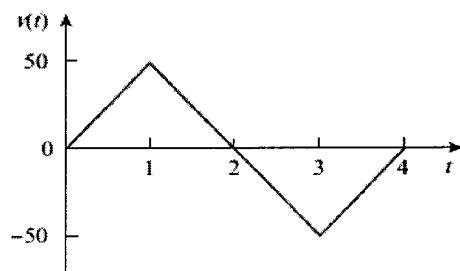


Fig.(1)

(b) Find the equivalent inductance  $L_{eq}$  seen between terminals  $a$  and  $b$  of the circuit shown in Fig. (2).

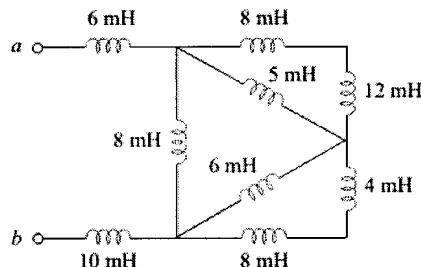


Fig.(2)

**Q3** Use the node-voltage method to find the branch currents  $i_a$ ,  $i_c$ , and  $i_e$  in the circuit shown in Fig.(3).

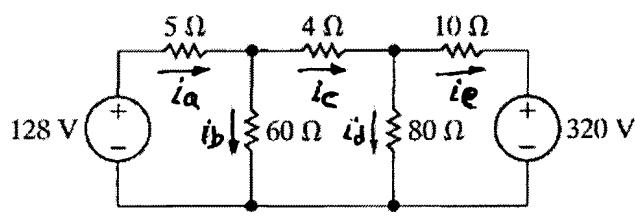


Fig.(3)

**Q4** (a) Find the value of  $R$  that enables the circuit shown in Fig.(4) to deliver maximum power to the terminals a,b.

(b) Find the maximum power delivered to  $R$ .

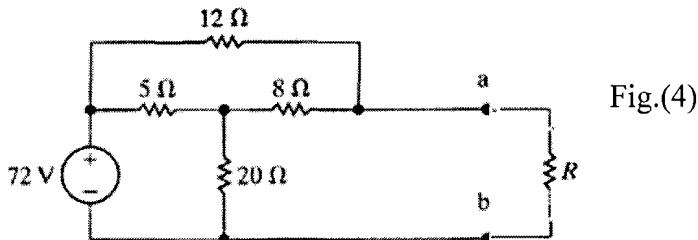


Fig.(4)

**Q5** (a) Assuming that the diodes in the circuit of Fig.(5) are ideal, find the values of the labeled voltage,  $V$ , and current,  $I$ .

(b) Describe the output voltage of the circuit shown in Fig.(6). Assuming the diodes to be ideal and  $V_1 = 10 \sin \omega t$ . Sketch one cycle of the output voltage.

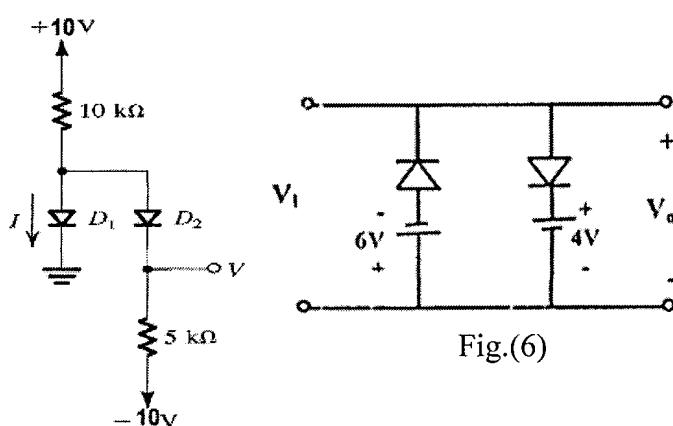


Fig.(5)

**BEST WISHES**

Hossam Labib




**Answer the following questions:**

**Q1:Chose the correct answer :**

1. If the current in a  $330 \Omega$  resistor is 15 mA, the applied voltage is approximately is  
**a. 5.0 V**


2. The output voltage from the voltage divider is

**b. 4 V**

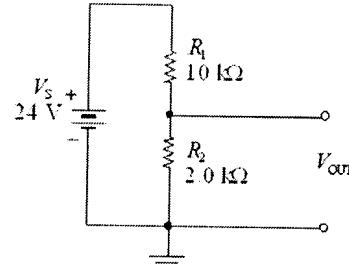


3. In a closed loop, the algebraic sum of all voltages (both sources and drops)  
**a. is 0**

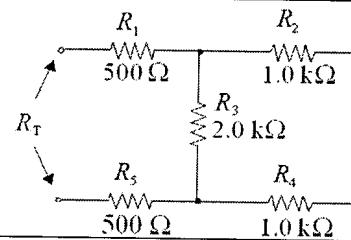4. The total resistance,  $R_T$ , of the group of resistors is  
**b.  $2.0 \text{ k}\Omega$**



5. An unbalanced Wheatstone bridge has the voltages  
 The voltage across  $R_4$  is

**a. 4.0 V**

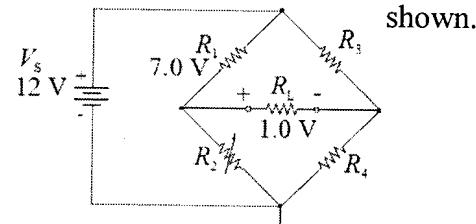

6. If a  $0.015 \mu\text{F}$  capacitor is in series with a  $6800 \text{ pF}$  capacitor, the total capacitance is  
**b.  $4678 \text{ pF}$**

7. Maximum power is transferred from a fixed source when

**b. the load resistor is equal to the source resistance**


8. When forward biased, a diod  
**b. conducts current**

9. The output frequency of the half wave rectifier is .....the input frequency.  
**b. same**

10. The average value of a half wave rectifier voltage with a peak value of 100 is  
**a.  $100/\pi$**

**Q2(a)** Determine the current through a  $200\ \mu\text{F}$  capacitor whose voltage is shown in Fig.(1).

Solution:

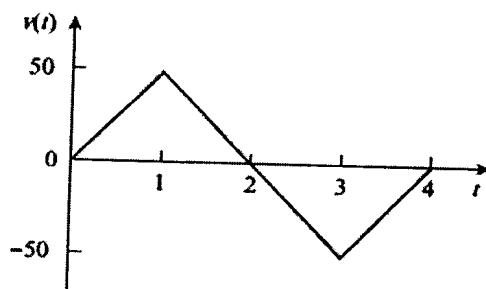


The voltage waveform can be described mathematically as

$$v(t) = \begin{cases} 50t \text{ V} & 0 < t < 1 \\ 100 - 50t \text{ V} & 1 < t < 3 \\ -200 + 50t \text{ V} & 3 < t < 4 \\ 0 & \text{otherwise} \end{cases}$$

Since  $i = C dv/dt$  and  $C = 200\ \mu\text{F}$ , we take the derivative of  $v$  to obtain


$$\begin{aligned} i(t) &= 200 \times 10^{-6} \times \begin{cases} 50 & 0 < t < 1 \\ -50 & 1 < t < 3 \\ 50 & 3 < t < 4 \\ 0 & \text{otherwise} \end{cases} \\ &= \begin{cases} 10 \text{ mA} & 0 < t < 1 \\ -10 \text{ mA} & 1 < t < 3 \\ 10 \text{ mA} & 3 < t < 4 \\ 0 & \text{otherwise} \end{cases} \end{aligned}$$

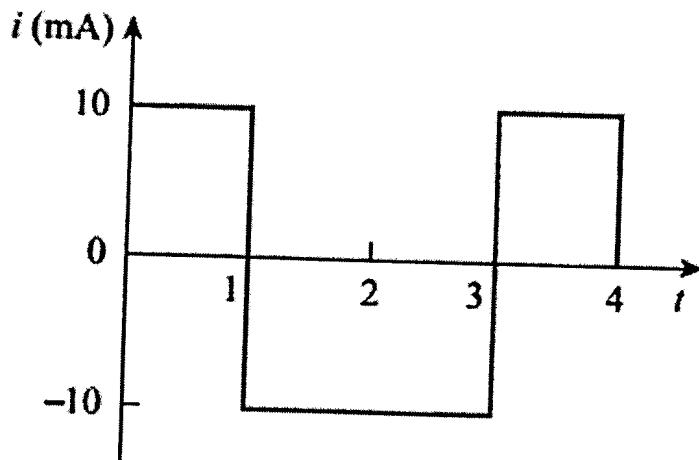Thus the current waveform is as shown in Fig.



Q<sub>2</sub>)(b)

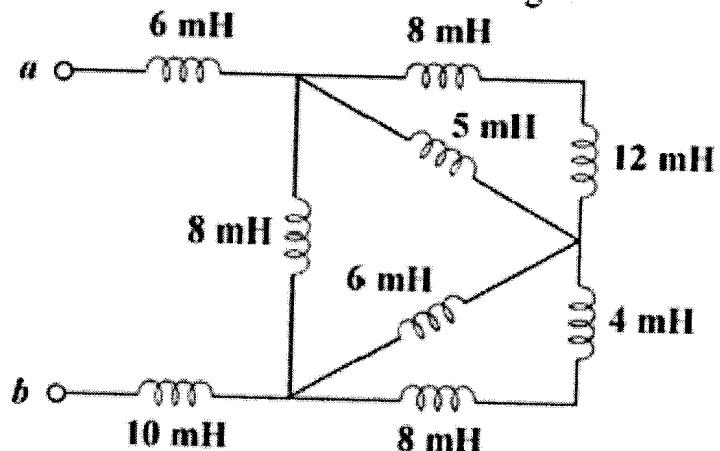Find  $L_{eq}$  at the terminals of the circuit in Fig.




Solution

$$L_{eq} = 6 + 10 + 8 \left[ \frac{5}{(8+12)} + \frac{6}{(8+4)} \right]$$

$$= 16 + 8 \left[ \frac{5}{20} + \frac{6}{12} \right] = 16 + 4$$

$$L_{eq} = \underline{\underline{20 \text{ mH}}}$$

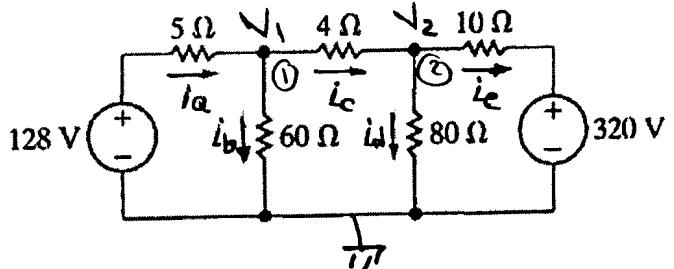Q 3) Use the node-voltage method to find the branch currents  $i_a$ ,  $i_c$ , and  $i_e$  in the circuit shown in Fig. 4.



Solution

at node(1)

$$\left( \frac{V_1 - 128}{5} + \frac{V_1 - V_2}{4} + \frac{V_1}{60} = 0 \right) * 60$$

$$12V_1 - 1536 + 15V_1 - 15V_2 + V_1 = 0$$

$$28V_1 - 15V_2 = 1536 \rightarrow ①$$

at node(2)

$$\left( \frac{V_2 - V_1}{4} + \frac{V_2}{80} + \frac{V_2 - 320}{10} = 0 \right) * 80$$

$$20V_2 - 20V_1 + V_2 + 8V_2 - 2560 = 0$$

$$-20V_1 + 29V_2 = 2560 \rightarrow ②$$

$$\text{from } ② \Rightarrow V_1 = \frac{29V_2 - 2560}{20} \rightarrow ③$$

$$\text{To } ① \Rightarrow 28 \left( \frac{29V_2 - 2560}{20} \right) - 15V_2 = 1536$$

$$40.6V_2 - 3584 - 15V_2 = 1536$$

$$25.6V_2 = 5120 \rightarrow V_2 = 200 \text{ V}$$

$$\text{To } ③ \Rightarrow V_1 = \frac{29 * 200 - 2560}{20} = 162 \text{ V}$$


$$\therefore i_a = \frac{128 - V_1}{5} = \frac{128 - 162}{5} = -6.8 \text{ A}$$

$$i_c = \frac{V_1 - V_2}{4} = \frac{162 - 200}{4} = -9.5 \text{ A}$$

$$i_e = \frac{V_2 - 320}{10} = \frac{200 - 320}{10} = -12 \text{ A}$$

**Q4** (a) Find the value of  $R$  that enables the circuit shown in Fig.(4) to deliver maximum power to the terminals a,b.

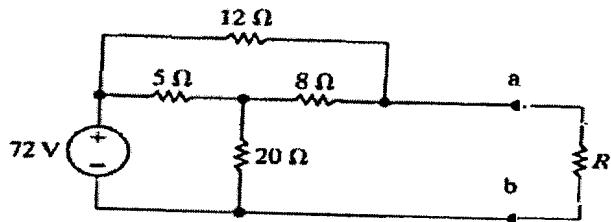(b) Find the maximum power delivered to  $R$ .



Solution:


1st find Thevenin equivalent circuit with respect to Terminal a,b  
To find  $\sqrt{V_{TH}}$

at node ①

$$\frac{\sqrt{V_1} - \sqrt{V_2}}{5} + \frac{\sqrt{V_1}}{20} + \frac{\sqrt{V_1} - \sqrt{V_{TH}}}{8} = 0 * 20$$

$$4\sqrt{V_1} - 288 + \sqrt{V_1} + 2.5\sqrt{V_1} - 2.5\sqrt{V_{TH}} = 0$$
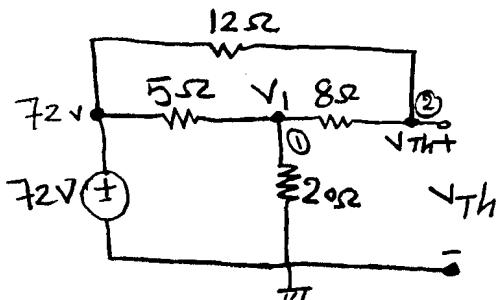
$$7.5\sqrt{V_1} - 2.5\sqrt{V_{TH}} = 288 \quad \text{--- } ①$$



at node ②

$$\frac{\sqrt{V_{TH}} - \sqrt{V_1}}{8} + \frac{\sqrt{V_{TH}} - \sqrt{V_2}}{12} = 0 * 12$$

$$1.5\sqrt{V_{TH}} - 1.5\sqrt{V_1} + \sqrt{V_{TH}} - \sqrt{V_2} = 0$$

$$2.5\sqrt{V_{TH}} - 1.5\sqrt{V_1} = 72 \quad \text{--- } ②$$

$$① + ② \Rightarrow 6\sqrt{V_1} = 360 \Rightarrow \sqrt{V_1} = 60V$$



$$\text{To } ② \therefore \sqrt{V_{TH}} = \frac{72 + 1.5 * 60}{2.5} = 64.8V$$

To find  $R_{TH}$

reduce DC sources  $\rightarrow$  V.S = S.C

$$5//20 = 4\Omega$$
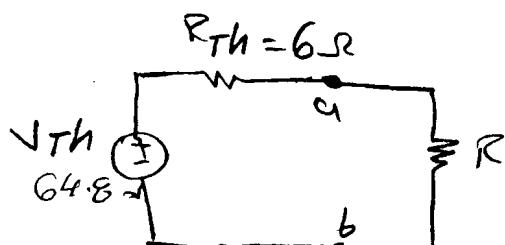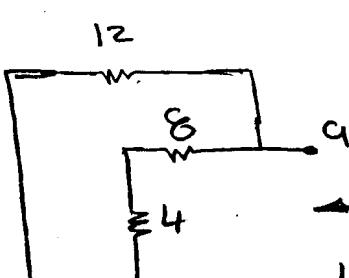
$$R_{TH} = (4+8)//12 \\ = 12//12 = 6\Omega$$



(a) For max. Power  $\Rightarrow R_L = R_{TH}$   
 $\therefore R = 6\Omega$

$$(b) P_{max} = \frac{\sqrt{V_{TH}}^2}{4R_L} = \frac{(64.8)^2}{4 \times 6} = 174.96W$$

**Q5(a)** Assuming that the diodes in the circuit of Fig.(5) are ideal, find the values of the labeled voltage,  $V$ , and current,  $I$ .

Solution


$$\text{let } I = I_{D_1}$$

let  $D_1$  and  $D_2$  are on

For  $D_1$  on  $\Rightarrow V_1 = 0 \Rightarrow V = 0$  for  $D_2$  on

$$\therefore I_1 = \frac{10 - V_1}{10K} = \frac{10 - 0}{10K} = 1 \text{ mA}$$
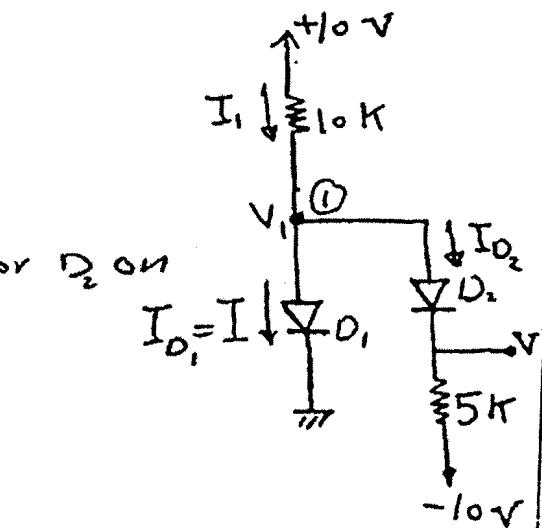
$$I_{D_2} = \frac{V_1 - (-10)}{5K} = \frac{0 + 10}{5K} = 2 \text{ mA}$$



$$\text{From Node ①} \Rightarrow I_1 = I_{D_1} + I_{D_2}$$

$$I_{D_1} = I_1 - I_{D_2} = 1 \text{ mA} - 2 \text{ mA} = -1 \text{ mA}$$

$\therefore I_{D_1}$  -ve  $\therefore$  NOT True

i.e The assumption NOT correct

Let  $D_1$  off and  $D_2$  on

For  $D_1$  off  $\Rightarrow I_{D_1} = 0 ; I_1 = I_{D_2}$

- For  $D_2$  on  $\Rightarrow I_1 = \frac{10 - (-10)}{10K + 5K} = \frac{20}{15K} = 1.333 \text{ mA}$

$$V = I_{D_2} * 5K - 10 = 1.333 * 5 - 10 = -3.335 \text{ V}$$

For  $V = -3.335 \text{ V} ; \therefore V_1 = V = V_{D_1} = -3.335 ; V_{D_2} = 0$   
i.e  $V_{D_1} < V_{D_2} \Rightarrow D_1$  off

$\therefore$  The assumption is True ( $D_1$  off &  $D_2$  on)

$$\therefore V = -3.335 \text{ V and } I = I_{D_1} = 0 \text{ A}$$

**Q5(b)** Describe the output voltage of the circuit shown in Fig.(6). Assuming the diodes to be ideal and  $V_i = 10 \sin \omega t$ . Sketch one cycle of the output voltage.

Solution:

\* for +ve half cycle.

- for  $v_i < 4$

∴  $D_1$  and  $D_2$  are off

$$\therefore v_o = v_i$$

- For  $v_i > 4$

$D_1$  on and  $D_2$  off

$$\therefore v_o = 4 \text{ V}$$

\* for -ve half cycle

- for  $v_i > -6$

$D_1$  off and  $D_2$  off

$$\therefore v_o = v_i$$

- for  $v_i < -6$

$D_1$  off and  $D_2$  on

$$\therefore v_o = -6 \text{ V}$$

