

**Answer all the following questions:**

Q1: Design a BJT differential amplifier that provides two single-ended outputs. The amplifier is to have a differential gain of at least 100 V/V, a differential input resistance  $\geq 10 \text{ k}\Omega$ , and a common mode gain no greater than 0.1 V/V. Use a 2-mA current source for biasing. Give the complete circuit with component values and suitable power supplies that allow for  $\pm 2 \text{ V}$  swing at each collector. The BJTs available have  $\beta \geq 100$ .

Q2: The 4-stages direct coupled op-amp circuit shown in Fig.(1) is operating at room temperature. Assuming all transistors have  $\beta = 200$ .

- Perform an approximate dc analysis to calculate the current and voltage everywhere in the circuit (assuming  $|V_{BE}|=0.7\text{V}$ , neglect the Early effect). Note that  $Q_6$  has four times the area of each of  $Q_9$  and  $Q_3$ .
- Compute the differential input resistance.
- Compute the overall voltage gain of the multistage amplifier.  
What is the input offset voltage if  $R_1$  changed by 2%

Q3: For the current mirror shown in Fig.(2), derive an expression for the current transfer function  $I_o(s)/I_i(s)$  as a function of transistor parameters taking into account the BJT internal capacitances and neglecting  $r_x$  and  $r_o$ . Assume the BJTs to be identical.

- Q4: Consider the complementary BJT class B output stage and neglect the effects of finite  $V_{BE}$  and  $V_{CEsat}$ . For  $\pm 10\text{V}$  power supplies and a  $100\Omega$  load resistance,
- What is the maximum sine wave output power available?
  - What is the power-conversion efficiency?
  - Show how to reduce the zero-crossing distortion in class B power amplifier?

- Q5: The circuit shown in Fig.(3) consists of a differential stage followed by an emitter follower, with series-shunt feedback supplied by the resistors  $R_1$  and  $R_2$ . Assuming that the dc component of  $V_s$  is zero, and that  $\beta$  of the BJTs is very high, find:
- The dc operating current of each of the three transistors and show that the dc voltage at the output is approximately zero.
  - The open loop gain ( $A$ ).
  - The feedback gain ( $B$ ).
  - The input resistance  $R_{in}$ , and The output resistance  $R_{out}$ . Assume that the transistors have  $\beta = 100$ .

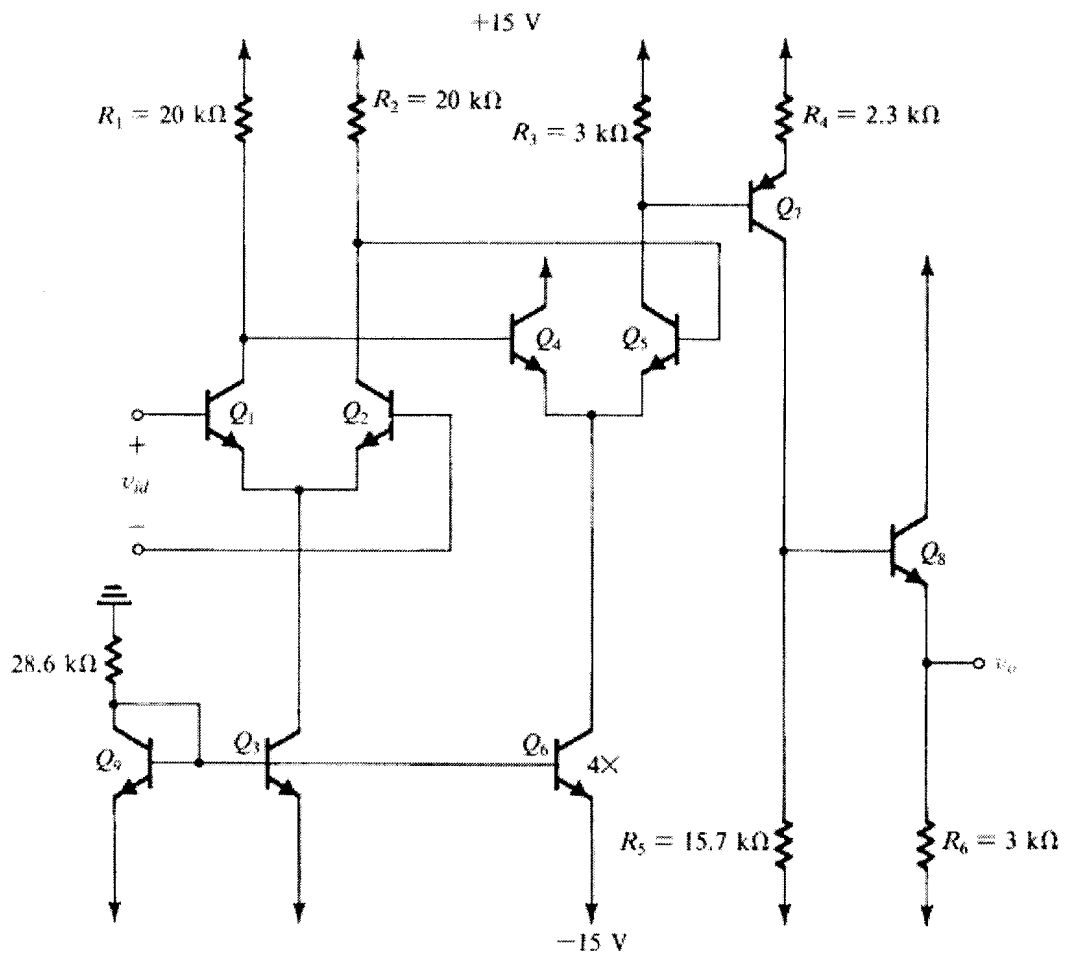


Fig. (1)

 


Fig. (2)

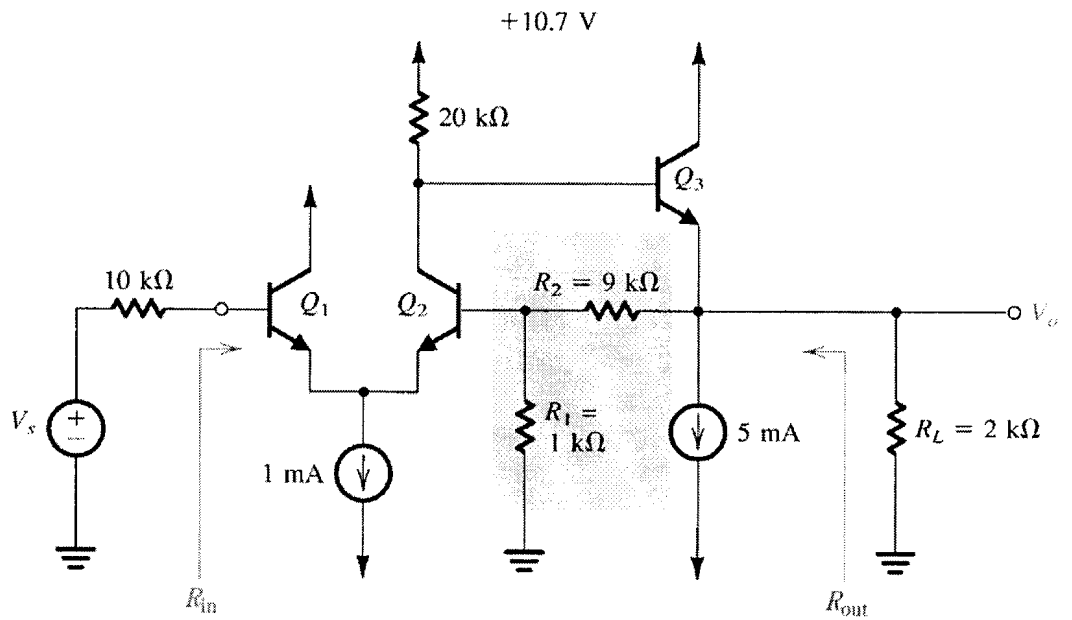


Fig. (3)

**BEST WISHES**

*Hossam Labib*

Q1: Design a BJT differential amplifier that provides two single-ended outputs. The amplifier is to have a differential gain of at least 100 V/V, a differential input resistance  $\geq 10 \text{ k}\Omega$ , and a common mode gain no greater than 0.1 V/V. Use a 2-mA current source for biasing. Give the complete circuit with component values and suitable power supplies that allow for  $\pm 2 \text{ V}$  swing at each collector. The BJTs available have  $\beta \geq 100$ .

**Solution:**

From DC

$$\therefore 2 I_E = I \Rightarrow I_E = \frac{I}{2}$$

$$\therefore I_E = 1 \text{ mA}$$

$$r_e = \frac{V_T}{I_E} = \frac{25 \text{ mV}}{1 \text{ mA}} = 25 \Omega$$

$$\therefore R_{id} \geq 10 \text{ k}\Omega \Rightarrow \text{Let } R_{id} = 10 \text{ k}\Omega$$

$$\beta \geq 100 \Rightarrow \beta = 100$$

For  $r_e = 25 \Omega \Rightarrow$  There must be  $R_E$  in the differential amplifier to meet the design requirement of  $R_{id} \geq 10 \text{ k}\Omega$ .

$$\therefore R_{id} = 2(1 + \beta)(r_e + R_E)$$

$$10 \text{ k} = 2(1 + 100)(25 + R_E)$$

$$R_E = \frac{10 \text{ k}}{2 \times 101} - 25 = 25 \Omega$$

- For differential gain  $A_d = 100 \text{ V/V}$  and two single ended OIP  $\Rightarrow A_d = \frac{V_o}{V_{id}} = \frac{V_{c1}}{V_{id}} = \frac{\text{Total resistance at collector}}{\text{Total resistance at emitter}}$


$$A_d = \frac{R_c}{2r_e + 2R_E} = \frac{R_c}{2(r_e + R_E)} = 100$$

$$100 = \frac{R_c}{2(25 + 25)} \Rightarrow R_c = 10 \text{ k}\Omega$$

- For  $\pm 2 \text{ V}$  swing  $\Rightarrow V_{c1} = V_{c2} = 2 \text{ V} = V_c$

$$\therefore V_c = V_{cc} - I_c R_c \Rightarrow V_{cc} = V_c + I_c R_c = 2 + 1 \text{ mA} \times 10 \text{ k}$$

 
$$V_{cc} = 12 \text{ V} \quad \text{Then } V_{cc} = \pm 12 \text{ V}$$



Q2:

The 4-stages direct coupled op-amp circuit shown in Fig.1 is operating at room temperature. Assuming all transistors have  $\beta = 200$

- Perform an approximate dc analysis to calculate the current and voltage everywhere in the circuit (assuming  $|V_{BE}|=0.7V$ , neglect the Early effect). Note that  $Q_6$  has four times the area of each of  $Q_9$  and  $Q_3$ .
- Compute the differential input resistant.
- Compute the overall voltage gain of the multistage amplifier.
- What is the input offset voltage if  $R_1$  changed by 2%

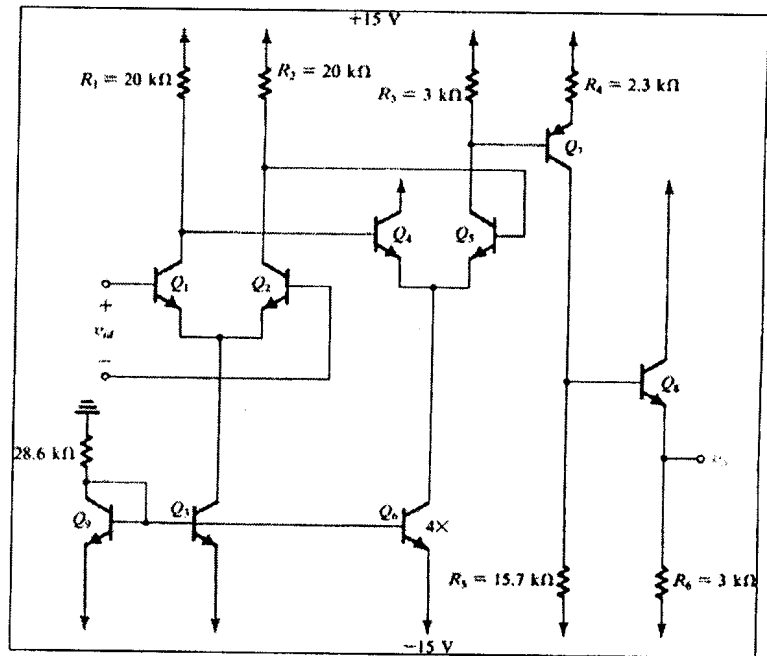


**Solution:**

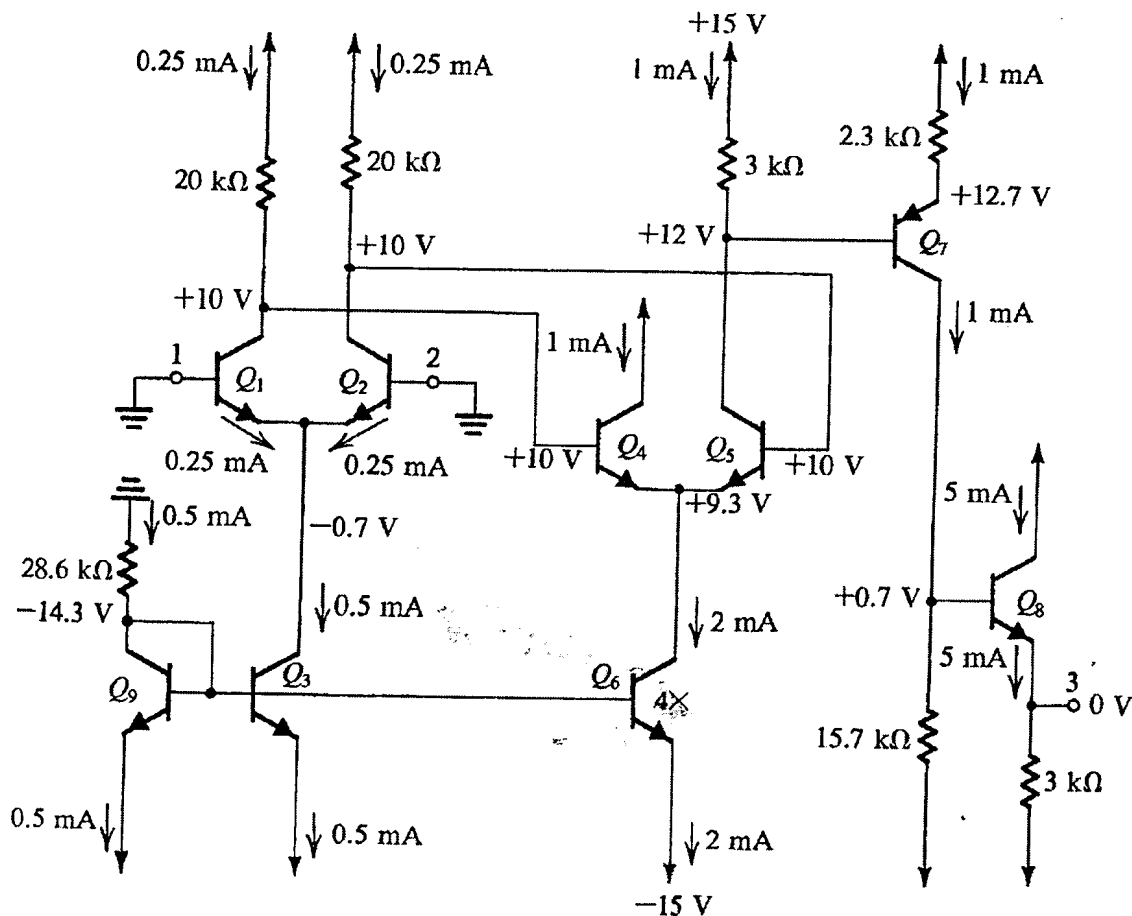(a) The values of all dc currents and voltages are indicated on the circuit diagram. These values were calculated by ignoring the base current of every transistor—that is, by assuming  $\beta$  to be very high. The analysis starts by determining the current through the diode-connected transistor  $Q_9$  to be 0.5 mA. Then we see that transistor  $Q_3$  conducts 0.5 mA and transistor  $Q_6$  conducts 2mA. The current-source transistor  $Q_3$  feeds the differential pair ( $Q_1, Q_2$ ) with 0.5 mA. Thus each of  $Q_1$  and  $Q_2$  will be biased at 0.25 mA. The collectors of  $Q_1$  and  $Q_2$  will be at  $[+15 - 0.25 \times 20] = +10 V$ .

Proceeding to the second differential stage formed by  $Q_4$  and  $Q_5$ , we find the voltage at their emitters to be  $[+10 - 0.7] = 9.3 V$ . This differential pair is biased by the current-source transistor  $Q_6$ , which supplies a current of 2 mA; thus  $Q_4$  and  $Q_5$  will each be biased at 1 mA. We can now calculate the voltage at the collector of  $Q_5$  as  $[+15 - 1 \times 3] = +12 V$ . This will cause the voltage at the emitter of the pnp transistor  $Q_7$  to be + 12. 7 V, and the emitter current of  $Q_7$  will be  $(+15 - 12.7)/2.3 = 1 mA$ . The collector current of  $Q_7$ , 1 mA, causes the voltage at the collector to be  $[-15 + 1 \times 15.7] = +0.7 V$ . The emitter of  $Q_8$  will be 0.7 V below the base; thus output terminal 3 will be at 0 V.

Finally, the emitter current of  $Q_8$  can be calculated to be  $[0 - (-15)]/3 = 5 mA$ .



(b) The input differential resistance  $R_{id}$  is given by:

$$R_{id} = r_{\pi 1} + r_{\pi 2}$$

Since  $Q_1$  and  $Q_2$  are each operating at an emitter current of 0.25 mA, it follows that

$$r_{e1} = r_{e2} = 25 / 0.25 = 100 \Omega$$

for  $\beta = 200$ ; then

$$r_{\pi 1} = r_{\pi 2} = 201 \times 100 = 20.1 \text{ k}\Omega$$

Thus  $R_{id} = 40.2 \text{ k}\Omega$

(c) To evaluate the gain of the first stage we first find the input resistance of the second stage,  $R_{i2}$ ,


$$R_{i2} = r_{\pi 4} + r_{\pi 5}$$

$Q_4$  and  $Q_5$  are each operating at an emitter current of 1 mA; thus

$$r_{e4} = r_{e5} = 25 \Omega$$

$$r_{\pi 4} = r_{\pi 5} = 201 \times 25 = 5.025 \text{ k}\Omega$$

Thus  $R_{i2} = 10.05 \text{ k}\Omega$ .

 

This resistance appears between the collectors of Q1 and Q2, as shown in - Fig. Thus the gain of the first stage will be

$$A1 \equiv \frac{v_{o1}}{v_{id}} \cong \frac{\text{Total resistance in collector circuit}}{\text{Total resistance in emitter circuit}} = \frac{R_{i2} \parallel (R_1 + R_2)}{r_{e1} + r_{e2}}$$

$$= \frac{10.05k \parallel 40k}{200} = \frac{8031.97}{200} = 40.16 \text{ V/V}$$

Figure 2 shows an equivalent circuit for calculating the gain of the second stage. As indicated, the input voltage to the second stage is the input voltage of the first stage,  $v_{o1}$ . Also shown is the resistance  $R_{i3}$  which is the input resistance of the third stage formed by Q7. The value of  $R_{i3}$  can be found by multiplying the total resistance in the emitter of Q7 by  $(\beta + 1)$ :

$$R_{i3} = (\beta + 1)(R_4 + r_{e7})$$

Since Q7 is operating at an emitter current of 1 mA,  
 $r_{e7} = 25/1 = 25\Omega$

$$R_{i3} = 201 \times (2.3k + 25) = 467.325 \text{ k}\Omega$$

We can now find the gain A2 of the second stage as the ratio of the total resistance in the collector circuit to the total resistance in the emitter circuit:

$$A2 = \frac{v_{o2}}{v_{o1}} = - \frac{(R_3 \parallel R_{i3})}{r_{e4} + r_{e5}}$$

$$= - \frac{(3k \parallel 467.325k)}{50} = \frac{2980.86}{50} = -59.6 \text{ V/V}$$



To obtain the gain of the third stage we refer to the equivalent circuit shown in Fig., where  $R_{i4}$  is the input resistance of the output stage formed by Q8. Using reflection resistance-reflection rule, we calculate the value of  $R_{i4}$  as

$$R_{i4} = (\beta + 1)(r_{e8} + R_6)$$

where

$$r_{e8} = 25/5 = 5\Omega$$
  
$$R_{i4} = 201(5 + 3000) = 604.005 \text{ k}\Omega$$



The gain of the third stage is given by

$$A3 \equiv \frac{v_{o3}}{v_{o2}} = -\frac{(R_5 \parallel R_{i4})}{r_{e7} + R_4} = -\frac{(15.7k \parallel 604.005k)}{25 + 2.3k}$$


$$= -\frac{15.302k}{2.325k} = -6.58 \text{ V/V}$$

Finally, to obtain the gain  $A4$  of the output stage we refer to the equivalent circuit in Fig. and write

$$A4 \equiv \frac{v_o}{v_{o3}} = \frac{R_6}{R_6 + r_{e8}} = \frac{3000}{3000 + 5} = 0.998 \approx 1$$

The overall voltage gain of the amplifier can then be obtained as follows:
 
$$\frac{v_o}{v_{id}} = A1A2A3A4 = 40.16 \times -59.6 \times -6.58 \times 1 = 15749.5$$





(d) The input offset voltage if  $R_1$  changed by 2%

The input offset voltage  $V_{os}$

$$|V_{os}| = V_T \left( \frac{\Delta R_c}{R_c} \right) = V_T \left( \frac{\Delta R_1}{R_1} \right) = 25m \times 0.02 = 0.5mV$$

Q3: For the current mirror shown in Fig.(2), derive an expression for the current transfer function  $I_o(s)/I_i(s)$  as a function of transistor parameters taking into account the BJT internal capacitances and neglecting  $r_x$  and  $r_o$ . Assume the BJTs to be identical.

**Solution:**

 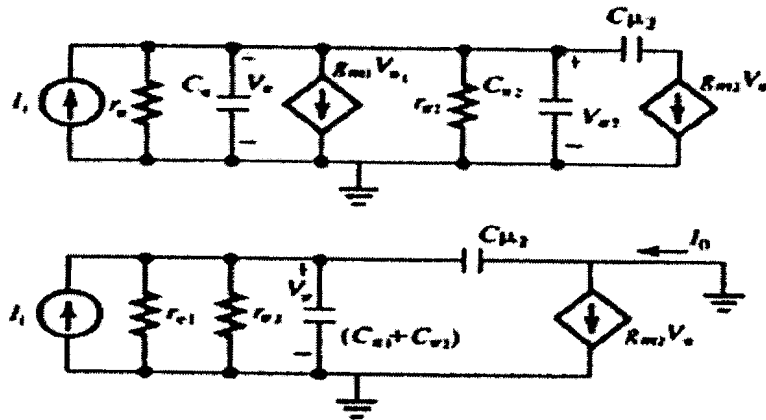

$$V_w = \frac{I_i}{\left(\frac{1}{r_{e1}} + \frac{1}{r_{w2}}\right) + s(C_{w1} + C_{w2} + C_{\mu2})}$$

$$I_o = g_{m2} V_w - C_{\mu2} s V_w$$

$$= \frac{(g_{m2} - C_{\mu2} s) I_i}{\left(\frac{1}{r_{e1}} + \frac{1}{r_{w2}}\right) + s(C_{w1} + C_{w2} + C_{\mu2})}$$

$$\frac{I_o}{I_i} = \frac{g_{m2} - C_{\mu2} s}{\left(\frac{1}{r_{e1}} + \frac{1}{r_{w2}}\right) + s(C_{w1} + C_{w2} + C_{\mu2})}$$

$$I_{C1} = I_{C2} \Rightarrow r_{w1} = r_{w2}$$

$$g_{m1} = g_{m2}, C_{w1} = C_{w2}$$

$$\frac{I_o}{I_i} = \frac{g_m - C_{\mu} s}{\left(\frac{1}{r_e} + \frac{1}{r_w}\right) + (C_{\mu} + 2C_w) s}$$

$$= \frac{1 - \frac{C_{\mu} s}{g_m}}{\left(\frac{1}{g_m r_e} + \frac{1}{g_m r_w}\right) + s \frac{C_{\mu} + 2C_w}{g_m}}$$

$$g_m r_e = \frac{I_C V_T}{I_E} = \alpha = \frac{\beta}{\beta + 1}$$

$$g_m r_w = \beta$$

$$\Rightarrow \frac{I_o}{I_i} = \frac{1 - \frac{C_{\mu} s}{g_m}}{1 + \frac{1}{\beta} + \frac{1}{\beta} + s(2C_w + C_{\mu}) / g_m}$$

$$\frac{I_o}{I_i} = \frac{1}{1 + \frac{2}{\beta}} \frac{1 - s \frac{C_{\mu}}{g_m}}{1 + s \frac{(2C_w + C_{\mu})}{g_m \left(1 + \frac{2}{\beta}\right)}}$$



Q4:

Consider the complementary BJT class B output stage and neglect the effects of finite  $V_{BE}$  and  $V_{CEsat}$ . For  $\pm 10V$  power supplies and a  $100\Omega$  load resistance,

- What is the maximum sine wave output power available?
- What is the power-conversion efficiency?
- Show how to reduce the zero-crossing distortion in class B power amplifier?

Solution

(a) The average load power:  $P_L = \frac{1}{2} \frac{\hat{V}_o^2}{R_L}$

where  $\hat{V}_o$  is the peak amplitude of o/p sine wave.

The maximum sine-wave o/p power occurs when  $\hat{V}_o = V_{CC}$  then

$$P_L|_{max} = \frac{1}{2} \frac{V_{CC}^2}{R_L} = \frac{1}{2} \frac{(10)^2}{100} = 0.5 \text{ W}$$

(b) The power conversion efficiency  $\eta = \frac{P_L}{P_S}$

where  $P_S$  is the total supply power

$$P_S = P_{S+} + P_{S-}$$

$\therefore$  The average power drawn from each of the two power supplies will be the same. - Then

$$P_{S+} = P_{S-} = \frac{1}{\pi} \frac{\hat{V}_o}{R_L} V_{CC} = \frac{1}{\pi} \frac{(10)}{100} \times 10 = 0.318 \text{ W}$$

$$\therefore P_S = 2 \times 0.318 = 0.637 \text{ W}$$



$\therefore$  The power conversion efficiency  $\eta$  is

$$\eta = \frac{P_L}{P_S} \times 100 = \frac{0.5}{0.637} \times 100 = 78.5 \%$$

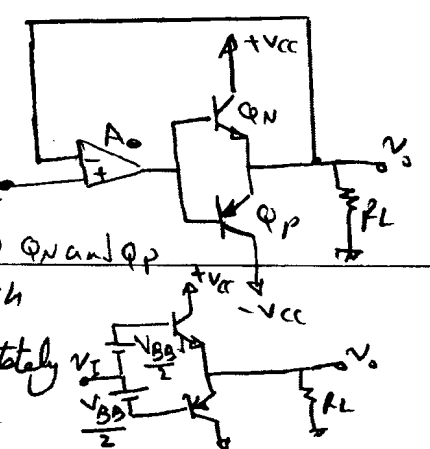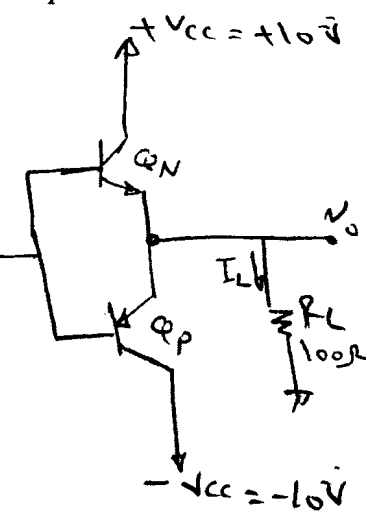
(c) - To reduce the zero-crossing distortion in class B Power Amp. by using a high-gain op-amp. and overall negative feedback as shown. The  $\pm 0.7V$  dead band is reduced to  $\pm 0.7/A_o$  volt.

where  $A_o$  is the DC gain of op-amp.

- OR by biasing the complementary transistors using bias voltage  $V_{BS}$  applied between the bases of  $Q_N$  and  $Q_P$  giving rise to bias current  $I_Q$ . Thus for small  $V_I$ , both transistors conduct and crossover distortion is almost completely eliminated. as shown in fig. (class AB o/p stage)



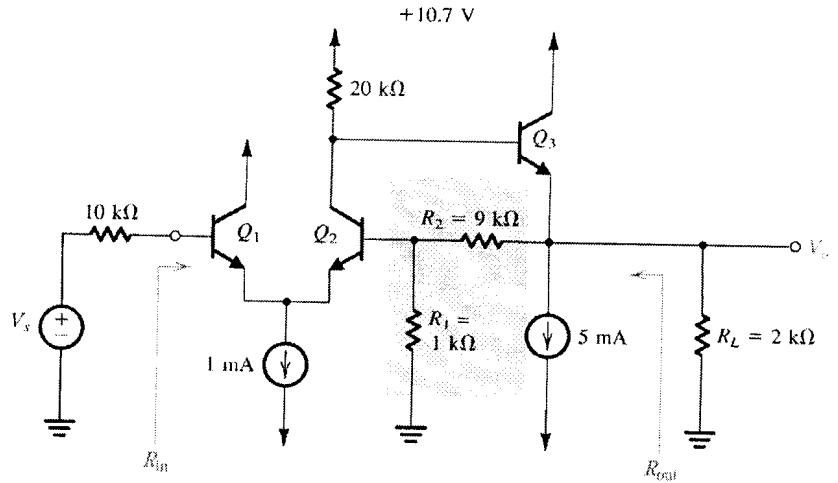Q5: The circuit shown in Fig.( ) consists of a differential stage followed by an emitter follower, with series-shunt feedback supplied by the resistors  $R_1$  and  $R_2$ . Assuming that the dc component of  $V_s$  is zero, and that  $\beta$  of the BJTs is very high, find:



- The dc operating current of each of the three transistors and show that the dc voltage at the output is approximately zero.
- The open loop gain ( $A$ ).
- The feedback gain ( $B$ ).
- The input resistance  $R_{in}$ , and The output resistance  $R_{out}$ . Assume that the transistors have  $\beta = 100$ .

**Solution:**

$$I_{E1} = I_{E2} = 0.5 \text{ mA}$$


$$V_{C2} = 10.7 - 0.5 \times 20 = +0.7 \text{ V}$$

$$V_o = 0.7 - V_{BE3} = 0$$

$$I_{E3} = 5 \text{ mA}$$

$$r_{e1} = r_{e2} = V_A / I = 50 \Omega, r_{e3} = 5 \Omega$$

A-Circuit:

 

$$A = \frac{V_o}{V_i} = \frac{[20 \parallel (\beta_2 + 1)(r_{e3} + 2 \parallel 10)]}{r_{e1} + r_{e2} + \frac{10}{\beta_1 + 1} + \frac{(1 \parallel 9)}{\beta_2 + 1}} \times$$


$$\frac{(2 \parallel 10)}{r_{e3} + (2 \parallel 10)} = 85.7 \text{ V/V}$$

$$R_i = R_s + (\beta + 1)(r_{e1} + r_{e2}) + R_E \parallel R_4$$

$$= 10 + 101(50 + 50) + (1 \parallel 9) = 21 \text{ k}\Omega$$

$$R_o = 2 \parallel 10 \parallel \left[ r_{e3} + \frac{20}{\beta_2 + 1} \right] = 181 \Omega$$

B-Circuit:

 

$$\beta = V_i' / V_o'$$

$$= \frac{1}{9 + 1} = 0.1 \text{ V/V}$$

$$A_f = \frac{V_o}{V_s} = \frac{A}{1 + A\beta} = \frac{85.7}{1 + 85.7 \times 0.1} = 8.96 \text{ V/V}$$

$$R_{if} = R_i(1 + A\beta) = 21 \times 9.57 = 201 \text{ k}\Omega$$

$$R_{in} = R_{if} - R_s = 201 - 10 = 191 \text{ k}\Omega$$

$$R_{of} = (R_{out} \parallel R_L) = \frac{R_o}{1 + A\beta} = \frac{181}{9.57} = 18.8 \Omega$$

$$\Rightarrow R_{out} = 19.1 \Omega$$