




Model Answer

Q1

Solved exactly in lecture.

Q2

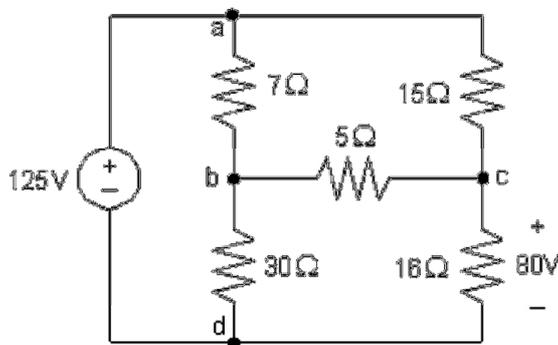

$$i_{cd} = 80/16 = 5 \text{ A}$$

$$v_{ac} = 125 - 80 = 45 \quad \text{so} \quad i_{ac} = 45/15 = 3 \text{ A}$$

$$i_{ac} + i_{bc} = i_{cd} \quad \text{so} \quad i_{bc} = 5 - 3 = 2 \text{ A}$$

$$v_{ab} = 15i_{ac} - 5i_{bc} = 15(3) - 5(2) = 35 \text{ V} \quad \text{so} \quad i_{ab} = 35/7 = 5 \text{ A}$$

$$i_{bd} = i_{ab} - i_{bc} = 5 - 2 = 3 \text{ A}$$

Calculate the power dissipated by the resistors using the equation

$$p_R = Ri_R^2:$$

$$p_{7\Omega} = (7)(5)^2 = 175 \text{ W} \quad p_{30\Omega} = (30)(3)^2 = 270 \text{ W}$$

$$p_{15\Omega} = (15)(3)^2 = 135 \text{ W} \quad p_{16\Omega} = (16)(5)^2 = 400 \text{ W}$$

$$p_{5\Omega} = (5)(2)^2 = 20 \text{ W}$$

[b] Calculate the current through the voltage source:

$$i_{ad} = -i_{ab} - i_{ac} = -5 - 3 = -8 \text{ A}$$

Now that we have both the voltage and the current for the source, we can calculate the power supplied by the source:

$$p_g = 125(-8) = -1000 \text{ W} \quad \text{thus} \quad p_g \text{ (supplied)} = 1000 \text{ W}$$


[c] $\sum P_{\text{dis}} = 175 + 270 + 135 + 400 + 20 = 1000 \text{ W}$

Therefore,


$$\sum P_{\text{supp}} = \sum P_{\text{dis}}$$

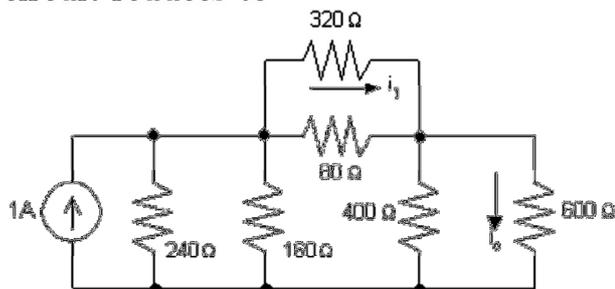Q3

After the $20 \Omega - 100 \Omega - 50 \Omega$ wye is replaced by its equivalent delta, the circuit reduces to




Now the circuit can be reduced to

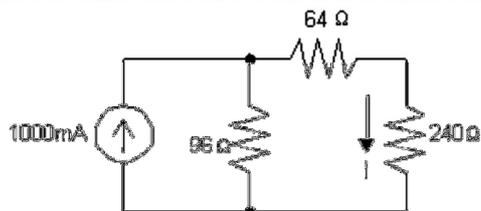

Then $R_{\text{total}} = 96 \cdot 304 / 400 =$

Q4

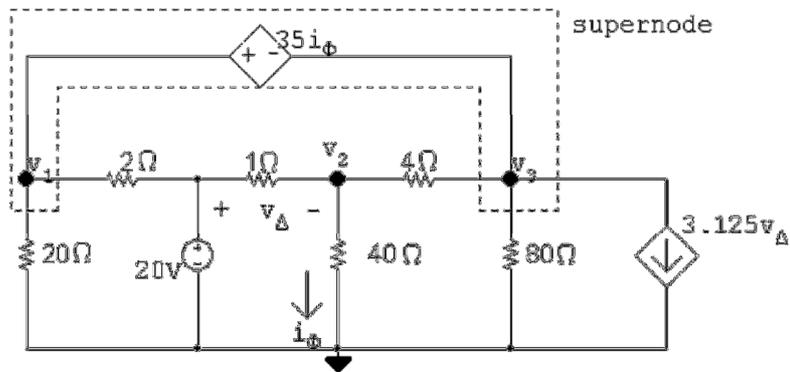

Node equations:

$$\frac{v_1}{20} + \frac{v_1 - 20}{2} + \frac{v_3 - v_2}{4} + \frac{v_3}{80} + 3.125v_\Delta = 0$$

$$\frac{v_2}{40} + \frac{v_2 - v_3}{4} + \frac{v_2 - 20}{1} = 0$$

Constraint equations:

$$v_\Delta = 20 - v_2$$

$$v_1 - 35i_\phi = v_3$$

$$i_\phi = v_2/40$$

$$\text{Solving, } v_1 = -20.25 \text{ V; } v_2 = 10 \text{ V; } v_3 = -29 \text{ V}$$

Let i_g be the current delivered by the 20 V source, then


$$i_g = \frac{20 - (20.25)}{2} + \frac{20 - 10}{1} = 30.125 \text{ A}$$

$$p_g (\text{delivered}) = 20(30.125) = 602.5 \text{ W}$$

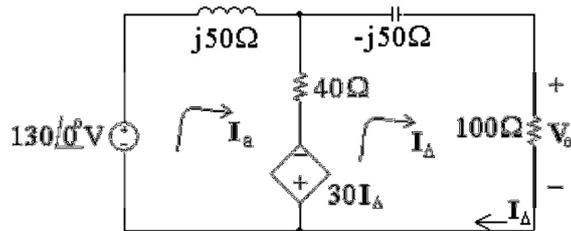Q5

$$j\omega L = j10,000(5 \times 10^{-3}) = j50 \Omega$$

$$\frac{1}{j\omega C} = \frac{-j}{(10,000)(2 \times 10^{-6})} = -j50 \Omega$$



$$130\angle 0^\circ = (40 + j50)\mathbf{I}_a - 40\mathbf{I}_\Delta + 30\mathbf{I}_\Delta$$

$$0 = -40\mathbf{I}_a + 30\mathbf{I}_\Delta + (140 - j50)\mathbf{I}_\Delta$$

Solving,

$$\mathbf{I}_\Delta = (400 - j400) \text{ mA}$$


$$\mathbf{V}_o = 100\mathbf{I}_\Delta = 40 - j40 = 56.57\angle -45^\circ$$

$$v_o = 56.57 \cos(10,000t - 45^\circ) \text{ V}$$

Q6


[a] Superposition must be used because the frequencies of the two sources are different.

[b] For $\omega = 2000$ rad/s:

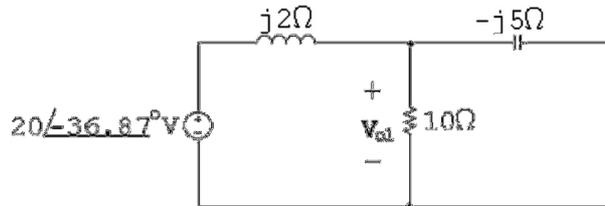

$$10 \parallel -j5 = 2 - j4 \Omega \quad \text{so} \quad \mathbf{V}_{o1} = \frac{2 - j4}{2 - j4 + j2} (20 \angle -36.87^\circ) = 31.62 \angle -55.3^\circ \text{ V}$$

For $\omega = 5000$ rad/s:

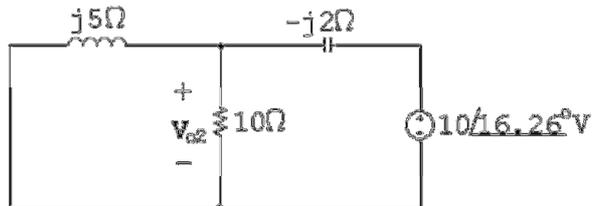

$$j5 \parallel 10 = 2 + j4 \Omega$$

$$\mathbf{V}_{o2} = \frac{2 + j4}{2 + j4 - j2} (10 \angle 16.26^\circ) = 15.81 \angle 34.69^\circ \text{ V}$$

Thus,

$$v_o(t) = [31.62 \cos(2000t - 55.3^\circ) + 15.81 \cos(5000t + 34.69^\circ)] \text{ V}, \quad t \geq 0$$